



National Institute Of Technology Durgapur

ELECTRICAL MEASUREMENT LABORATORY Group V

Experiment 1

MEASUREMENT OF POWER IN SINGLE-PHASE CIRCUIT BY
THREE-VOLTMETER METHOD AND THREE-AMMETER METHOD

2nd June, 2021

Members (63-77)

- | | |
|----------------------------|--------------------------|
| ✓ Sayan Mondal (63) | ✓ Subham Gupta (71) |
| ✓ Abantika Saha (64) | ✓ Tuhin Karak (72) |
| ✓ Sayan Das (65) | ✓ Souradeepta Pal (73) |
| ✓ Raj Suyash Ranjan (66) | ✓ Koustav Sanyal (74) |
| ✓ Vemula Rahul (67) | ✓ Diksha Senapati (75) |
| ✓ Sohini Bhattacharya (68) | ✓ Aman Kumar (76) |
| ✓ Anirban Moi (69) | ✓ Yogeswar Sarnakar (77) |
| ✓ Dheeraj Kalakonda (70) | |

Experiment No: 1

Measurement Of Power in Single-Phase Circuit by Three-Voltmeter Method and Three-Ammeter Method

Objective:

- To measure the single-phase power in a single-phase A.C. circuit by using three voltmeters.
- To measure the single-phase power in a single-phase A.C. circuit by using three ammeters.



Apparatus Required:

It consists of following instruments:

Sl. No.	Instrument Name	Specification	Quantity
1.	AC Voltage Supply	20V rms, 50 Hz	1
2.	Ammeter	0 - 35 A (AC)	3
3.	Voltmeter	0 - 50 V (AC)	3
4.	Resistors	1.7Ω, 1.8Ω, 1.9Ω, 2.0Ω	4
5.	RL load	R = 1 Ω, L = 3 mH	1
6.	Connecting Wires	-	-

Theory:

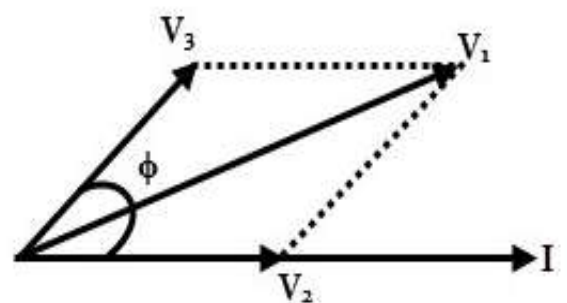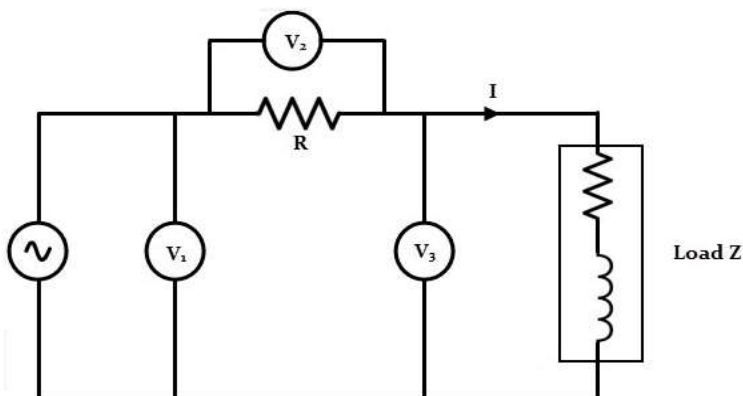Power measurement in Single phase A.C. circuit by using three voltmeters:



From the phasor diagram,

$$V_1^2 = V_2^2 + V_3^2 + 2V_2V_3 \cos \phi \quad \longrightarrow (1)$$

But,

$$V_2 = IR$$

Sayan Mondal Abantika Saha Sayan Das Raj Saha Tanula Pal Sohini Bhattacharya Anirban Moi
K.Dhanyashree Subhom Gupta Tukin Karak Souradepta Pal Koustav Sanyal DSenapati Aman Kumar Jyotirmay Samanta

Therefore,

$$V_1^2 = V_2^2 + V_3^2 + 2(IR)V_3 \cos \phi \quad \longrightarrow (2)$$

Now, power consumed by load $\Rightarrow P = V_3 I \cos \phi$

Therefore, equation (2) gives,

$$V_1^2 = V_2^2 + V_3^2 + 2PR$$



$$\Rightarrow P = \frac{V_1^2 - V_2^2 - V_3^2}{2R} \quad \longrightarrow (3)$$

Now, simplifying equation (1),

$$\cos \phi = \frac{V_1^2 - V_2^2 - V_3^2}{2V_2 V_3} \quad \longrightarrow (4)$$

From equations (3) and (4), it can be observed that the power and power factor in an A.C. circuit can be measured by using three single-phase voltmeters, instead of a wattmeter.

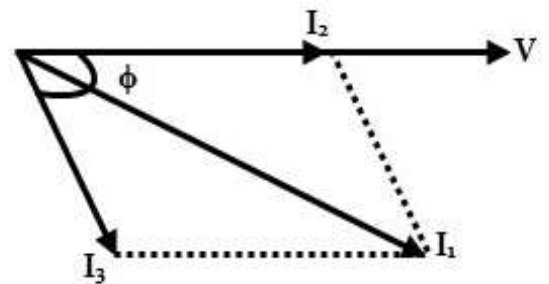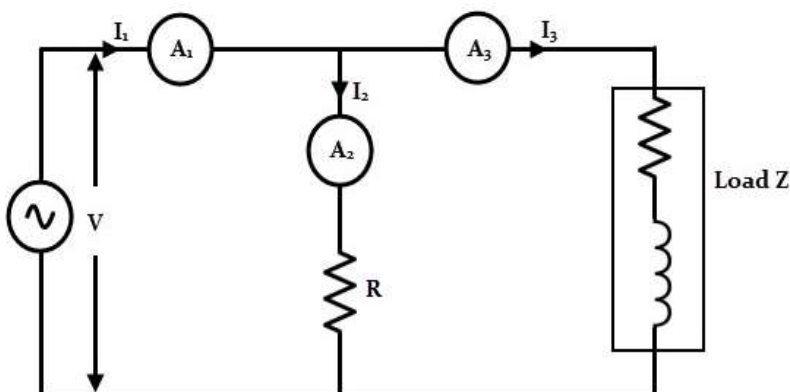Power measurement in Single phase A.C. circuit by using three ammeters:



From the phasor diagram,

$$I_1^2 = I_2^2 + I_3^2 + 2I_2 I_3 \cos \phi \quad \longrightarrow (1)$$

But,

$$I_2 = \frac{V}{R}$$

Therefore,

$$I_1^2 = I_2^2 + I_3^2 + 2\left(\frac{V}{R}\right) I_3 \cos \phi \quad \longrightarrow (2)$$

Sayan Mondal *Abantika Saha* *Sayan Das* *Devi Saha* *Devi Saha* *Sohini Bhattacharya* *Amirbanu Moir*
K.Dharmajyoti *Sudhansu Gupta* *Tuhin Karak* *Souradeepa Pal* *Koustav Sanyal* *Dipenapati* *Aman Kumar* *Jyoti Sanyal*

Now, power across load, $P = VI_3 \cos \varphi$

Therefore, equation (2) gives,

$$I_1^2 = I_2^2 + I_3^2 + 2 \left(\frac{P}{R} \right)$$

$$P = \left(\frac{I_1^2 - I_2^2 - I_3^2}{2} \right) R \longrightarrow (3)$$

Now, simplifying equation (1),

$$\cos \varphi = \frac{I_1^2 - I_2^2 - I_3^2}{2I_2I_3} \longrightarrow (4)$$

From equations (3) and (4), it can be observed that the power and power factor in an A.C. circuit can be measured by using three single-phase ammeters, instead of a wattmeter.

Schematic Circuit Diagram:

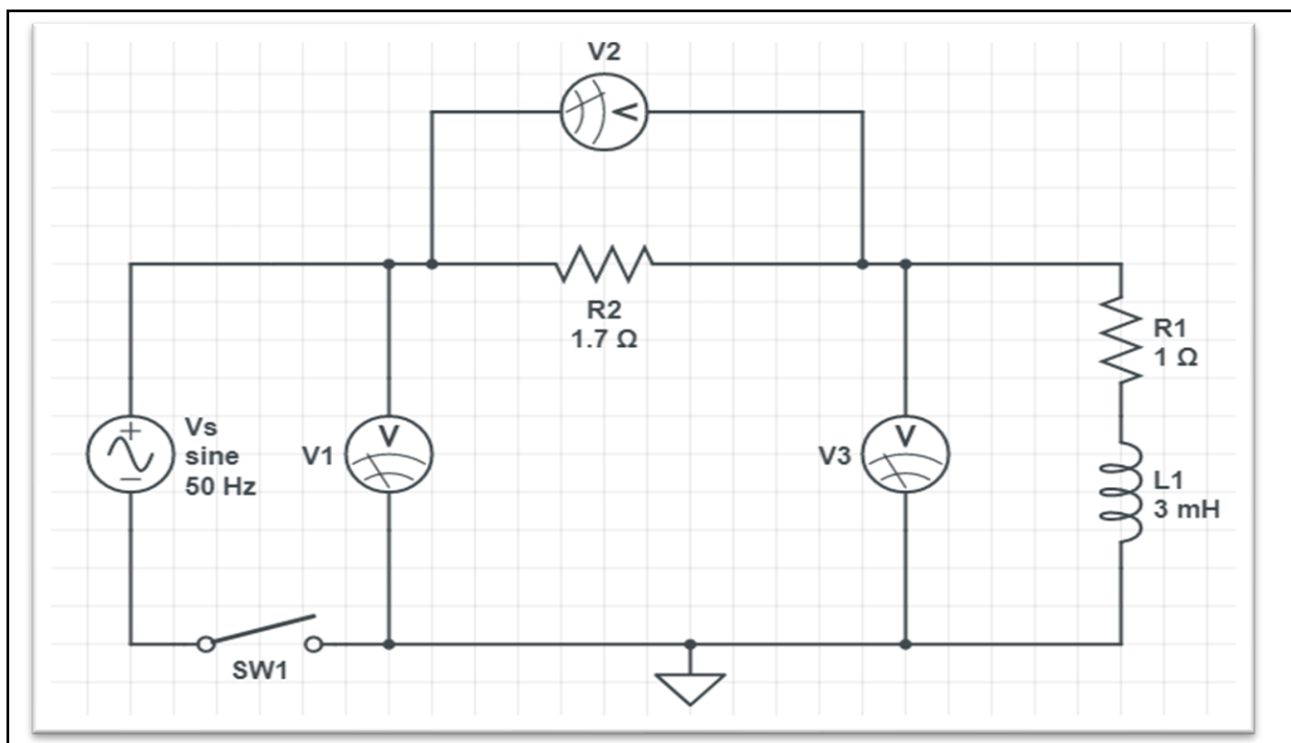


Figure 1 : Circuit Diagram for Three Voltmeter Method when $R = 1.7 \Omega$

Sayan Mondal Abantika Saha Sayan Das Raj Saha Tanu Pal Sohini Bhattacharya Anirban Maiti
 K.Dharmajyoti Subham Gupta Tuhin Karak Souvadepta Pal Koustav Sanyal D. Senapati Aman Kumar Jyotirmay Samanta

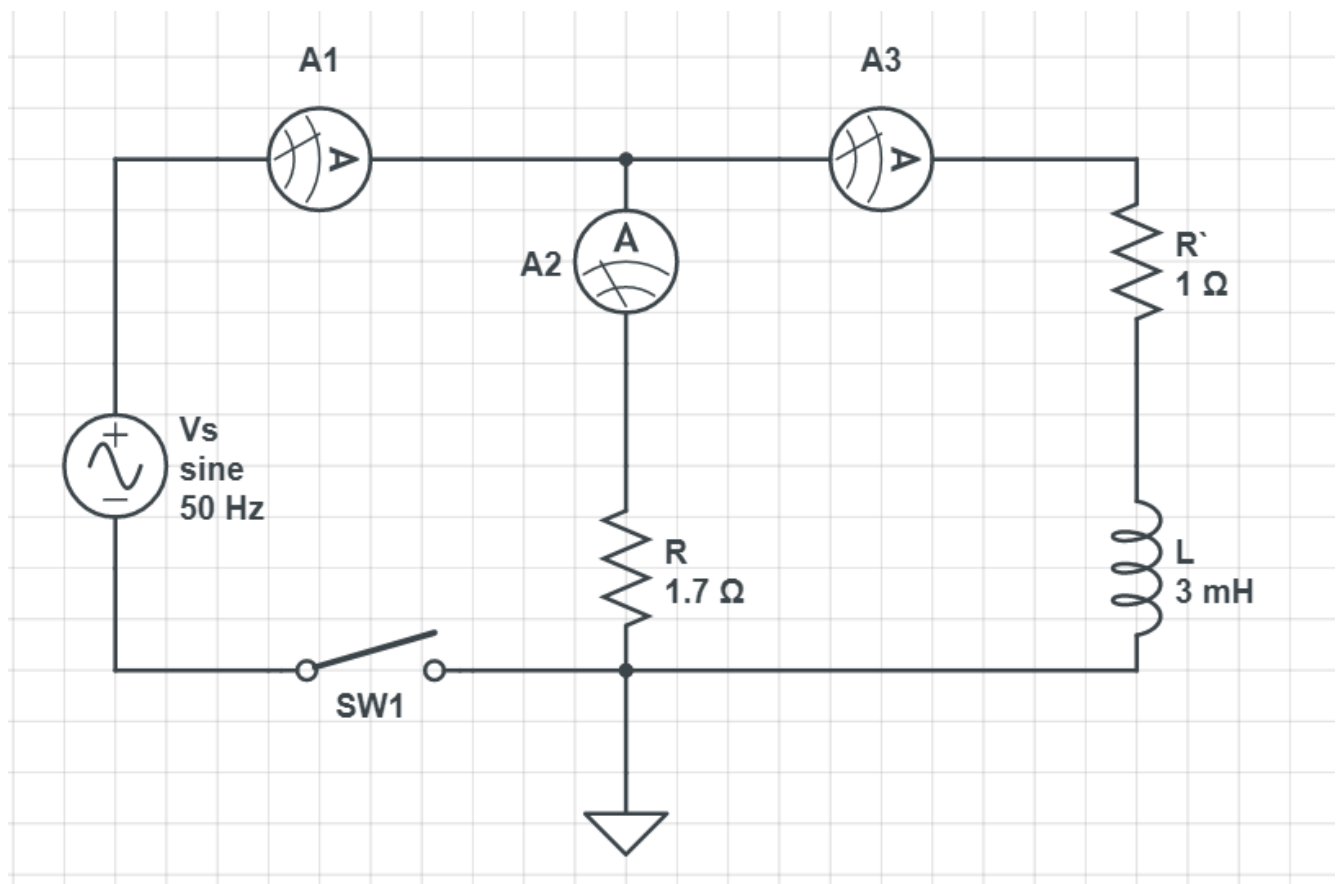


Figure 2: Circuit Diagram for Three Ammeter Method when $R = 1.7 \Omega$

Sayan Mondal Abantika Saha Sayan Das Raj Saha Debnata Pal Sohini Bhattacharya Anirban Maiti
 K.Dhennaj Reddy Subham Gupta Tuhin Karmak Souradepta Pal Koustav Sanyal D. Senapati Aman Kumar Jyotirmay Samanta

Experimental Results:

Table 1: Three-Voltmeter Method

Sl. No.	R (ohm)	V1 (Volt)	V2 (Volt)	V3 (Volt)	Power (Watt)	Power factor(pf)	Mean	
							Power	Power Factor(pf)
1.	1.7	20	11.8690	9.6097	48.9133	0.7277	Mean P = 44.5551 W	Mean pf = 0.7278
2.	1.8	20	12.1853	9.3020	45.8309	0.7278		
3.	1.9	20	12.4618	9.0124	43.0211	0.7278		
4.	2.0	20	12.7202	8.7393	40.4553	0.7278		

Table 2: Three-Ammeter Method

Sl. No	R (ohm)	I ₁ (A)	I ₂ (A)	I ₃ (A)	Power (Watt)	Power factor(pf)	Mean	
							Power	Power Factor(pf)
1.	1.7	24.4845	11.7647	14.5551	211.8468	0.7277	Mean P = 211.8448 W	Mean pf = 0.7277
2.	1.8	23.8891	11.1110	14.5551	211.8454	0.7278		
3.	1.9	23.3591	10.5263	14.5551	211.8493	0.7277		
4.	2.0	20.5925	10.0000	14.5551	211.8448	0.7277		

Sayan Mondal *Abantika Saha* *Sayan Das* *Devi Saha* *Devi Saha* *Sohini Bhattacharya* *Amirbanu Moi*
K.Dhanya Reddy *Sathish Gupta* *Tushin Karak* *Souradepta Pal* *Houstar Sanyal* *D. Senapati* *Aman Kumar* *Jyoti Sanyal*

Calculations:

Three-Voltmeter Method:

For $R = 1.7 \Omega$

Here, $V_1 = 20V \angle 0^\circ$

So, Load = $1 + j [2\pi \cdot 50 \cdot 0.003]$

$$\Rightarrow \text{Load} = 1 + j(0.9424)$$

$$Z = (1 + 1.7) + j(0.9424)$$

$$\Rightarrow Z = 2.7 + 0.9424j$$

$$\Rightarrow Z = 2.8597 \angle 19.24^\circ$$

According to KVL,

$$V_1 = I_{\text{total}} [R + \text{Load}]$$

$$\text{So, } I_{\text{total}} = 20 / (2.7 + 0.9424j)$$

$$\Rightarrow I_{\text{total}} = (6.6029 - 2.3046j) \text{ A}$$

$$V_2 = I_{\text{total}} * R$$

$$= (6.6029 - 2.3046j) * 1.7$$

$$\text{So, } V_2 = 11.2249 - 3.9178j \text{ V}$$

$$\text{or, } V_2 = 11.8890 \angle -19.24^\circ \text{ V}$$

$$V_3 = I_{\text{total}} * \text{Load}$$

$$= (6.6029 - 2.3046j) * (1 + 0.9424j)$$

$$V_3 = (8.7747 + 3.9179j) \text{ V}$$

$$\text{or, } V_3 = 9.6097 \angle 24.06^\circ \text{ V}$$

$$\text{So, Power } P = (V_1^2 - V_2^2 - V_3^2) / 2R$$


$$\Rightarrow P = (166.3053) / (2 * 1.7) \text{ W}$$

$$\Rightarrow P = 48.9133 \text{ W}$$

$$\cos \Phi = (V_1^2 - V_2^2 - V_3^2) / 2(V_2 * V_3)$$

$$\Rightarrow \cos \Phi = 166.3053 / (2 * 11.8890 * 9.6097)$$

$$\Rightarrow \cos \Phi = 0.7277$$

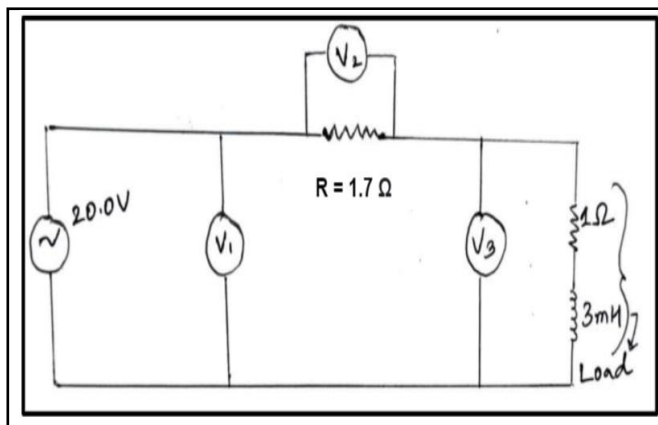

Sayan Mondal Abantika Saha Sayan Das Raj Saha Tanu Pal Sohini Bhattacharya Anirban Maiti
K.Dhanyashree Subhankar Gupta Tuhin Karmak Souvadepta Pal Koustav Sanyal D Senapati Aman Kumar Jyotirmay Samanta

For $R = 1.8 \Omega$

Here, $V_1 = 20V \angle 0^\circ$

So, Load = $1 + j [2\pi \cdot 50 \cdot 0.003]$

$$\Rightarrow \text{Load} = 1 + j(0.9424)$$

$$Z = (1 + 1.8) + j(0.9424)$$


$$\Rightarrow Z = 2.8 + 0.9424j$$

According to KVL,

$$V_1 = I_{\text{total}} [R + \text{Load}]$$

$$\text{So, } I_{\text{total}} = 20 / (2.8 + 0.9424j)$$
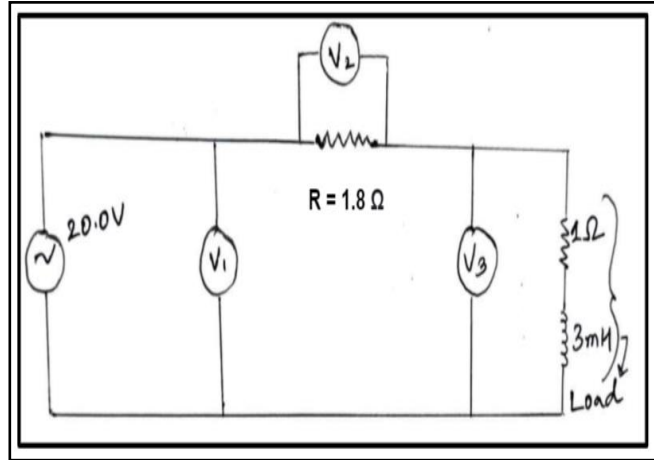
$$\Rightarrow I_{\text{total}} = (6.4160 - 2.1594j) \text{ A}$$



$$V_2 = I_{\text{total}} * R$$

$$= (6.4160 - 2.1594j) * 1.8$$

$$\text{So, } V_2 = 11.5488 - 3.8869j \text{ V}$$

$$\text{or, } V_2 = 12.1853 \angle -18.60^\circ \text{ V}$$

$$V_3 = I_{\text{total}} * \text{Load}$$

$$= (6.4160 - 2.1594j) * (1 + 0.9424j)$$

$$V_3 = (8.4510 + 3.8870j) \text{ V}$$

$$\text{or, } V_3 = 9.3020 \angle 24.69^\circ \text{ V}$$

$$\text{So, Power } P = (V_1^2 - V_2^2 - V_3^2) / 2R$$

$$\Rightarrow P = (164.9912) / (2 * 1.8) \text{ W}$$

$$\Rightarrow P = 45.8309 \text{ W}$$

$$\cos \Phi = (V_1^2 - V_2^2 - V_3^2) / 2(V_2 * V_3)$$

$$\Rightarrow \cos \Phi = 164.9912 / (2 * 12.1853 * 9.3020)$$

$$\Rightarrow \cos \Phi = 0.7278$$

Sayan Mondal Abantika Saha Sayan Das Raj Saha Tanu Pal Sohini Bhattacharya Anirban Maiti
K.Dhanya Reddy Subham Gupta Tuhin Kanak Souradepta Pal Koustav Sanjay D Senapati Aman Kumar Jyotirmay Samanta

For $R = 1.9 \Omega$

Here, $V_1 = 20V \angle 0^\circ$

So, Load = $1 + j [2\pi \cdot 50 \cdot 0.003]$

$$\Rightarrow \text{Load} = 1 + j(0.9424)$$

$$Z = (1 + 1.9) + j(0.9424)$$


$$\Rightarrow Z = 2.9 + 0.9424j$$

According to KVL,

$$V_1 = I_{\text{total}} [R + \text{Load}]$$

$$\text{So, } I_{\text{total}} = 20 \angle 0^\circ / (2.9 + 0.9424j)$$
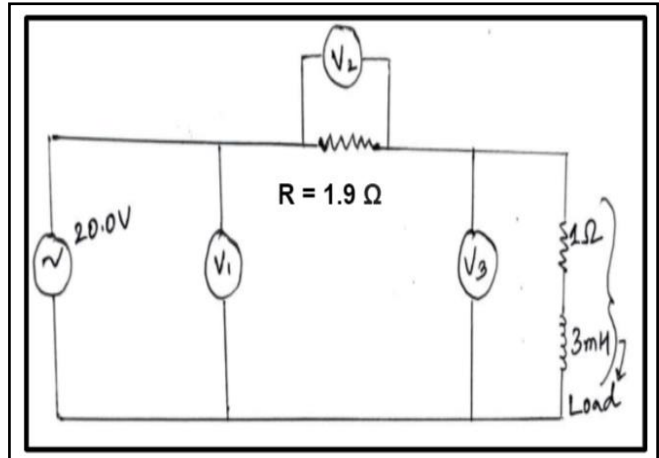
$$\Rightarrow I_{\text{total}} = (6.2378 - 2.0270j) \text{ A}$$



$$V_2 = I_{\text{total}} * R$$

$$= (6.2378 - 2.0270j) * 1.9$$

$$\text{So, } V_2 = 11.8518 - 3.8513j \text{ V}$$

$$\text{or, } V_2 = 12.4618 \angle -18.00^\circ \text{ V}$$

$$V_3 = I_{\text{total}} * \text{Load}$$

$$= (6.2378 - 2.0270j) * (1 + 0.9424j)$$

$$V_3 = (8.1480 + 3.8515j) \text{ V}$$

$$\text{or, } V_3 = 9.0124 \angle 24.29^\circ \text{ V}$$

$$\text{So, Power } P = (V_1^2 - V_2^2 - V_3^2) / 2R$$

$$\Rightarrow P = (163.4801) / (2 * 1.9) \text{ W}$$

$$\Rightarrow P = 43.0211 \text{ W}$$

$$\cos \Phi = (V_1^2 - V_2^2 - V_3^2) / 2(V_2 * V_3)$$

$$\Rightarrow \cos \Phi = 163.4801 / (2 * 12.4618 * 9.0124)$$

$$\Rightarrow \cos \Phi = 0.7278$$

Sayan Mondal Abantika Saha Sayan Das Raj Saha Tanula Pal Sohini Bhattacharya Anirban Maiti
K.Dhanya Reddy Subhomi Gupta Tuhin Kanak Souradepta Pal Koustav Sanyal D Senapati Aman Kumar Jyotirmay Samanta

For $R = 2.0 \Omega$

Here, $V_1 = 20V \angle 0^\circ$

So, Load = $1 + j[2\pi \cdot 50 \cdot 0.003]$

$$\Rightarrow \text{Load} = 1 + j(0.9424)$$

$$Z = (1 + 2.0) + j(0.9424)$$


$$\Rightarrow Z = 3.0 + 0.9424j$$

According to KVL,

$$V_1 = I_{\text{total}} [R + \text{Load}]$$

$$\text{So, } I_{\text{total}} = 20 \angle 0^\circ / (3.0 + 0.9424j)$$
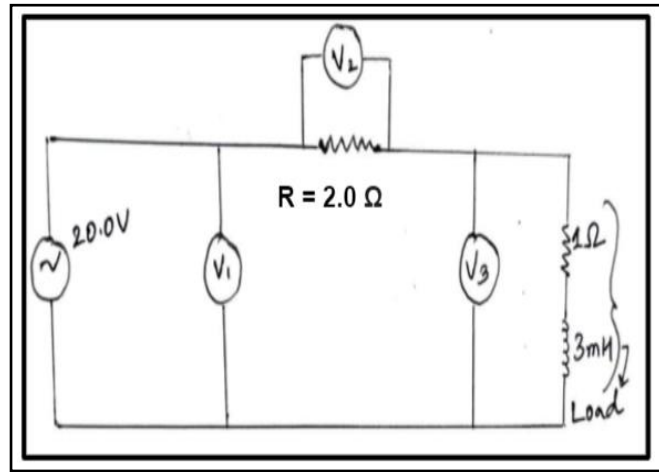
$$\Rightarrow I_{\text{total}} = (6.0678 - 1.9061j) \text{ A}$$



$$V_2 = I_{\text{total}} * R$$

$$= (6.0678 - 1.9061j) * 2.0$$

$$\text{So, } V_2 = 12.1356 - 3.8122j \text{ V}$$

$$\text{or, } V_2 = 12.7202 \angle -17.4392^\circ \text{ V}$$

$$V_3 = I_{\text{total}} * \text{Load}$$

$$= (6.0678 - 1.9061j) * (1 + 0.9424j)$$

$$V_3 = (7.8641 + 3.8121j) \text{ V}$$

$$\text{or, } V_3 = 8.7393 \angle 25.86^\circ \text{ V}$$

$$\text{So, Power } P = (V_1^2 - V_2^2 - V_3^2) / 2R$$

$$\Rightarrow P = (161.8211) / (2 * 2.0) \text{ W}$$

$$\Rightarrow P = 40.4553 \text{ W}$$

$$\cos \Phi = (V_1^2 - V_2^2 - V_3^2) / 2(V_2 * V_3)$$

$$\Rightarrow \cos \Phi = 161.8211 / (2 * 12.7202 * 8.7393)$$

$$\Rightarrow \cos \Phi = 0.7278$$

Sayan Mondal *Abantika Saha* *Sayan Das* *Devi Saha* *Devi Saha* *Sohini Bhattacharya* *Amirbanu Moir*
K.D. Heng Raj *Sobhan Gupta* *Tuhin Karak* *Souradepta Pal* *Koustav Sanyal* *D. Senapati* *Aman Kumar* *Jyotirmay Samanta*

Three-Ammeter Method:

$$\text{For } R = 1.7 \, \Omega$$

$$I_2 = 20/1.7 \, \text{A}$$

$$I_2 = 11.7647 \angle 0^\circ$$

$$I_3 = 20/(1+j\omega L)$$

$$= 20 / (1+j(2\pi \cdot 50 \cdot 0.003))$$

$$I_3 = (10.5925 - 9.8924j) \, \text{A}$$

$$|I_3| = 14.5551 \angle -43.30^\circ$$

According to KCL,

$$I_1 = I_2 + I_3$$

$$\Rightarrow I_1 = (22.3572 - 9.9824j) \, \text{A}$$


$$\text{So, } I_1 = 24.4845 \angle -24.06^\circ \, \text{A}$$

$$\text{Therefore, Power, } P = (I_1^2 - I_2^2 - I_3^2) R/2$$

$$\Rightarrow P = 211.8468 \, \text{W}$$

$$\cos \Phi = (I_1^2 - I_2^2 - I_3^2)/2(I_2 \cdot I_3)$$

$$\Rightarrow \cos \Phi = 0.7277$$

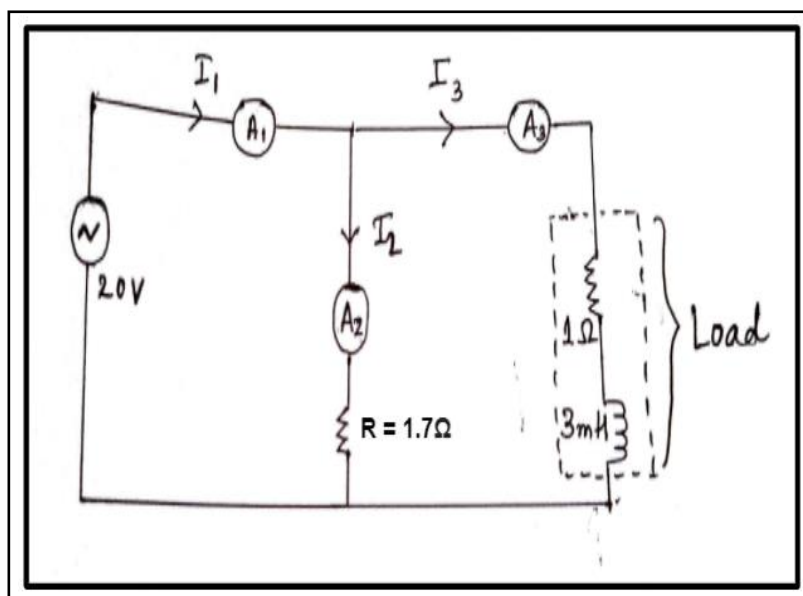

Sayan Mondal Abantika Saha Sayan Das Raj Saha Tanuka Pal Sohini Bhattacharya Anirban Maiti
K.Dharmajyoti Sathorn Gupta Tukin Karak Souradepta Pal Koustav Sanyal DSenapati Aman Kumar Jyotirmay Samanta

For $R = 1.8 \Omega$

$$I_2 = 20/1.8 \text{ A}$$

$$I_2 = 11.111 \angle 0^\circ \text{ A}$$

$$I_3 = 20/(1+j\omega L)$$

$$= 20 / (1+j(2\pi \cdot 50 \cdot 0.003))$$

$$I_3 = (10.5925 - 9.8924j) \text{ A}$$

$$|I_3| = 14.5551 \angle -43.30^\circ$$

According to KCL,

$$I_1 = I_2 + I_3$$

$$\Rightarrow I_1 = (21.7035 - 9.9824j) \text{ A}$$


$$\text{So, } I_1 = 23.8891 \angle -24.6997^\circ \text{ A}$$

$$\text{Therefore, Power, } P = (I_1^2 - I_2^2 - I_3^2) R/2$$

$$\Rightarrow P = 211.8454 \text{ W}$$

$$\cos \Phi = (I_1^2 - I_2^2 - I_3^2)/2(I_2 \cdot I_3)$$

$$\Rightarrow \cos \Phi = 0.7278$$

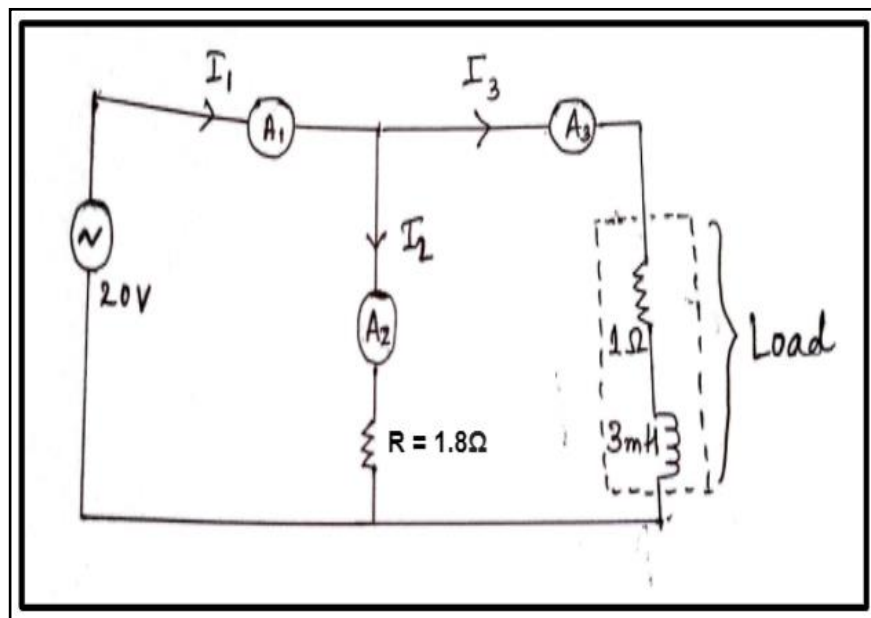

Sayan Mondal Abantika Saha Sayan Das Raj Saha Tanuka Pal Sohini Bhattacharya Anirban Maiti
K.Dhennaj Reddy Subhom Gupta Tukin Karak Souradepta Pal Koustav Sanyal DSenapati Aman Kumar Jyotirmay Samanta

For $R = 1.9 \Omega$

$$I_2 = 20/1.9 \text{ A}$$

$$I_2 = 10.5263 \angle 0^\circ \text{ A}$$

$$I_3 = 20/(1+j\omega L)$$

$$= 20 / (1+j(2\pi \cdot 50 \cdot 0.003))$$

$$I_3 = (10.5925 - 9.8924j) \text{ A}$$

$$|I_3| = 14.5551 \angle -43.30^\circ \text{ A}$$

According to KCL,

$$I_1 = I_2 + I_3$$

$$\Rightarrow I_1 = (21.1188 - 9.9824j) \text{ A}$$


$$\text{So, } I_1 = 23.3591 \angle -25.30^\circ \text{ A}$$

$$\text{Therefore, Power, } P = (I_1^2 - I_2^2 - I_3^2) R/2$$

$$\Rightarrow P = 211.8439 \text{ W}$$

$$\cos \Phi = (I_1^2 - I_2^2 - I_3^2)/2(I_2 \cdot I_3)$$

$$\Rightarrow \cos \Phi = 0.7277$$

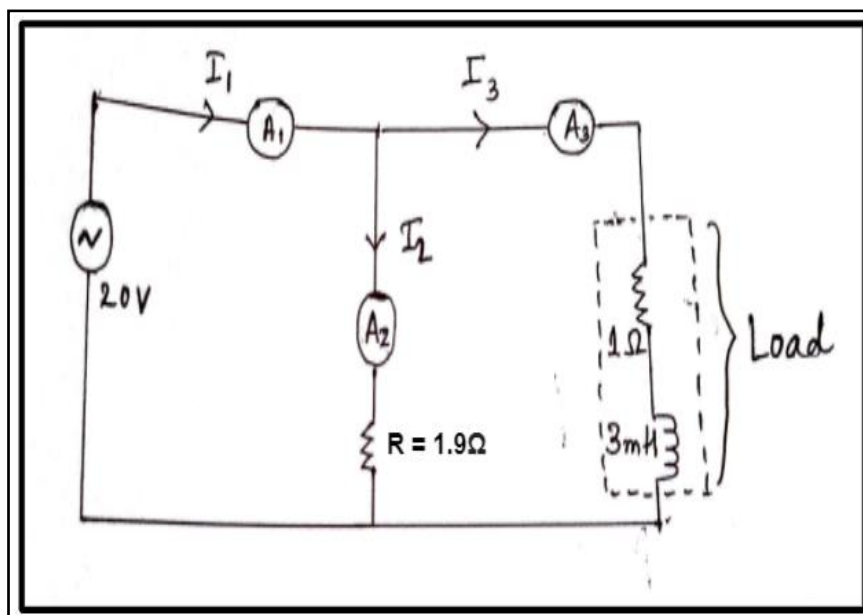

Sayan Mondal Abantika Saha Sayan Das Raj Saha Tanula Pal Sohini Bhattacharya Anirban Maiti
K.Dhennaj Reddy Subham Gupta Tukin Karak Souradepta Pal Koustav Sanyal D Senapati Aman Kumar Jyotirmay Samanta

For $R = 2.0 \Omega$

$$I_2 = 20/2.0 \text{ A}$$

$$I_2 = 10 \angle 0^\circ \text{ A}$$

$$I_3 = 20/(1+j\omega L)$$

$$= 20 / (1+j(2\pi \cdot 50 \cdot 0.003))$$

$$I_3 = (10.5925 - 9.8924j) \text{ A}$$

$$|I_3| = 14.5551 \angle -43.30^\circ$$

According to KCL,

$$I_1 = I_2 + I_3$$

$$\Rightarrow I_1 = (20.5925 - 9.9824j) \text{ A}$$


$$\text{So, } I_1 = 22.8844 \angle -25.86^\circ \text{ A}$$

$$\text{Therefore, Power, } P = (I_1^2 - I_2^2 - I_3^2) R/2$$

$$\Rightarrow P = 211.8448 \text{ W}$$

$$\cos \Phi = (I_1^2 - I_2^2 - I_3^2)/2(I_2 \cdot I_3)$$

$$\Rightarrow \cos \Phi = 0.7277$$

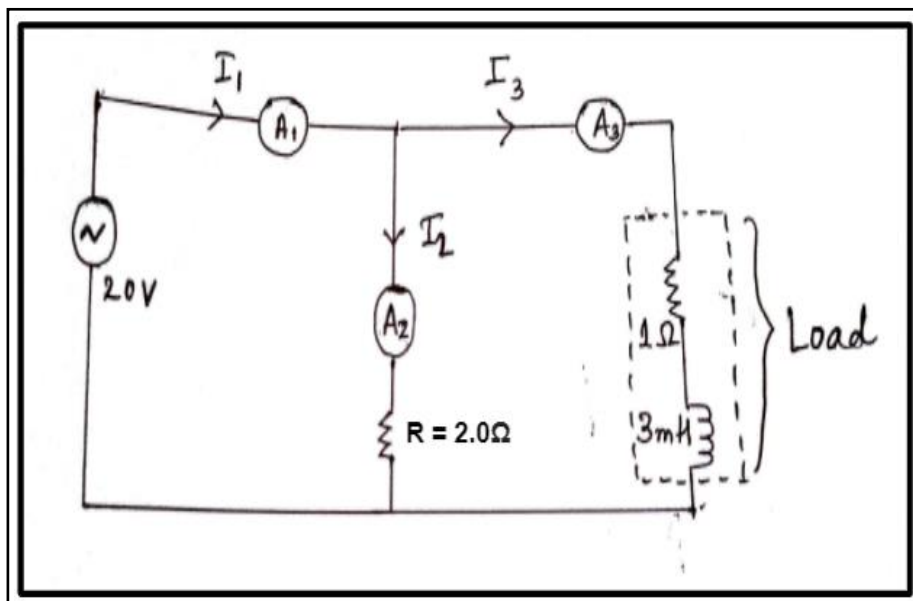

Sayan Mondal Abantika Saha Sayan Das Raj Saha Tanuka Pal Sohini Bhattacharya Anirban Maiti
K.Dhennaj Reddy Subham Gupta Tukin Karak Souradepta Pal Koustav Sanyal DSenapati Aman Kumar Jyotirmay Samanta

Error Analysis:

- Here Percentage (%) Error = $\frac{(P_{\text{calculated}} - \text{Wattmeter Reading})}{\text{Wattmeter Reading}}$
- $R_{\text{load}} = 1\Omega$, $|I_3| = 14.5551 \text{ A}$ (as evident from the calculations above)

1.) Three-Voltmeter Method:

Sl. No.	R(Ω)	I (A)	$ I $ (Magnitude of Current)	Wattmeter Reading (= $ I ^2 R_{\text{load}}$)	P _{Calculated} (W)	P _{calculated} - Wattmeter Reading	% Error
1.	1.7	6.6029-2.3046i	6.993530551	48.90946957	48.9133	0.00383043	7.83E-05
2.	1.8	6.4160-2.1594i	6.769642853	45.82806436	45.8309	0.00283564	6.19E-05
3.	1.9	6.2378-2.027i	6.558877788	43.01887784	43.0211	0.00222216	5.17E-05
4.	2	6.0678-1.96061i	6.376691024	40.66218841	40.4553	-0.206888412	-0.00508798

2.) Three-Ammeter Method:

Sl. No.	R (Ω)	P _{calculated} (W)	Wattmeter Reading (= $(I_3 ^2)R_{\text{load}}$) (W)	P _{calculated} - Wattmeter Reading	% Error
1.	1.7	211.8468	211.850936	0.00413601	1.95E-05
2.	1.8	211.8454	211.850936	0.00553601	2.61E-05
3.	1.9	211.8493	211.850936	0.00163601	7.72E-06
4.	2	211.8448	211.850936	0.00613601	2.90E-05

Sayan Mondal Abantika Saha Sayan Das Raj Saha Tanula Pal Sohini Bhattacharya Anirban Maiti
 K.Dhanya Reddy Subhomi Gupta Tuhin Kanak Souradepta Pal Houshav Samyol D Senapati Aman Kumar Jyotirmay Samanta

Result:

1) Three-Voltmeter Method:

Mean Power (P_{avg}) = 44.5551 W

Mean Power Factor ($\cos \Phi$) $_{avg}$ = 0.7278

2) Three-Ammeter Method:

Mean Power (P_{avg}) = 211.8448 W

Mean Power Factor ($\cos \Phi$) $_{avg}$ = 0.7277

Conclusion:

1) **KCL and KVL are used** to compute the readings of the three voltmeters and three ammeters in the respective methods. Furthermore, power consumed by the load and the power factor of the circuit is calculated by using the computed values of voltages and currents in the working formulae.

2) The calculated values are observed to be in the expected range as seen in the simulations **performed in Simulink with the help of Simscape electrical toolbox.**

3) It is observed that **the power and power factor in an A.C.** circuit can be measured by using **three single-phase voltmeters as well as ammeters successfully, instead of a wattmeter.**

Sayan Mondal *Abantika Saha* *Sayan Das* *Devi Saha* *Devi Saha* *Sohini Bhattacharya* *Anirban Maiti*
K.Dhanya Reddy *Sathish Gupta* *Tuhin Karmak* *Souradeepa Pal* *Koustav Sanyal* *D. Senapati* *Aman Kumar* *Jyoti Sanyal*

Simulation

All the graphs are obtained by running the simulations for 0.05s in Simulink.

Three Voltmeter Method:

For $R = 1.7 \text{ ohm}$

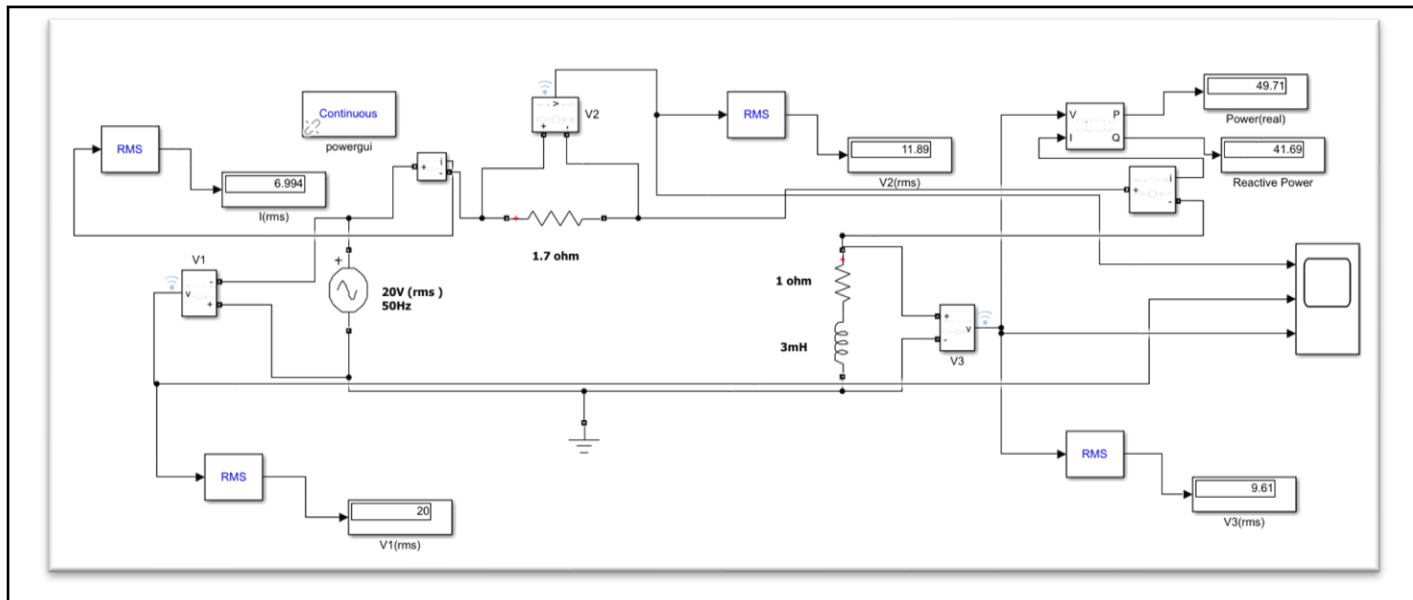


Figure: circuit at 1.7 ohms after running the simulation for 0.05s

Voltage waveforms of V_1 , V_2 and V_3 for 0.05 seconds:

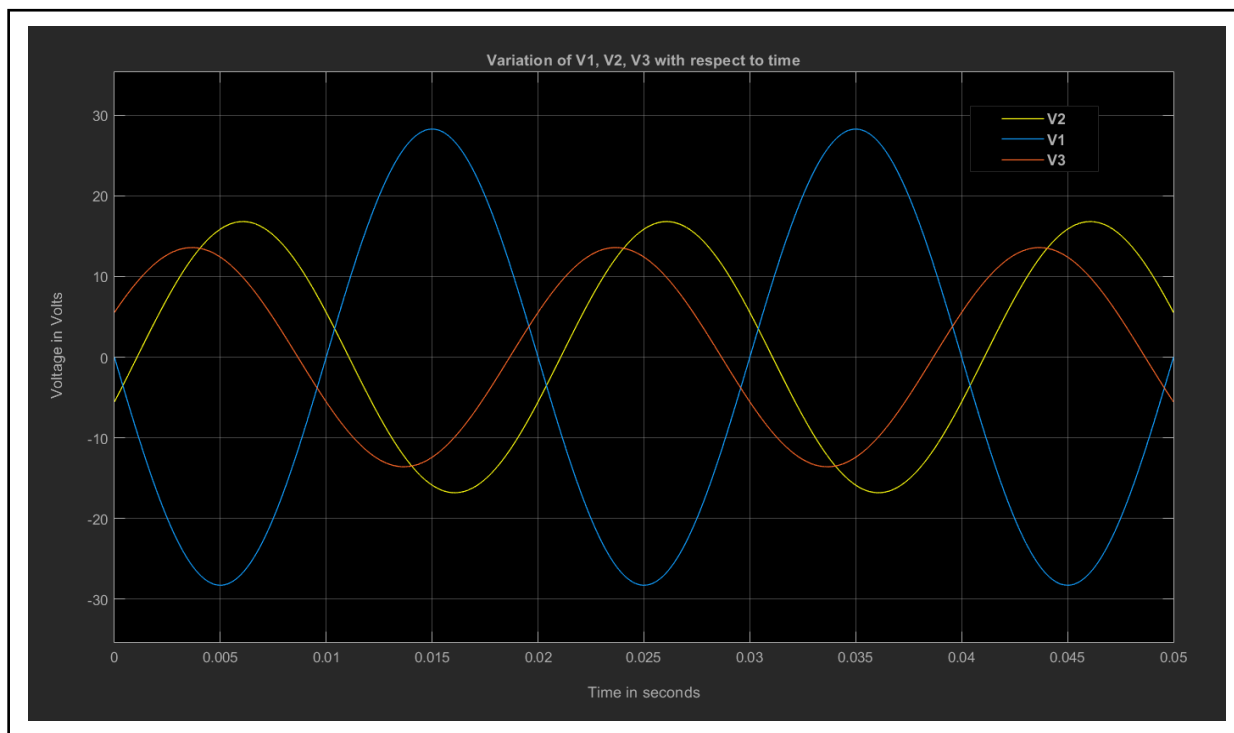


Figure 3: Simulation curves of voltages V_1 , V_2 , V_3

Sayan Mondal Abantika Saha Sayan Das Raj Saha Tanuka Pal Sohini Bhattacharya Anirban Maiti
K.Dhennaj Reddy Subhom Gupta Tuhin Kanak Souradepta Pal Houshav Samal D. Senapati Aman Kumar Jyotirmay Samanta

Three Ammeter Method:

For $R = 1.7 \text{ ohms}$

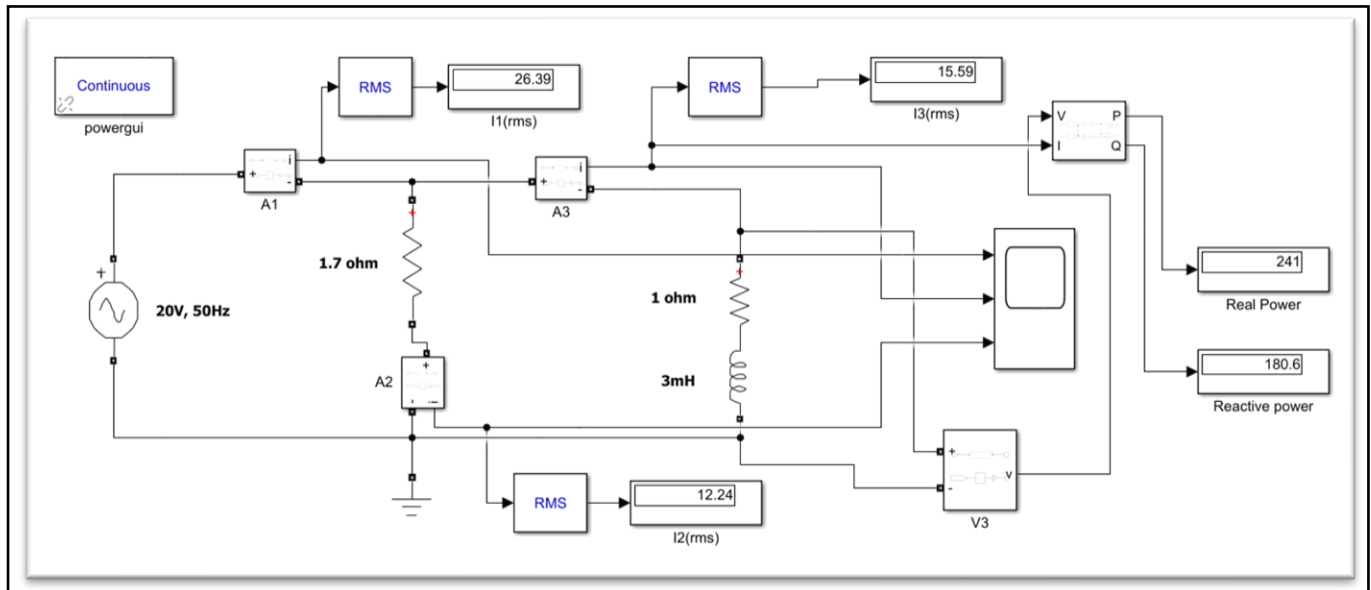


Figure: circuit at 1.7 ohms after running the simulation for 0.05s

Current waveforms of I_1 , I_2 and I_3 for 0.05 seconds:

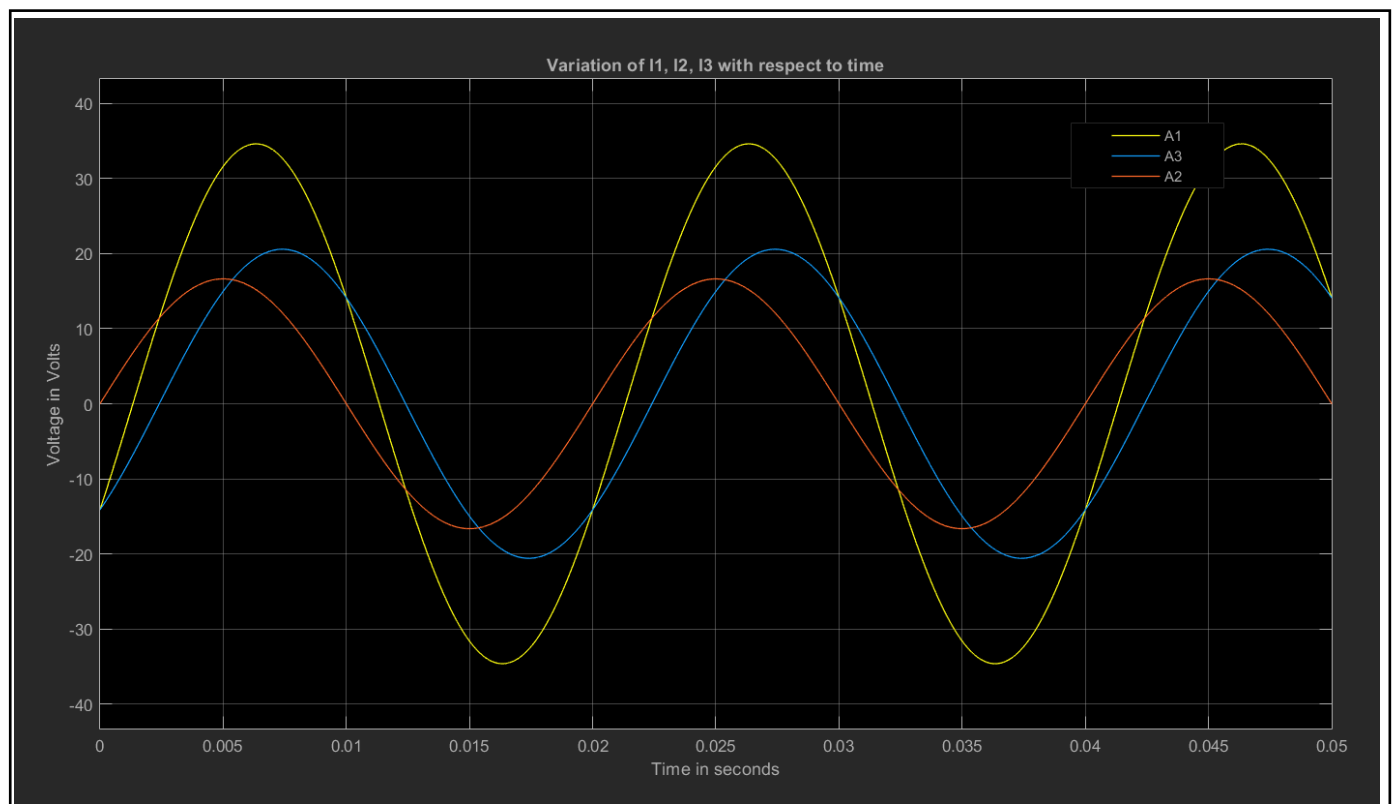


Figure 4: Simulation curve of currents, Here A1,A2, A3 refers to the instantaneous current reading of the ammeter

Sayan Mondal, Abantika Saha, Sayan Das, Raj Saha, Tanula Pal, Sohini Bhattacharya, Anirban Moi,
 K.Dhanya Reddy, Subhomi Gupta, Tuhin Kanak, Souradepta Pal, Koustav Sanyal, D. Senapati, Aman Kumar, Jyoti Sanyal