



National Institute Of Technology Durgapur

ELECTRICAL MEASUREMENT LABORATORY(EES-351)

Group V

Experiment 3

Measurement of earth resistance.

18th June, 2021

Members (63-77)

- | | |
|--------------------------------|--------------------------|
| ✓ Sayan Mondal (63) | ✓ Subham Gupta (71) |
| ✓ Abantika Saha (64) | ✓ Tuhin Karak (72) |
| ✓ Sayan Das (65) | ✓ Souradeepa Pal (73) |
| ✓ Raj Suyash Ranjan (66) | ✓ Koustav Sanyal (74) |
| ✓ Vemula Rahul (67) | ✓ Diksha Senapati (75) |
| ✓ Sohini Bhattacharya (68) | ✓ Aman Kumar (76) |
| ✓ Anirban Moi (69) | ✓ Yogeswar Sarnakar (77) |
| ✓ Kalakonda Dheeraj Reddy (70) | |

Aim: Measurement of earth resistance.

Objective: Measurement of earth resistance by three electrode method.

Apparatus Required:


Serial Number	Instrument Name	Specifications	Quantity	Maker's Name
1	Earth resistance testing kit	-	1	Nanin Bokun Instrument Equipment Co. LTD.
1 a.	Earth tester (Model:AR-4105A)	$2\Omega-0.5 \sim 1.99\Omega$ $20\Omega-2 \sim 19.99\Omega$ $200\Omega-20 \sim 199.9\Omega$	1	Nanin Bokun Instrument Equipment Co. LTD.
1 b.	Connecting leads (with crocodile clips)	Red, yellow, green colour codes	3	Nanin Bokun Instrument Equipment Co. LTD.
1 c.	Auxiliary earth spikes	-	2	Nanin Bokun Instrument Equipment Co. LTD.
2	Earth electrode	-	2	Nanin Bokun Instrument Equipment Co. LTD.
3	Metering tape	30 meters	1	FMI LTD.

Sayan Mondal Abantika Saha Sayan Das Raj Suri Venula Rabi Shonini Bhattacharya Amritan Maiti
K. Dhanya Reddy Sathyanayagam Tushin Kanak Souradeepa Pal Houston Sanyal D. Senapati Aman Kumar Jyoti Senapati

Theory:

This instrument makes earth resistance measurement with fall-of-potential method, which is a method to obtain earth resistance value R_x by applying AC constant current I between the measurement object E (earth electrode) and C (current electrode), and finding out the potential difference V between E and P (potential electrode).


$$R_x = \frac{V}{I}$$

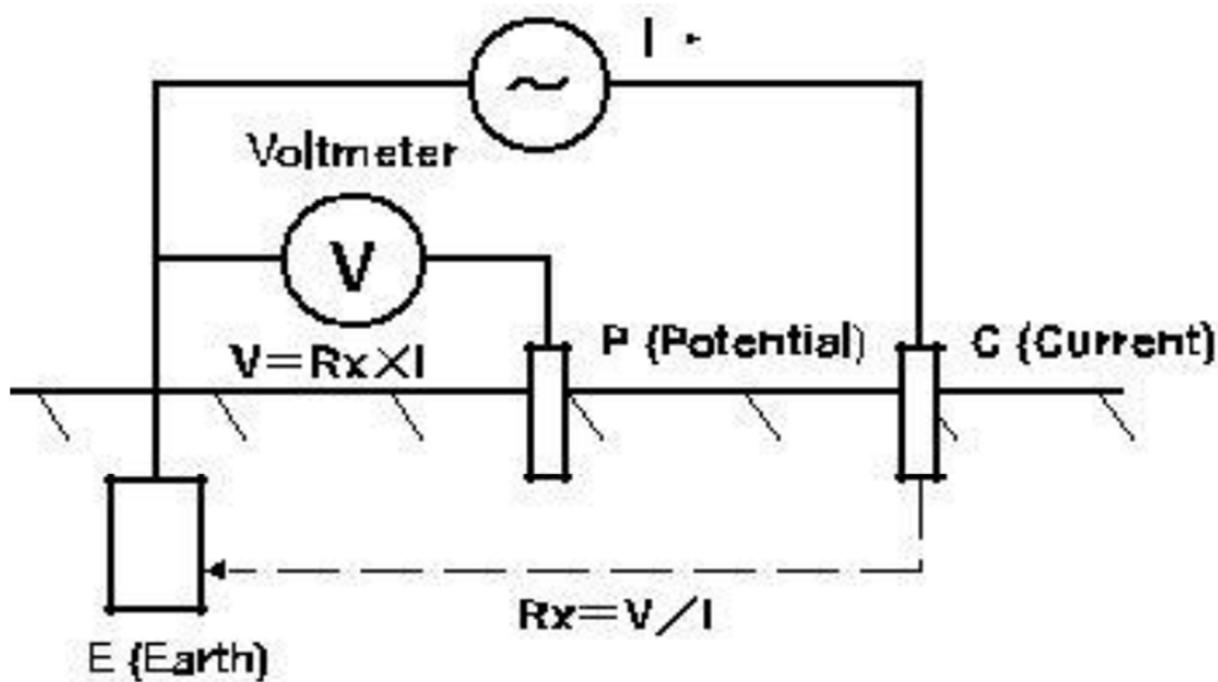

Sayan Mondal Abantika Saha Sayan Das Sajit Saha Debnath Ray Sohini Bhattacharya Amirban Maitra

K.Dhanya Reddy Suttoram Gupta Tuhin Karak Suvadeepa Pal Houshav Sanyal D.Senapati Aman Kumar Jyoti Basu

Original Circuit:

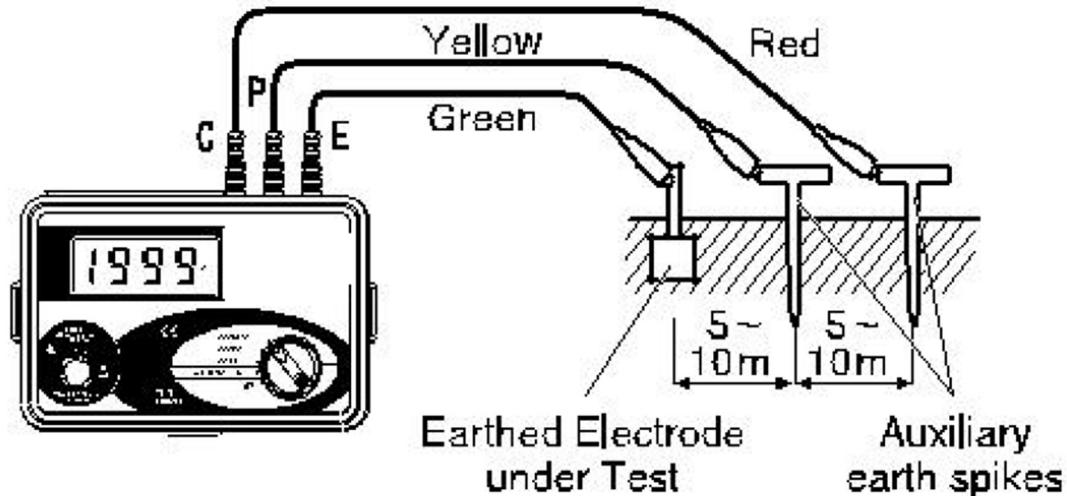


Observation Table:

Serial Number	Distance from Earth Electrode (in meters)	Earth Resistance (Ω)
1	0.9	0.8
2	1.9	1.0
3	2.9	1.58
4	3.9	1.59
5	4.9	1.56
6	5.9	1.61
7	6.9	10
8	7.9	15
9	8.9	19
10	9.9	26

Sayan Mandal Abantika Saha Sayan Das Rajeev Saha Denuka Pal Sohini Bhattacharya Amirban Maitra
 K. Dhanya Radhika Sathorn Gupta Tuhin Karak Suvradeepa Pal Houston Sanyal D. Senapati Aman Kumar Jyotishree Samanta

Graph:

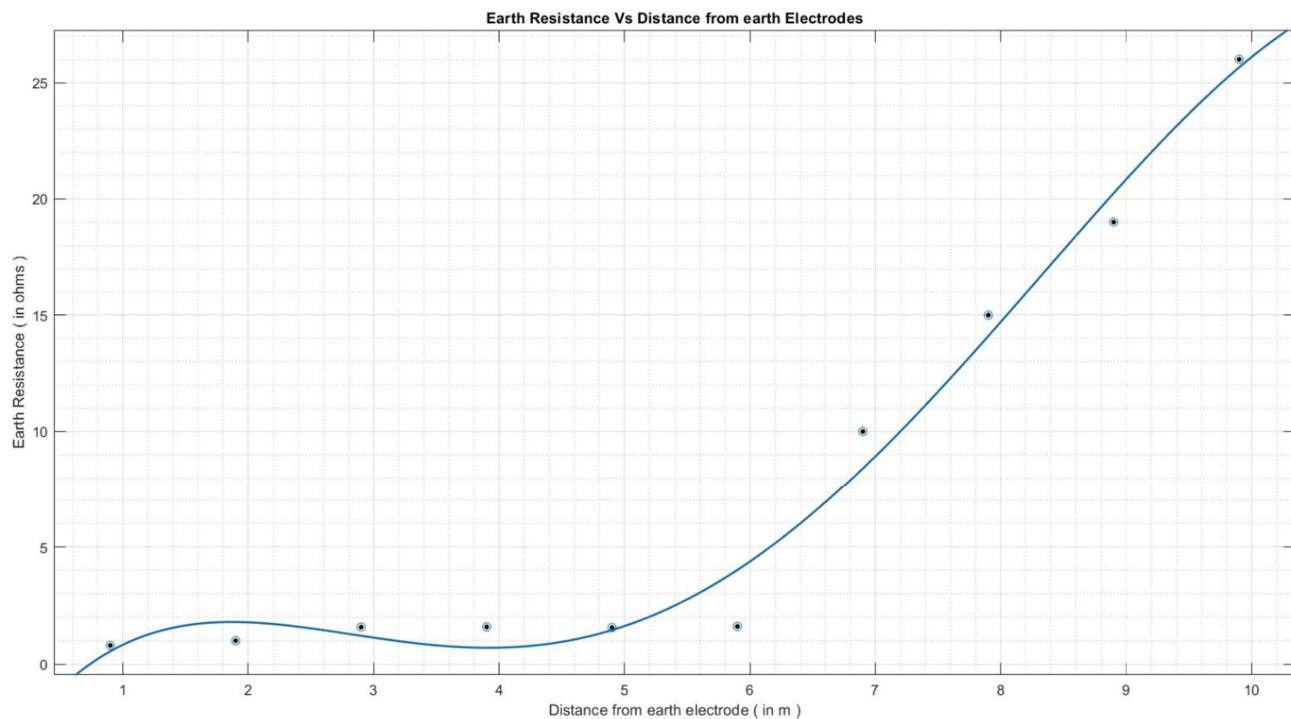

Calculations:

From the graph we find the value of earth resistance remain almost constant from 2.9m to 5.9m. Thus, earth resistance offered by the earth electrode is approximately equal to 1.58Ω .

Sayan Mandal Abantika Saha Sayan Das Raj Sankar Venula Rahi Shohini Bhattacharya Amritan Maitra

X Dheray Reddy Subham Gupta Tushin Karak Souradeepa Pal Koustav Sanyal D Senapati Aman Kumar Jyotir Samanta

Conclusion:

- The measured earth resistance readings are better on a rainy day than a sunny day due to the moisture in the soil.
- The earth resistance value should not exceed 5 ohms in practice (according to Indian Electricity Earthing Standards).
- The measured earth resistance increases with the increase in distance from the earth electrode until it becomes constant. However, when we move closer to the current electrode, the value of earth resistance increases again. This is because the electric field lines are concentrated at the earth and current electrodes and become almost constant around the midway point between the two electrodes, provided that they are sufficiently far apart from each other and their effective resistance areas do not overlap.

Sayan Mondal Abantika Saha Sayan Das Rajeev Suri Venula Rabi Sohini Bhattacharya Amritan Maiti
K.Dhengra Ray Suttoram Gupta Tuhin Karak Saradeepa Pal Houston Sanyal D.Senapati Aman Kumar Jyoti Basu



National Institute Of Technology Durgapur

ELECTRICAL MEASUREMENT LABORATORY(EES-351)

Group V

Experiment 4

MEASUREMENT OF POWER USING CT & PT

18th June, 2021

Members (63-77)

- ✓ Sayan Mondal (63) ✓ Subham Gupta (71)
- ✓ Abantika Saha (64) ✓ Tuhin Karak (72)
- ✓ Sayan Das (65) ✓ Souradeepa Pal (73)
- ✓ Raj Suyash Ranjan (66) ✓ Koustav Sanyal (74)
- ✓ Vemula Rahul (67) ✓ Diksha Senapati (75)
- ✓ Sohini Bhattacharya (68) ✓ Aman Kumar (76)
- ✓ Anirban Moi (69) ✓ Yogeswar Sarnakar (77)
- ✓ Kalakonda Dheeraj Reddy (70)

Experiment No: 4

Measurement of Power Using CT & PT

Objective:

- To study the working of current transformer and potential transformer.
- To connect instrument transformer in electrical circuits for measurements of current, voltage and power.

Apparatus Used:

The following instruments are to be used for this experiment: -


Sl. No	Name of equipment's	Range
1	Current Transformer	30A / 5A
2	Potential Transformer	300V / 100V
3	M.I type Ammeter	Primary: (0 – 30A) Secondary: (0 – 5A)
4	M.I type Voltmeter	Primary: (0 – 230V) Secondary: (0 – 230V)
5	Dynamometer type Wattmeter	0 – 1.5kW
6	Loading arrangement	-

Sayan Mondal Abantika Saha Sayan Das Sai Sanket Debnula Rabbi Shohini Bhattacharya Amirbom Mol
 K.Dhingra Subham Gupta Tukin Karak Suvadipita Pal Koustav Sanyal D.Senapati Aman Kumar Shyamal Banerjee


Theory:

In dc circuits, large currents can be measured with the help of low range ammeters with appropriate shunts. For measuring high voltages, low range voltmeters are used in conjunctions with a high series resistance. Same methods cannot be used with ac circuits because of the presence if inductance and capacitance in the circuit. For this purpose, specially designed accurate ratio instrument transformers are used in conjunction with standard low range ac instruments. These instrument transformers are of two types: -

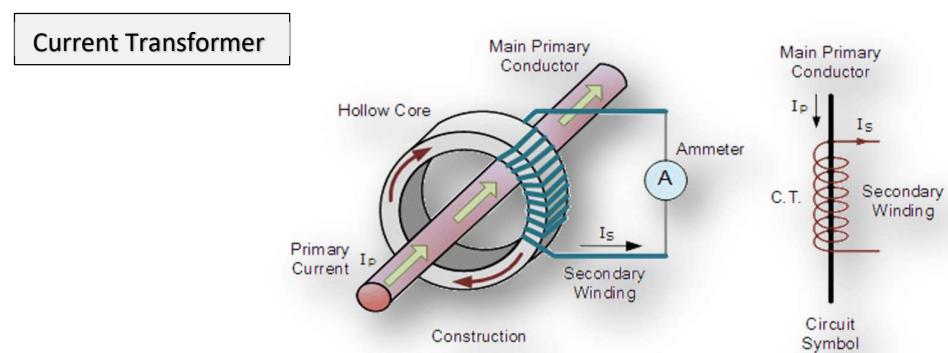- **Current Transformers** for measuring large alternating currents and,
- **Potential Transformers** for measuring high alternating voltages.



A Current Transformer (CT) is used to measure the current of another circuit. CTs are used worldwide to monitor high-voltage lines across national power grids. A CT is designed to produce an alternating current in its secondary winding that is proportional to the current that it is measuring in its primary. In doing so, the current transformer reduces a high voltage current to a lower value and therefore provides a safe way of monitoring electrical current flowing in an AC transmission line.

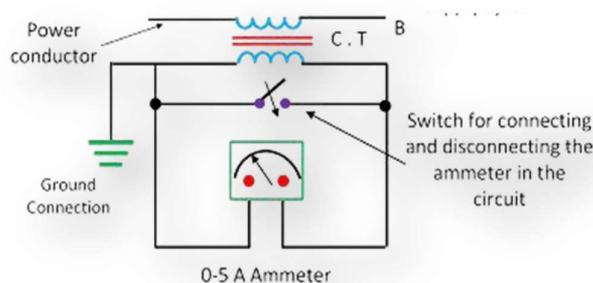


Current Transformer

Mayank Handal Abantika Saha Sayan Das *[Signatures]* Venkata Ravi Sekhoni Bhattacharya Amritben Mehta
K.Dhanya Reddy Sathoma Gupta Tuhin Karak Saradeepa Pal Houston Sengal D.Senapati Aman Kumar


The current transformer is basically a step-up transformer and obviously the current in the secondary winding will be less than that in the primary winding. Thus, a current transformer having primary to secondary voltage transformation ratio of 1:20 will have a current transformation ratio of 100:5 (or 20:1). Hence if we know the current transformation ratio (I_1/I_2) then line current is obtained by multiplying the ammeter reading i.e., I_2 by the ratio I_1/I_2 .

Potential Transformer

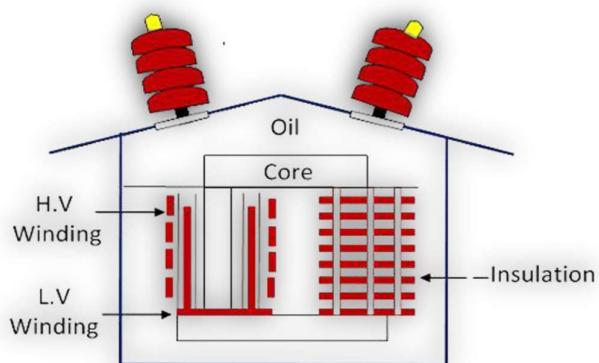

Single Phase Potential Transformer

A Potential Transformer (PT) on the other hand is a step-down transformer used along with a low range voltmeter for measuring high voltage. The primary is connected across the high voltage supply and the secondary to the voltmeter or potential coil of the wattmeter. Since, the voltmeter (or potential coil) impedance is very high, the secondary current is very small and the potential transformer (PT) behaves as an ordinary two winding transformer operating on no-load. Potential transformer (PT) secondary is commonly designed for an output of 110 Volts.

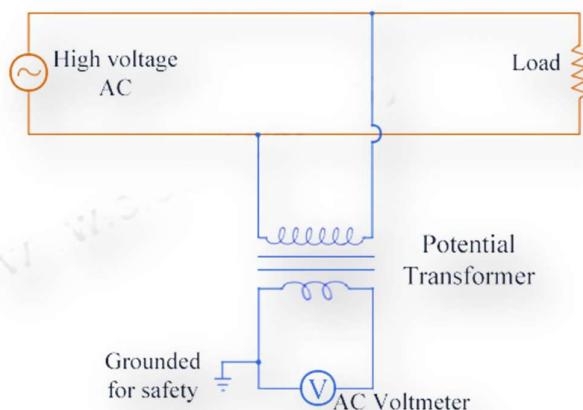


Sayan Mondal Abantika Saha Sayan Das Devenula Rahi Schini Bhattacharya Amritan Maiti


K. Dhanya Reddy Suhani Gupta Tuhin Karak Swaradeepa Pal Koustav Sengupta D. Senapati Aman Kumar

Since secondary load is either an instrument, a relay or a pilot lamp, the rating of PTs is 40W to 100W. For safety the secondary should be completely insulated from the high voltage primary and should be earthed.


Circuit Diagrams:

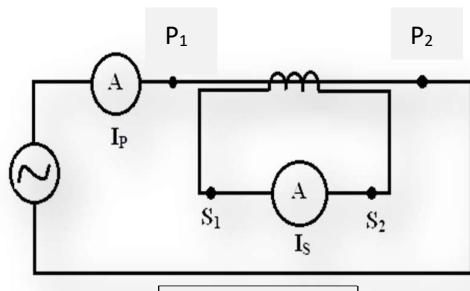

CT Calibration

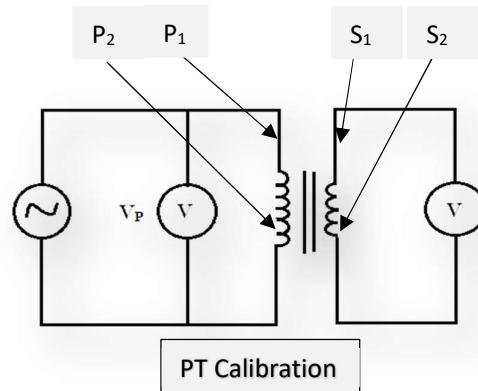

PT Calibration

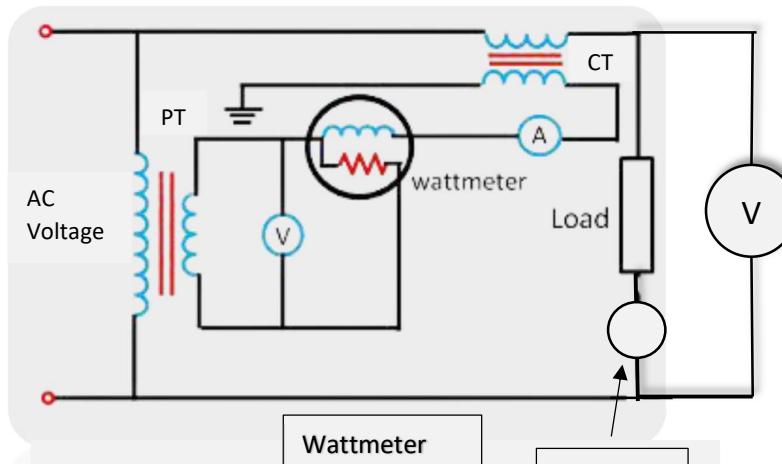

Wattmeter Connection

Ammeter

CT Calibration: - By this method, the current circulating in the secondary windings of a CT is calculated using an ammeter of suitable range and then keeping in view of the Nominal ratio and Transformation ratio of CT, the actual Line current I_s is calculated.

$$\text{Nominal Ratio (Turns Ratio)} = N = \frac{N_p}{N_s}$$

$$\text{Transformation Ratio} = R_{CT} = N + \frac{I_o}{I_s}$$

Therefore, $I_p = I_o + NI_s$, P is Primary, S is secondary and I_o is the summation of core loss current and magnetizing current on the primary section.

Sayan Mondal Abantika Saha Sayan Das *[Signature]* Venula Palu Shini Bhattacharya *[Signature]* Miriam Mol

K. Dhanya Reddy Subham Gupta Tuhin Karak Sarvadeepa Pal Koustav Sanyal D. Senapati Aman Kumar *[Signature]*

PT Calibration: - By this method, the voltage in the secondary windings of the PT is calculated using a voltmeter of suitable range and then keeping in view of the Nominal ratio and Transformation ratio of PT, the actual phase voltage is calculated.

$$\text{Nominal Ratio (Turns Ratio)} = N = \frac{N_P}{N_S}$$

$$\text{Transformation Ratio} = R_{CT} = N + \frac{I_S(R_P \cos \phi + X_P \sin \phi) + I_C R_P + I_M X_P}{N V_S}, \text{ where } R_P, X_P, I_C, I_M, I_S, V_S$$

V_S are Primary resistance, Primary reactance, Core loss component of exciting current, Magnetizing component of exciting current, Secondary current and Secondary voltage respectively.

Wattmeter Connection: - The Pressure coil is connected in parallel with the voltmeter, which is already connected with the S_1 and S_2 terminals of the PT secondary winding.

The Current coil is connected in series with the ammeter which was earlier connected to the S_1 and S_2 terminals of the CT secondary winding.

Observations:

Measurement of Current

Sl. No.	CT Nominal Transformation ratio N	Primary Current I_P (A)	Secondary Current I_S (A)	Actual Ratio $R_{CT} = I_P/I_S$	Ratio Error $[(N - R_{CT}) / R_{CT}] * 100\%$
1	$30/5 = 6$	1.1	0.186	5.914	1.454%
2	$30/5 = 6$	1.9	0.303	6.270	-4.306%
3	$30/5 = 6$	2.9	0.46	6.304	-4.822%
4	$30/5 = 6$	3.7	0.632	5.854	2.494%
5	$30/5 = 6$	4.6	0.753	6.108	-1.768%

Measurement of Voltage

Sl. No.	PT Nominal Transformation ratio N	Primary Voltage V_P (V)	Secondary Voltage V_S (V)	Actual Ratio $R_{PT} = V_P/V_S$	Ratio Error $[(N - R_{PT}) / R_{PT}] * 100\%$
1	$300/100 = 3$	17	6	2.833	5.895%
2	$300/100 = 3$	25	8	3.125	-4%
3	$300/100 = 3$	41	14	2.928	2.46%
4	$300/100 = 3$	55	18	3.055	-1.8%
5	$300/100 = 3$	67	22	3.045	-1.477%

Sayan Mondal Abantika Saha Sayan Das  Debnata Rakha Shakti Bhattacharya Anirban Maitra 

Kishore Rauti Subham Gupta Tuhin Karak Saradadeepa Pal Houston Samayal D'Souza Aman Kumar 

Measurement of Power

Sl. No.	CT Primary Current(A) I_p	CT Secondary Current(A) I_s	PT Primary Voltage(V) V_p	PT Secondary Voltage(V) V_s	Actual CT Ratio(I_p/I_s) R_{CT}	Actual PT Ratio(V_p/V_s) R_{PT}	Measured Power = Wattmeter Reading * 18 (W)	True Power $V_s I_s * R_{CT} * R_{PT}$	% Error
1	0.95	0.154	220	73.4	6.168	2.997	11.1*18=199.8	208.95	-4.38
2	1.96	0.322	220	73.5	6.087	2.993	22.1*18=397.8	431.17	-7.74
3	2.98	0.485	220	73.2	6.144	3.005	32.9*18=592.2	655.46	-9.65
4	3.94	0.641	220	72.9	6.146	3.017	44.7*18=804.6	866.47	-7.14
5	4.95	0.811	220	73	6.103	3.013	54.8*18=986.4	1088.64	-9.39

Calculations:

Calculations for first set of readings:

Measurement of current:

$$\text{CT Nominal transformation ratio} = N = \frac{30}{5A} = \frac{6}{1} = 6$$

$$\text{Actual ratio} = R_{CT} = \frac{I_p}{I_s} = \frac{1.1A}{0.186A} = 5.914$$

$$\begin{aligned} \text{Ratio Error} &= \frac{N - R_{CT}}{R_{CT}} \times 100\% = \frac{6.000 - 5.914}{5.914} \times 100\% = \frac{0.086}{5.914} \times 100\% \\ &= 0.01454 \times 100\% = 1.454\% \end{aligned}$$

Measurement of voltage:

$$\text{PT Nominal transformation ratio} = N = \frac{300V}{100V} = \frac{3}{1} = 3$$

$$\text{Actual ratio} = R_{PT} = \frac{V_p}{V_s} = \frac{17V}{6V} = 2.833$$

$$\begin{aligned} \text{Ratio Error} &= \frac{N - R_{PT}}{R_{PT}} \times 100\% = \frac{3.000 - 2.833}{2.833} \times 100\% = \frac{0.167}{2.833} \times 100\% \\ &= 0.05895 \times 100\% = 5.895\% \end{aligned}$$

Sayan Mandal Abantika Saha Sayan Das Subham Chakraborty Deenula Rakhi Shonali Bhattacharya Miriam Mol

K. Dhanya Reddy Subham Chakraborty Tuhin Karak Swapnil Pal Houston Sanyal D. Senapati Aman Kumar Gopikrishna Samanta

Measurement of power:

$$\text{Actual CT ratio} = R_{CT} = \frac{I_P}{I_S} = \frac{0.95A}{0.154} = 6.168$$

$$\text{Actual PT ratio} = R_{PT} = \frac{V_P}{V_S} = \frac{220V}{73.4V} = 2.997$$

$$\text{Measured Power } (W_M) = \text{Wattmeter reading} \times 3 \times 6 = 11.1 \times 18 = 199.8W$$

$$\text{True Power } (W_T) = (V_S I_S) \times R_{CT} \times R_{PT} = (73.4 \times 0.154) \times 6.168 \times 2.997 = 208.95W$$

$$\begin{aligned}\text{Ratio Error} &= \frac{W_M - W_T}{W_T} \times 100\% = \frac{199.8 - 208.95}{208.95} \times 100\% = \frac{-9.15}{208.95} \times 100\% \\ &= -0.0438 \times 100\% = -4.380\%\end{aligned}$$

Calculations using mean values:

Actual Transformation ratios (I_P/I_S) of the Current Transformer came out to be: -

- $\frac{1.1A}{0.186A} = 5.914$
- $\frac{1.9A}{0.303A} = 6.270$
- $\frac{2.9A}{0.46A} = 6.304$
- $\frac{3.7A}{0.632A} = 5.854$
- $\frac{4.6A}{0.753A} = 6.108$

So, the mean value of the Transformation ratio of this particular Current transformer is: -

$$\frac{(5.914 + 6.270 + 6.304 + 5.854 + 6.108)}{5} = 6.09$$

$$\text{Turns Ratio} = N = \frac{30A}{5A} = \frac{6}{1} = 6$$

$$\text{So, Ratio Error is } \frac{6-6.09}{6.09} \times 100\% = -1.4778\%$$

Actual Transformation ratios (V_P/V_S) of the Potential Transformer came out to be: -

- $\frac{17V}{6V} = 2.833$
- $\frac{25V}{8V} = 3.125$
- $\frac{41V}{14V} = 2.928$
- $\frac{55V}{18V} = 3.055$
- $\frac{67}{22V} = 3.045$

Sayan Mondal Abantika Saha Sayan Das [Signature] Deenula Rahi Shonali Bhattacharya Amritben Maji

X Dhruv Reddy Subham Gupta Tuhin Karak Soumada Pal Houston Sangal D Senapati Aman Kumar [Signature]

So, the mean value of the Transformation ratio of this particular Potential transformer is: -

$$\frac{(2.833 + 3.125 + 2.928 + 3.055 + 3.045)}{5} = 2.9972$$

$$\text{Turns Ratio } N = \frac{300V}{100} = \frac{3}{1} = 3$$

$$\text{So, Ratio Error is } \frac{3-2.9972}{2.9972} \times 100\% = 0.093\%$$

Power Calculation for different values of I_p and Constant value of $V_p = 220V$ yields different values of I_s and V_s : -

I_p	I_s	V_p	V_s	$R_{CT} = I_p/I_s$	$R_{PT} = V_p/V_s$	True Power $(V_s I_s) * R_{CT} * R_{PT} (W)$
0.95A	0.154A	220V	73.4V	0.95A/0.154A = 6.168	220V/73.4V = 2.997	73.4V * 0.154A * 6.168 * 2.997 = 208.95W
1.96A	0.322A	220V	73.5V	1.96A/0.322A = 6.087	220V/73.5V = 2.993	73.5V * 0.322A * 6.087 * 2.993 = 431.17W
2.98A	0.485A	220V	73.2V	2.98A/0.485A = 6.144	220V/73.2V = 3.005	73.2V * 0.485A * 6.144 * 3.005 = 655.46W
3.94A	0.641A	220V	72.9V	3.94A/0.641A = 6.146	220V/72.9V = 3.017	72.9V * 0.641A * 6.146 * 3.017 = 866.47W
4.95A	0.811A	220V	73V	4.95A/0.811A = 6.103	220V/73V = 3.013	73V * 0.811A * 6.103 * 3.013 = 1088.64W


And the deviation of the wattmeter reading from the true power is: -

True Power $(V_s I_s) * R_{CT} * R_{PT} (W)$	Measured Power = Wattmeter Reading * 18 = W_m	Percentage Error $= [(W_m - W_t)/W_t] * 100\%$
73.4V * 0.154A * 6.168 * 2.997 = 208.95 W	11.1 * 18 = 199.8 W	-4.38%
73.5V * 0.322A * 6.087 * 2.993 = 431.17 W	22.1 * 18 = 397.8 W	-7.74%
73.2V * 0.485A * 6.144 * 3.005 = 655.46 W	32.9 * 18 = 592.2 W	-9.65%
72.9V * 0.641A * 6.146 * 3.017 = 866.47 W	44.7 * 18 = 804.6 W	-7.14%
73V * 0.811A * 6.103 * 3.013 = 1088.64 W	54.8 * 18 = 986.4 W	-9.39%

Sayan Mondal Abantika Saha Sayan Das Sayantika Saha Debnata Ray Sankha Bhattacharya Miriam Maiti

K. Dhanya Reddy Subham Gupta Tuhin Karak Swadeepa Pal Houston Sanyal D. Senapati Aman Kumar Himanshu Samanta


True Power & Measured Power VS I_s

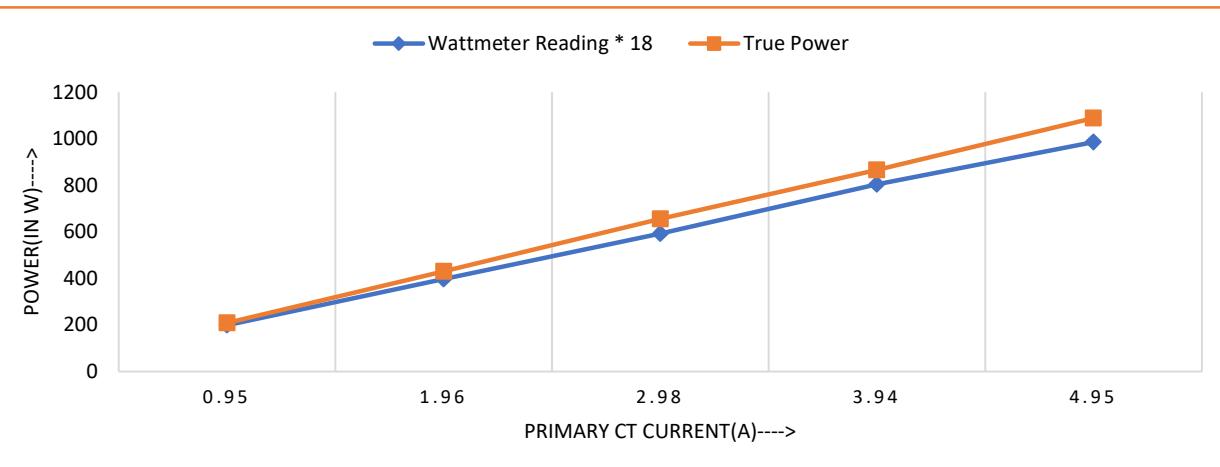

Here, we can see there is a very slight difference between the True power and Measured power curves due to instrumental errors.

Experimental Graphs:

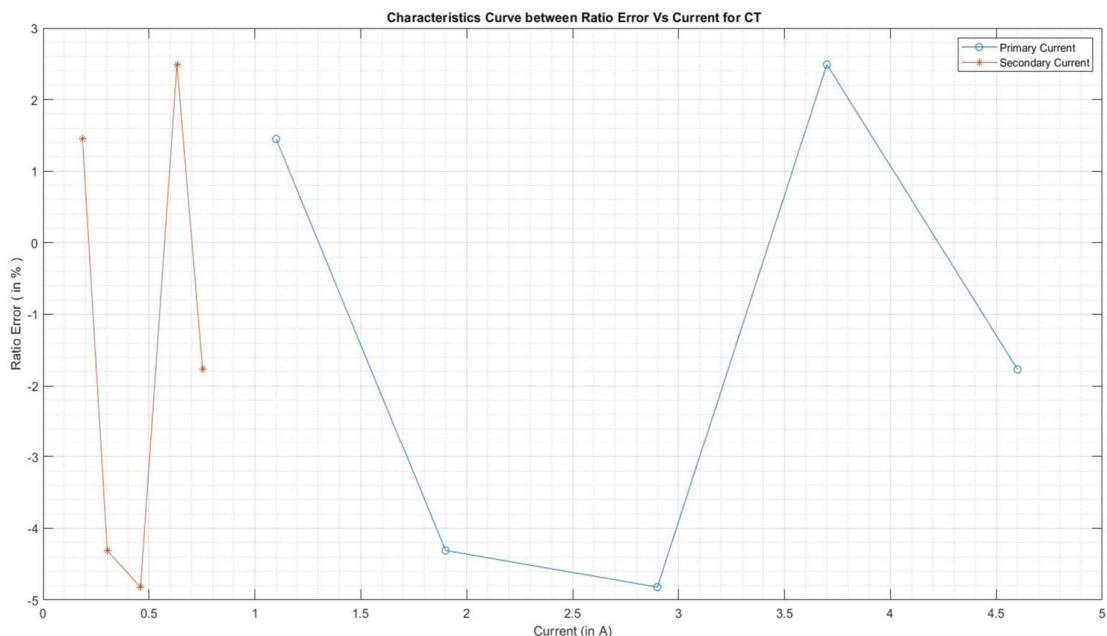
Ratio Error vs Current for CT (I_s & I_p)




Sayan Mondal Abantika Saha Sayan Das Debjit Sen Debnath Ray Suhani Bhattacharya Amritam Maji

K. D. Bhargav Reddy Subham Gupta Tuhin Kumar Suvadipda Pal Koustav Sanyal D. Senapati Aman Kumar Dipak Kumar

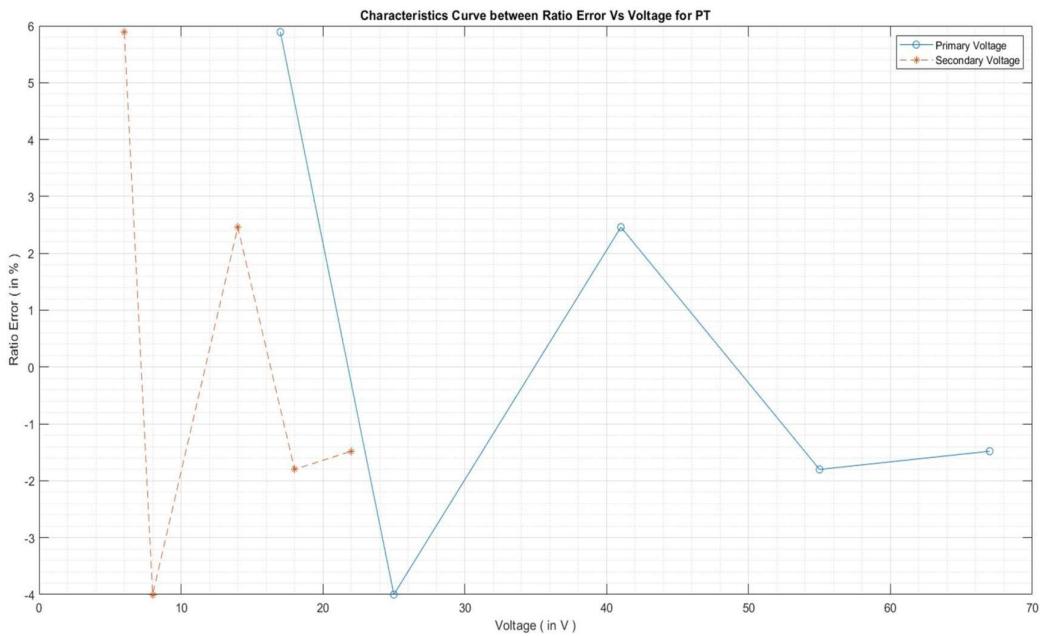Ratio Error vs Voltage for PT (V_S & V_P)



% Power Error vs Measured Nominal Power

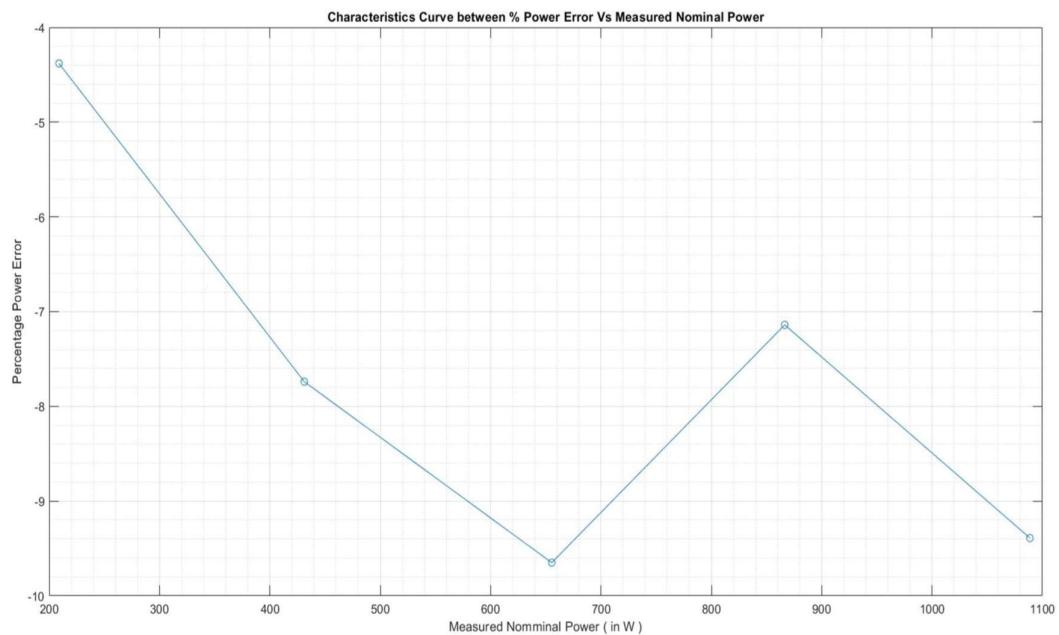

Sayan Mondal Abantika Saha Sayan Das  Deenula Rahi Shonali Bhattacharya Miriam Mol

K. Dhanya Reddy Subham Gupta Tuhin Karak Saradadeep Pal Koustav Sanyal D. Senapati Aman Kumar 

Conclusion:

From the experiment and the results above we conclude that -

The mean transformation ratio of the CT is 6.09

The mean transformation ratio of the PT is 2.9972

The mean percentage error is -7.66%.

Using a CT, we can easily step down the high current across any load and measure it safely with normal instruments.

Using a PT, we can easily step down the high voltage across any load and measure it safely with normal instruments.

Thus, a combination of CT and PT can be used to measure the power across a load. They effectively step down the high voltage or current and the readings can be taken safely with instruments in the normal range.

Sayan Mondal Abantika Saha Sayan Das Dipankar Dey Dipankar Dey Sokini Bhattacharya Amitabh Maji

K.Dhingra Siddhartha Gupta Tuhin Karak Suvadeepa Pal Koustav Sanyal D Senapati Anan Kumar Suparna Samanta