

National Institute of Technology, Durgapur
Department of Electrical Engineering

Experiment No: 1

**MEASUREMENT OF POWER IN SINGLE-PHASE CIRCUIT BY
THREE-VOLTMETER METHOD AND THREE-AMMETER METHOD**

Objective:

- (i) To measure the single-phase power in a single phase a.c. circuit by using three voltmeters.
- (ii) To measure the single-phase power in a single phase a.c. circuit by using three ammeters.

Apparatus Required: It consists of following instruments

Sr No	Instrument Name	Specification	Quantity	Makers Name

Theory

Power measurement in Single phase a.c. circuit by using three voltmeters

Power consumed by load= $P = V_2 I \cos \phi$

From the phasor diagram we can write,

$$V_3^2 = V_1^2 + V_2^2 + 2 \cdot V_1 \cdot V_2 \cos \phi$$

$$\text{Power factor, } \cos \phi = (V_3^2 - V_1^2 - V_2^2) / 2 \cdot V_1 \cdot V_2$$

$$I = V_1 / R$$



Now,

$$P_{\text{calculated}} = V_2 I \cos \phi = V_2 (V_1 / R) \cos \phi$$

$$= (V_1 V_2 / R) ((V_3^2 - V_1^2 - V_2^2) / 2 \cdot V_1 \cdot V_2) = (1/2R) * (V_3^2 - V_1^2 - V_2^2)$$

From the above equation it can be observed that, the power and power factor in an a.c circuit can be measured by using 3-single phase voltmeters, instead of a wattmeter.
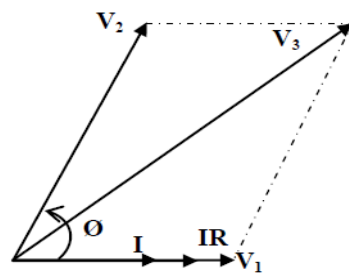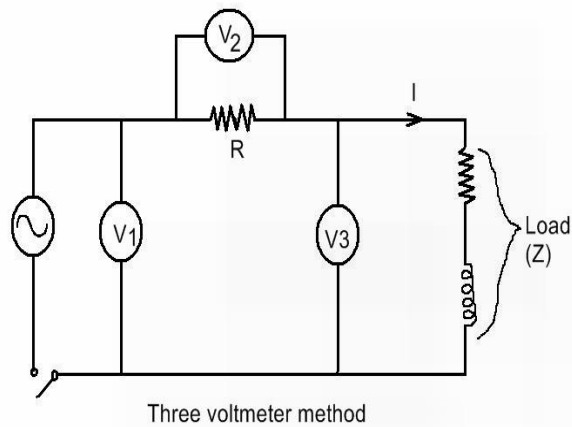
$$\text{Percentage Error} = (P_{\text{calculated}} - \text{Wattmeter Reading}) / \text{Wattmeter Reading}$$



Single ph

Phasor diagram of the above circuit.

Power consumed by load = $P = V I_3 \cos \theta$

From the phasor diagram we can write,

$$I_1^2 = I_2^2 + I_3^2 + 2 I_2 I_3 \cos \theta$$

$$\text{Power factor, } \cos \theta = (I_1^2 - I_2^2 - I_3^2) / 2 I_2 I_3$$

$$I_2 = V/R$$


Now,


$$P_{\text{calculated}} = V I_3 \cos \theta = I_2 R I_3 \cos \theta$$

$$= R I_2 I_3 ((I_1^2 - I_2^2 - I_3^2) / 2 I_2 I_3) = (R/2) * (I_1^2 - I_2^2 - I_3^2)$$

From the above equation it can be observed that, the power and power factor in an a.c circuit can be measured by using 3-single phase ammeters, instead of a wattmeter.
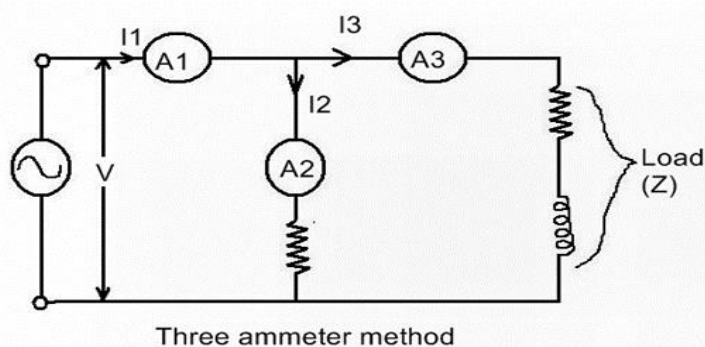
$$\text{Percentage Error} = (P_{\text{calculated}} - \text{Wattmeter Reading}) / \text{Wattmeter Reading}$$



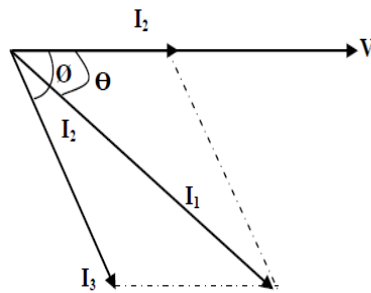

Phasor diagram of the above circuit.

Procedure:

Three-Voltmeter Method

1. Make connections according to circuit diagram.
2. Measure the value of R and record it in the observation table.
3. Observe V_1 , V_2 and V_3 for a given load and record these in the observation table. Calculate the power and power factor for the given load.
4. Change the load resistance R , measure it (after disconnecting the voltmeter V_2) and record its value in the observation table.
5. Take another set of observation of V_1 , V_2 and V_3 , calculate the power and power factor and record these in the observation table.
6. Take at least three sets of observations for three different values of R and calculate the power and power factor in each case. Take mean of the calculated values of power and power factor and record in the table.

Three-Ammeter Method

1. Make connections according to circuit diagram.
2. Measure the value of R and record it in the observation table.
3. Observe I_1 , I_2 and I_3 for a given load and record these in the observation table. Calculate the power and power factor for the given load.
4. Change the load resistance R , measure it (after disconnecting the Circuit) and record its value in the observation table.
5. Take at least three sets of observations for three different values of R and calculate the power and power factor in each case. Take mean of the calculated values of power and power factor and record in the table.

Experimental Results:

Table1: Three-Voltmeter Method

Sl No	R (ohm)	V ₁ (Volt)	V ₂ (Volt)	V ₃ (Volt)	Power (Watt)	p.f	Mean	
							P	p.f

Table1: Three-Ammeter Method

Sl No	R (ohm)	I ₁ (Amp)	I ₂ (Amp)	I ₃ (Amp)	Power (Watt)	p.f	Mean	
							P	p.f

Suggested Reading:

1. Electrical Measurement & Measuring Instrument by E.W.Golding