



National Institute Of Technology Durgapur

ELECTRICAL MEASUREMENT LABORATORY (EES-351)

Group V

Experiment 5

Measurement power in a three-phase circuit

23rd June, 2021

Members (63-77)

- | | |
|--------------------------------|--------------------------|
| ✓ Sayan Mondal (63) | ✓ Subham Gupta (71) |
| ✓ Abantika Saha (64) | ✓ Tuhin Karak (72) |
| ✓ Sayan Das (65) | ✓ Souradepta Pal (73) |
| ✓ Raj Suyash Ranjan (66) | ✓ Koustav Sanyal (74) |
| ✓ Vemula Rahul (67) | ✓ Diksha Senapati (75) |
| ✓ Sohini Bhattacharya (68) | ✓ Aman Kumar (76) |
| ✓ Anirban Moi (69) | ✓ Yogeswar Sarnakar (77) |
| ✓ Kalakonda Dheeraj Reddy (70) | |

EXPERIMENT NUMBER: 5


AIM OF THE EXPERIMENT: Measurement power in a three-phase circuit

OBJECTIVE: To measure power in a three-phase load by two wattmeter methods.

APPARATUS REQUIRED:

Sl. No.	Instrument Name	Specification	Quantity
1	A.C. Wattmeter	0-600V, 750W	2
2	A.C. Voltmeter	0-600V	1
3	A.C. Ammeter	0-5 A	1
4	Resistors	25,50 Ω	2
5	Inductance	0.27566 H, 0.437274 H, 0.5 H, 0.37 H	4
6	A.C Voltage Source	440 V (peak), 50 Hz	1

Circuit diagram:

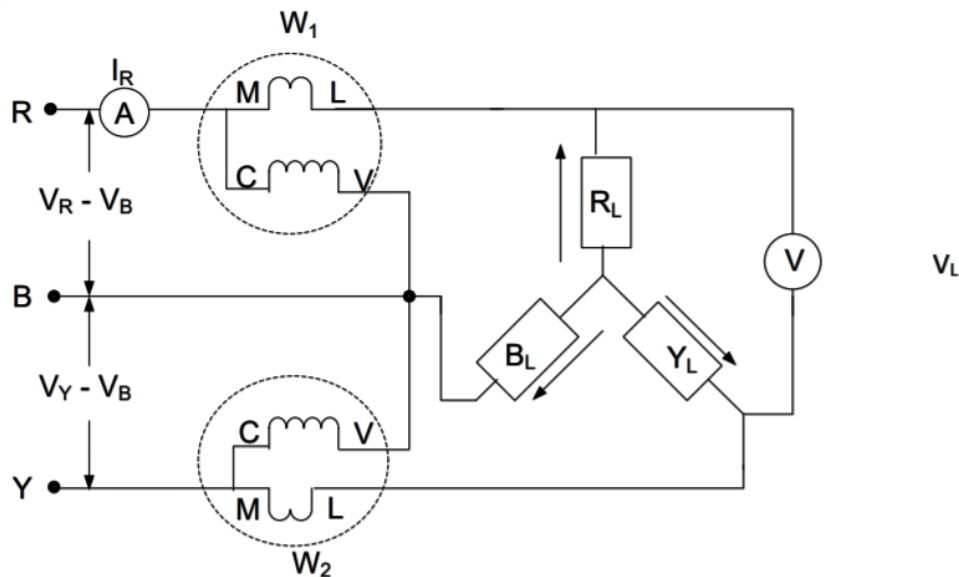

Circuit diagram of Power measurement by two wattmeter method

Gayan Mondal, Abantika Saha, Sayan Das, Raju Saha, Tanuika Bala, Shikhi Bhattacharya, Anirban M, Dhruv Rathi, Subhom Gupta, Tushin Karak, Souradepta Pal, Houshu Sanyal, D Senapati, Anurag Kumar, Himanshu Samal

OBSERVATION TABLE:

1. Balanced Load:

SL. NO.	LINE CURRENT (I_L) in Amp	LINE VOLTAGE (V_L) in Volt	1st Wattmeter reading (W_1) in Watt	2nd Wattmeter reading (W_2) in Watt	POWER = $W_1 + W_2$	$\phi = \tan^{-1} \frac{\sqrt{3}(W_1 - W_2)}{W_1 + W_2}$ (In degrees)	P. F. = $\cos \phi$
1	5.081	440	1936	1936	3872	0	1
2	2.54	440	0.05042	968	968.05042	-59.997	0.500
3	1.738	440	-132.7	585.7	453	-69.996	0.342
4	2.818	440	-297.8	893.5	595.7	-73.897	0.277
5	1.597	440	-251.3	442.6	191.3	-80.956	0.157
6	2.317	440	-288.3	630.7	342.4	-77.860	0.210

2. Unbalanced Load:

SL. NO.	LINE CURRENT (I_L) in Amp	LINE VOLTAGE (V_L) in Volt	1st Wattmeter reading (W_1) in Watt	2nd Wattmeter reading (W_2) in watt	POWER = $W_1 + W_2$
1	3.811	440	1452	1936	3388
2	2.324	440	135.1	89.2	224.3
3	1.664	440	-52.47	555.7	503.23

CALCULATIONS:

Reading 1:

First Wattmeter reading = $W_1 = 1936 \text{ W}$

Second Wattmeter reading = $W_2 = 1936 \text{ W}$

Total Power = $W_1 + W_2 = 3872 \text{ W}$

$$\phi = \tan^{-1} \frac{\sqrt{3}(W_1 - W_2)}{W_1 + W_2} = \tan^{-1} \frac{\sqrt{3}(1936 - 1936)}{3872} = 0^\circ$$

Power factor = $\cos \phi = \cos 0^\circ = 1$

Sayan Mondal *Abantika Saha* *Sayan Das* *Devi Saha* *Devi Saha* *Sohini Bhattacharya* *Anirban M*
K. Dhanya Rathi *Subhom Gupta* *Tushin Karak* *Souradepta Pal* *Houstar Sanyal* *D. Senapati* *Anurag Kumar* *Harshad Sankar*

Reading 2:

First Wattmeter reading = $W_1 = 0.05042 \text{ W}$

Second Wattmeter reading = $W_2 = 968 \text{ W}$

Total Power = $W_1 + W_2 = 968.05942 \text{ W}$

$$\phi = \tan^{-1} \frac{\sqrt{3}(W_1 - W_2)}{W_1 + W_2} = \tan^{-1} \frac{\sqrt{3}(0.05042 - 968)}{968.05942} = -59.997^\circ$$

Power factor = $\cos \phi = \cos(-59.997^\circ) = 0.500$

Reading 3:

First Wattmeter reading = $W_1 = -132.7 \text{ W}$

Second Wattmeter reading = $W_2 = 585.7 \text{ W}$

Total Power = $W_1 + W_2 = 453 \text{ W}$

$$\phi = \tan^{-1} \frac{\sqrt{3}(W_1 - W_2)}{W_1 + W_2} = \tan^{-1} \frac{\sqrt{3}(-132.7 - 585.7)}{453} = -69.996^\circ$$

Power factor = $\cos \phi = \cos(-69.996^\circ) = 0.342$

Reading 4:

First Wattmeter reading = $W_1 = -297.8 \text{ W}$

Second Wattmeter reading = $W_2 = 893.5 \text{ W}$

Total Power = $W_1 + W_2 = 595.7 \text{ W}$

$$\phi = \tan^{-1} \frac{\sqrt{3}(W_1 - W_2)}{W_1 + W_2} = \tan^{-1} \frac{\sqrt{3}(-297.8 - 893.5)}{595.7} = -73.897^\circ$$

Power factor = $\cos \phi = \cos(-73.897^\circ) = 0.277$

Reading 5:

First Wattmeter reading = $W_1 = -251.3 \text{ W}$

Second Wattmeter reading = $W_2 = 442.6 \text{ W}$

Total Power = $W_1 + W_2 = 191.3 \text{ W}$

$$\phi = \tan^{-1} \frac{\sqrt{3}(W_1 - W_2)}{W_1 + W_2} = \tan^{-1} \frac{\sqrt{3}(-251.3 - 442.6)}{191.3} = -80.956^\circ$$

Power factor = $\cos \phi = \cos(-80.956^\circ) = 0.157$

Sayan Mondal *Abanika Saha* *Sayan Das* *Devi Saha* *Debnata Pal* *Sohini Bhattacharya* *Anirban M*
S. Dhanyashree *Subhom Gupta* *Tuhin Karak* *Souradepta Pal* *Houstar Sanyal* *D. Senapati* *Anurag Kumar* *Himadri Sanyal*

Reading 6:

$$\text{First Wattmeter reading} = W_1 = -288.3 \text{ W}$$


$$\text{Second Wattmeter reading} = W_2 = 630.7 \text{ W}$$

$$\text{Total Power} = W_1 + W_2 = 342.4 \text{ W}$$


$$\phi = \tan^{-1} \frac{\sqrt{3}(W_1 - W_2)}{W_1 + W_2} = \tan^{-1} \frac{\sqrt{3}(-288.3 - 630.7)}{342.4} = -77.860^\circ$$

$$\text{Power factor} = \cos \phi = \cos(-77.860^\circ) = 0.210$$

PHASOR DIAGRAM:

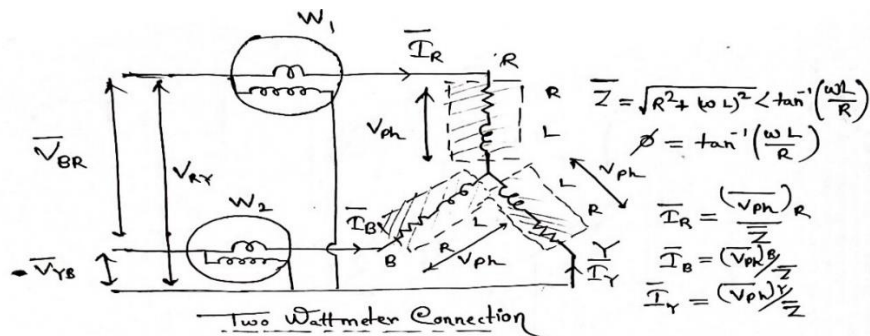

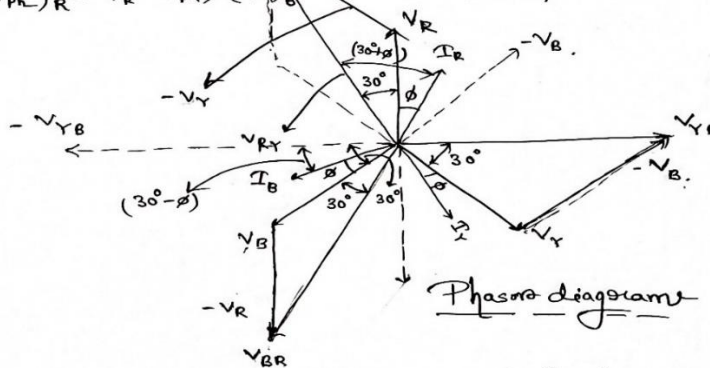Phase sequence is RYB.
 $\bar{V}_R = V_{ph} \angle 0^\circ$, $\bar{V}_Y = V_{ph} \angle -120^\circ$, $\bar{V}_B = V_{ph} \angle +120^\circ$
 ωL , $\angle -120^\circ = \omega^2$, $\angle +120^\circ = \omega$.
 $\therefore (\bar{V}_{ph})_R = \bar{V}_R = V_{ph}$, $(\bar{V}_{ph})_B = \bar{V}_B = V_{ph} \omega$, $(\bar{V}_{ph})_Y = \bar{V}_Y = V_{ph} \omega^2$.




$$\begin{aligned} \text{Now, for } W_1, \quad P_1(W_1) &= I_R V_{RY} \cos(30^\circ + \phi) \\ \text{and for } W_2, \quad P_2(W_2) &= I_B V_{YB} \cos(30^\circ - \phi) = I_B V_{BY} \cos(30^\circ - \phi) \\ \therefore W_1 + W_2 &= I_R V_{RY} \cos(30^\circ + \phi) + I_B V_{BY} \cos(30^\circ - \phi) \\ &= I_L V_{LL} \left\{ \cos(30^\circ + \phi) + \cos(30^\circ - \phi) \right\} \\ &= V_{LL} I_L \left\{ 2 \cos \left\{ \frac{30^\circ + \phi + 30^\circ - \phi}{2} \right\} \cos \left\{ \frac{30^\circ + \phi - 30^\circ - \phi}{2} \right\} \right\} \\ &= \frac{\sqrt{3}}{2} \times 2 V_{LL} I_L \cos \phi = \sqrt{3} V_{LL} I_L \cos \phi \\ W_1 - W_2 &= V_{LL} I_L \sin \phi, \quad \therefore \frac{W_1 - W_2}{W_1 + W_2} = \frac{1}{\sqrt{3}} \tan \phi, \quad \phi = \tan^{-1} \left[\frac{\sqrt{3}(W_1 - W_2)}{W_1 + W_2} \right] \end{aligned}$$

Jayan Mondal, Abanika Saha, Sayan Das, Raju Sun, Jannala Babu, Sukini Bhattacharya, Anirban M,
 Chhaya Bhatt, Subhom Gupta, Tushin Karak, Souradepta Pal, Houshu Sanyal, D Senapati, Anuraj Kumar, Himadri Samanta

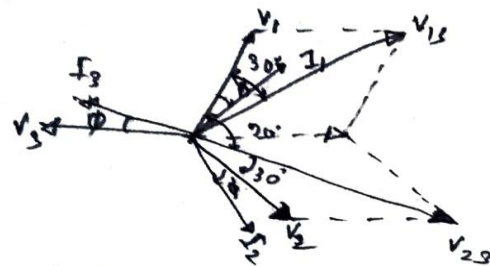QUESTIONS:

- Establish that power factor may also be estimated from two wattmeter readings.



Let V_1, V_2, V_3 be the rms values of phase voltage and I_1, I_2, I_3 be the rms values of phase currents

The total load is balanced therefore,

Phase Voltages, $V_1 = V_2 = V_3 = V$ (say)

Line Voltages, $V_{12} = V_{23} = V_{31} = \sqrt{3}V$

Phase Currents, $I_1 = I_2 = I_3 = I$ (say)

Line Currents, $I_1 = I_2 = I_3 = I$

Power factor $= \cos \phi$

The phase currents lag the corresponding phase voltages by an angle ϕ .

The current through wattmeter P_1 is I_1 and voltage across its pressure coil is V_{12} . I_1 lags V_{12} by an angle $(30^\circ - \phi)$

\therefore Reading of P_1 wattmeter, $P_1 = V_{12} I_1 \cos(30^\circ - \phi) = \sqrt{3}VI \cos(30^\circ - \phi)$

The current through wattmeter P_2 is I_2 and voltage across its pressure coil is V_{23} . I_2 lags V_{23} by an angle $(30^\circ + \phi)$

\therefore Reading of P_2 wattmeter, $P_2 = V_{23} I_2 \cos(30^\circ + \phi) = \sqrt{3}VI \cos(30^\circ + \phi)$

Sum of reading of two wattmeters, $P_1 + P_2$

$$= \sqrt{3}VI [\cos(30^\circ - \phi) + \cos(30^\circ + \phi)]$$

$$= \sqrt{3}VI \cos \phi$$

This is the total power consumed by the load $P = P_1 + P_2$

\therefore Difference of readings of two wattmeters

$$P_1 - P_2 = \sqrt{3}VI [\cos(30^\circ - \phi) - \cos(30^\circ + \phi)]$$

$$= \sqrt{3}VI \sin \phi$$

$$\frac{P_1 - P_2}{P_1 + P_2} = \frac{\sqrt{3}VI \sin \phi}{\sqrt{3}VI \cos \phi} = \tan \phi \quad \text{or} \quad \tan^{-1} \sqrt{3} \frac{P_1 - P_2}{P_1 + P_2}$$

$$\therefore \text{Power factor, } \cos \phi = \cos \left(\tan^{-1} \sqrt{3} \frac{P_1 - P_2}{P_1 + P_2} \right)$$

Therefore established power factor can be measured by two wattmeter method.

Gayam Mondal Abantika Saha Sayan Das Raju Sun Jannala Rishi Sanku Bhattacharya Anirban M
 Dhruv Rathi Subhom Gupta Tushin Karak Souradepta Pal Houshu Sanyal Dhanabati Anur Kumar Himanshu Samal

- Explain why the wattmeter will give (a) zero reading (b) negative reading.

The reading of a wattmeter is proportional to (current through the current coil) x (voltage across the pressure coil) x Cosine (angle between this current and this voltage). Depending on the value of the cosine the wattmeter reading can be zero or negative. For a three-phase balanced load the two wattmeter readings will be, $W_1 = V_{ab} \cdot I_a \cdot \cos(30^\circ + \phi)$ and $W_2 = V_{cb} \cdot I_c \cdot \cos(30^\circ - \phi)$.

- When this angle becomes equal to 90 degrees the reading of the wattmeter will be zero. So, if $\phi = 60^\circ$ (P.F. equal to 0.5), a zero reading will be obtained for the first wattmeter.
- When this angle becomes more than 90 degrees the reading of the wattmeter will be negative. For a three-phase balanced load when $\phi > 60^\circ$ (P.F. less than 0.5), a negative reading will be obtained for the first wattmeter (W_1). In this case, the voltage-coil connections must be reversed in order that the instrument may give a positive or forward reading.

CONCLUSION:

- With this method we can measure power in a phase three wire system with unbalanced or balance load. The load may be star or delta connected; in this experiment we have used star connected load.
- Reading of wattmeter W_1 is zero when the load power factor is 0.5 lagging i.e., $\phi = 60^\circ$.
- Reading of wattmeter W_1 is negative for $\phi > 60^\circ$. In this case, we reverse the connections to the pressure coil in order to measure power registered by wattmeter W_1 . However, the reading thus obtained must be taken as negative while calculating total power and power factor.
- The reading of W_1 is positive when $\phi < 60^\circ$.
- Both the wattmeters indicate the same readings when power factor of load is unity.
- All our calculations match with these observations and the experiment thus was successful.

Sayan Mondal Abanika Saha Sayan Das Devi Saha Devi Saha Sohini Bhattacharya Anirban M
Chiranjit Subhom Tuhin Souradepta Pal Houstar Sanyal D. Senapati Anurag Kumar Himanshu