

National Institute of Technology
Durgapur

Network Analysis & Synthesis Lab
(EES-451)

- Sayan Mondal
- 19EE8063
- 3rd Sem (Lab)

Experiment - 1

Transient Response of RC & RL Circuits

Experiment No. EES / 451/01

Title : Transient Response of RC and RL Circuits

Objective -

1. Study the transient response of a series RC circuit and understand the time concept by using pulse waveforms.

Theory:

In this experiment, we apply a pulse waveform to the RC circuit to analyse the transient response of the circuit. The pulse width relative to a circuit's time constant determines how it is affected by an RC circuit.

Time Constant (τ): A measure of time required for certain changes in voltage and current in RC and RL circuits. Generally, when the elapsed time exceeds five time constants (5τ) after switching has occurred, the currents and voltages have reached their final value, which is called steady state response.

The time constant of an RC circuit is the product of equivalent capacitance and Thenevin resistance as viewed from the terminals of an equivalent capacitor.

$$\tau = RC \quad \dots \quad (1)$$

A pulse is a voltage or current that changes from one level to the other and back again. If a waveform's high time equals its low time, it is called a square wave.

- The pulse width (t_p) of an ideal square wave is equal to half the time period.
- Then frequency, $f = \frac{1}{2t_p}$

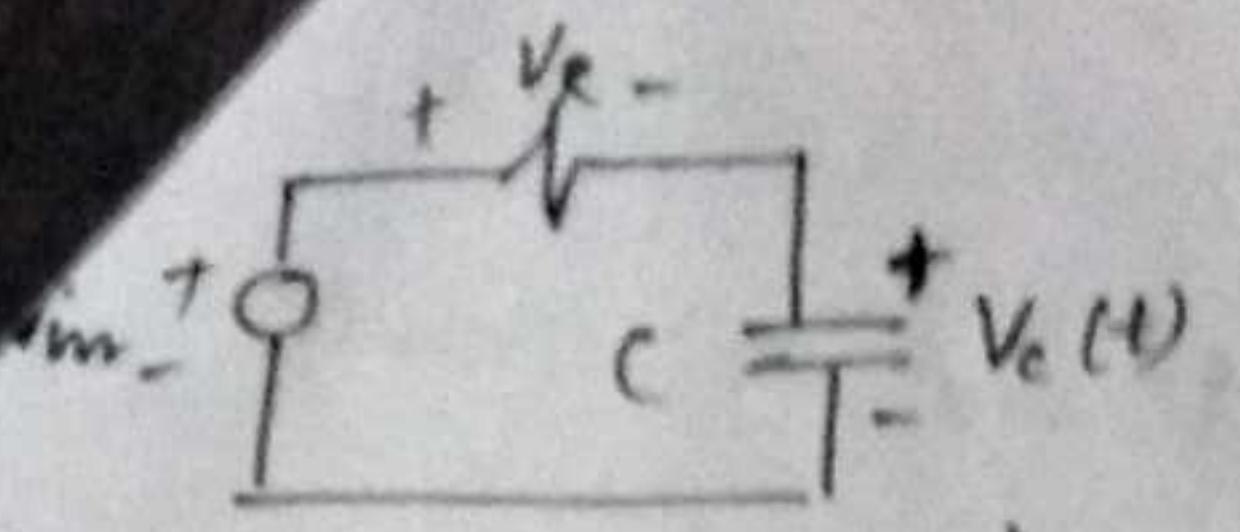


Fig-1 (series RC ckt)

Given by: $V_c(t) = V(1 - e^{-t/RC}) + V_{in} \quad t \geq 0 \quad \text{--- (3)}$
where V is the applied voltage to the circuit for $t \geq 0$.

$RC = \tau$ as the time constant. The response is shown in the figure below.

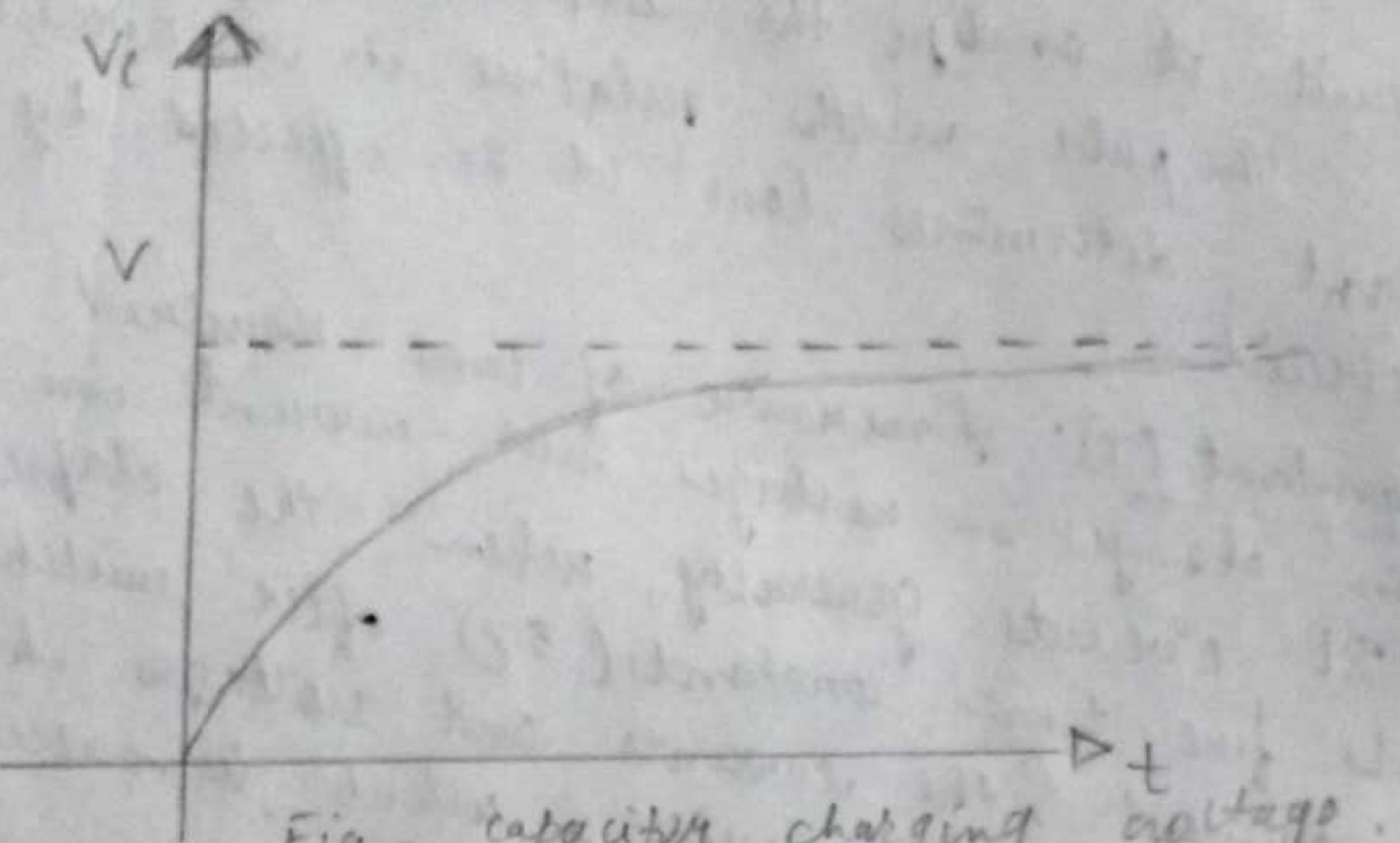


Fig. capacitor charging voltage

The discharge voltage for the capacitor is given by

$V_c(t) = V_0 e^{-t/RC} \quad t \geq 0 \quad \text{--- (4)}$, where V_0 is the initial voltage stored in capacitor at $t = 0$, and $RC = \tau$ as the time constant. The response curve is decaying exponential as shown below -

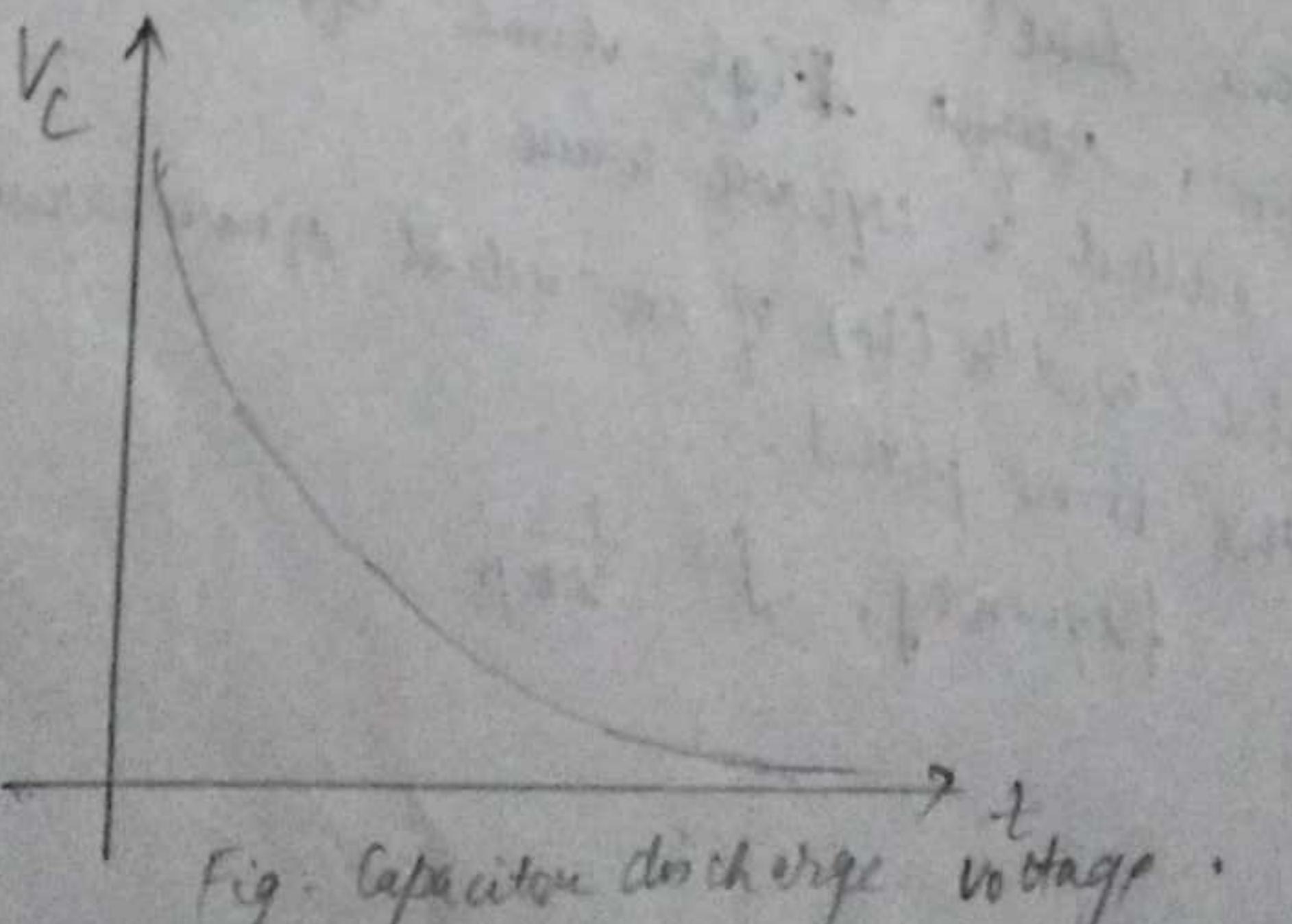


Fig. Capacitor discharge voltage

From Kirchhoff's law, it can be shown that the charging voltage $V_c(t)$ across the capacitor is

Objective
2. Study
R L cou
concept

Theory:

In this to the R of the time const

R-L circuit

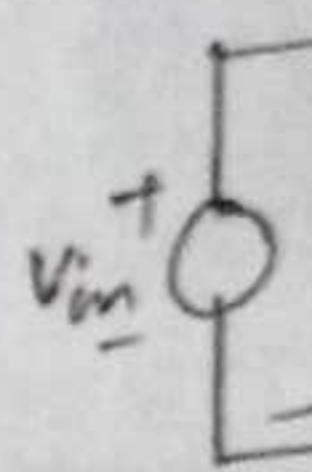


Fig-

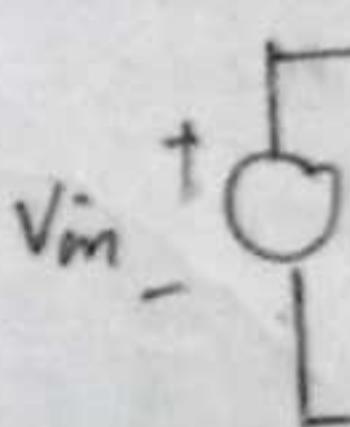


Fig-

increases \propto
has the \propto
they both
to $1 -$
across the

$i_L(t) = \frac{V_{in}}{L}$
where
for $t >$
shown

Objective

2. Study the transience due to inductors using a series R L circuit and understand the time constant concept.

Theory:

In this experiment we apply a square waveform to the RL circuit to analyse the transient response of the circuit. The pulse-width relative to the circuit's time constant determines how it is affected by the R-L circuit.

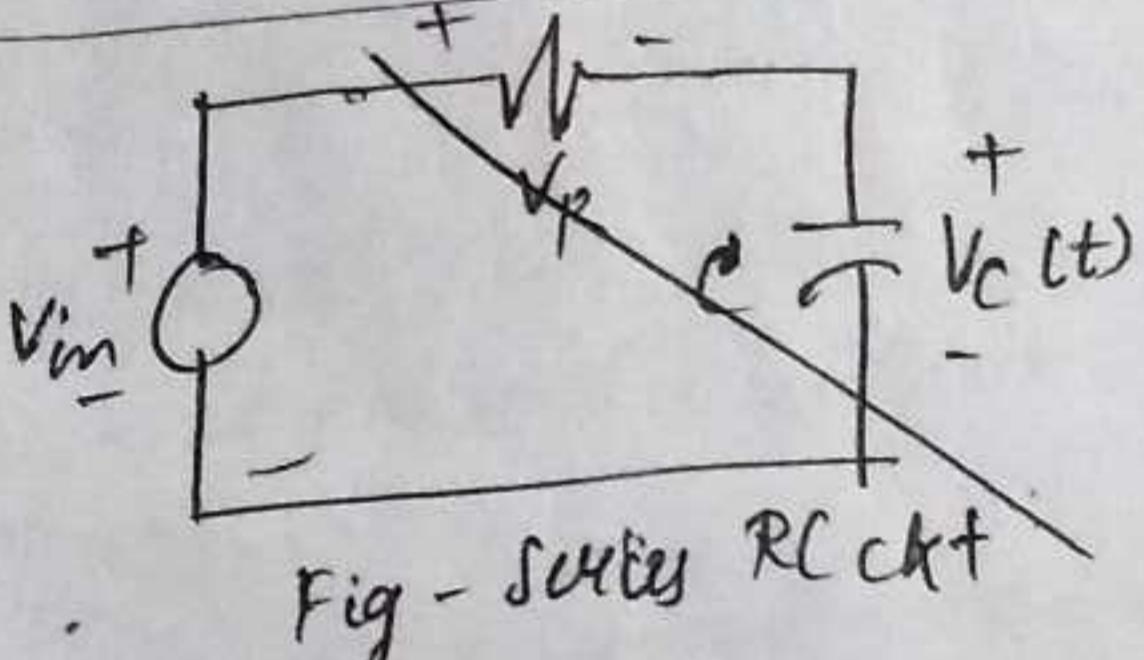


Fig - Series RC ckt

From Kirchoff's law it can be shown that the charging voltage $V_C(t)$ across the capacitor is given by $V_C(t) = V(1 - e^{-t/RC})$ for $t \geq 0$

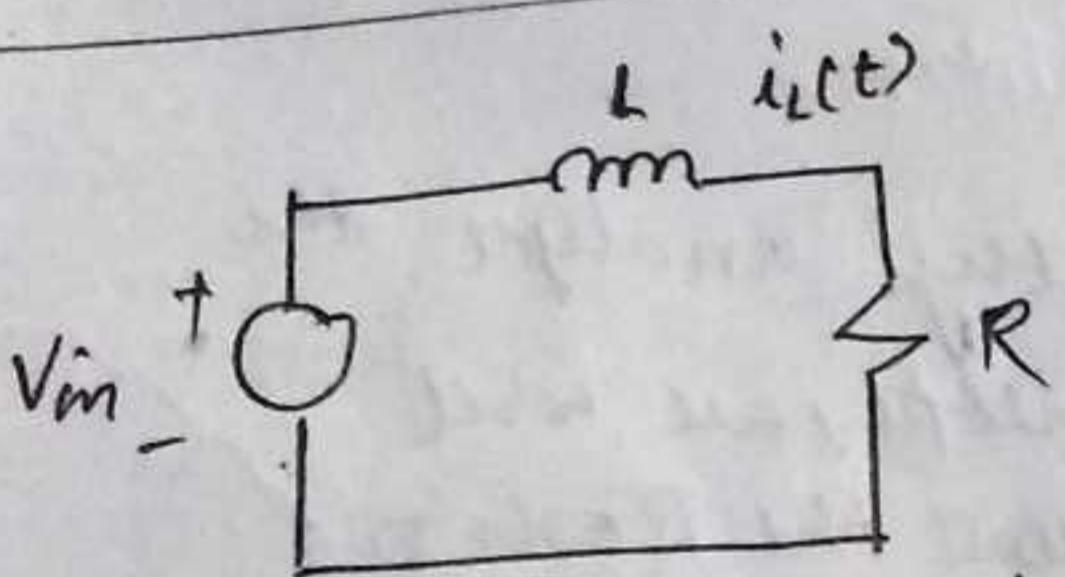


Fig - R L series ckt

In an RL circuit, voltage across the inductor decreases with time while in the RC circuit the voltage across the capacitor

increases with time. Thus, current in an RL circuit has the same waveform as voltage in an RC circuit they both rise to their final value exponentially according to $1 - e^{-t/\tau}$. The expression for the current build-up across the inductor is given by

$$i_L(t) = \frac{V}{R} [1 - e^{-\frac{t}{RC}}] \quad t \geq 0 \quad \dots \quad (3)$$

where V is the applied source voltage to the circuit. For $t > 0$, the response curve is increasing and is shown in figure 2.

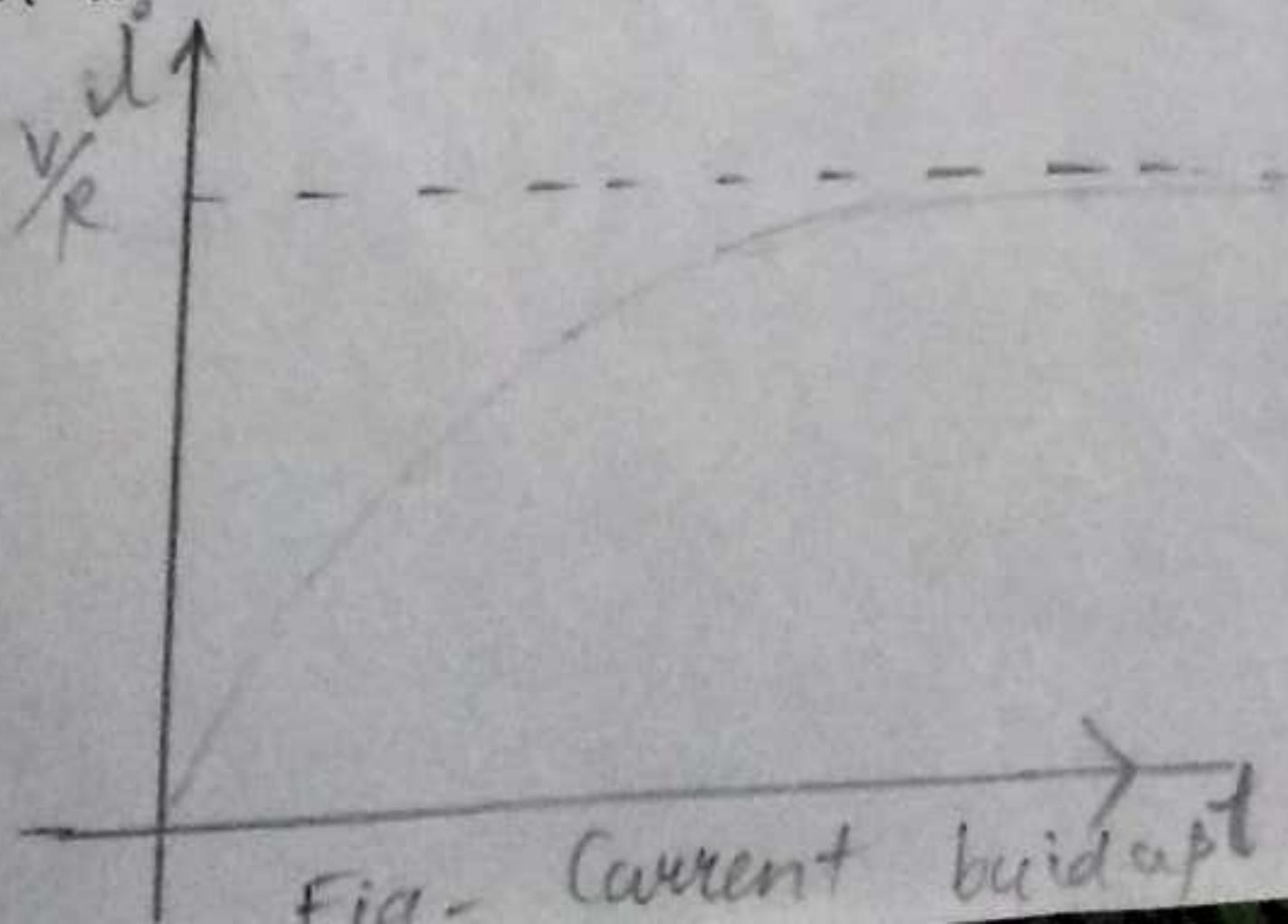


Fig - Current buildup across inductor

The expression for the current decay across the inductor is given by :

$$i_L(t) = i_0 e^{-(R/L)t} \quad \dots \dots \quad (1)$$

where i_0 is the initial current stored in the inductor at $t=0$, $\frac{R}{L} = \tau$ as time constant.

The response curve is a decaying exponential and is shown in figure 3.

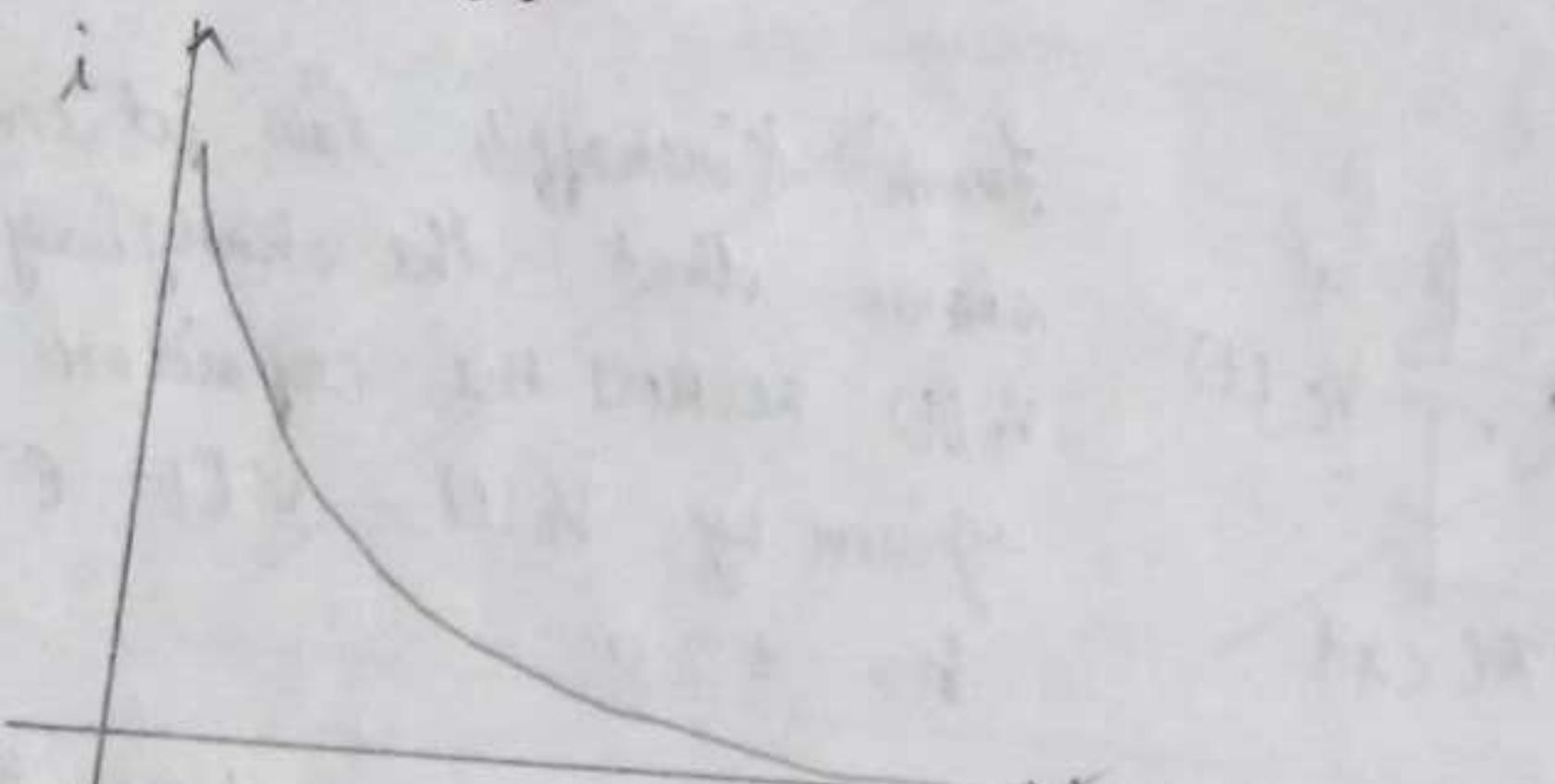


Fig 3 current decay across inductor

Since it is not possible to directly analyse the current through inductor on a scope, we will measure the output voltage across the Resistor. The resistive waveform will be similar to the inductor current as $V_R = I R$. From the resistor voltage on the scope, we should be able to measure the time constant τ which should be equal to

$\tau = \frac{L}{R_{\text{total}}}$. Here, R_{total} is the total resistance and can be calculated from $R_{\text{total}} = R_{\text{inductance}} + R$.

where $R_{\text{inductance}}$ is the measured value of the inductor resistance and can be measured by connecting inductor to an ohm meter prior to running the experiment.

Observati

Table - I

Sl. No.	FRE
1.	
2.	6
3.	

questions -

1) Calculate to the m

ans: Tim

Variat

FRE

2) Discu

Ans: We

discu

st &

conv

Observation Table -

Table-I : For RC circuit, $R_1 = 1.48 \text{ k}\Omega$, $C = 3.9 \mu\text{F}$

Sl. No.	Frequency of square wave (Hz)	Amplitude (V) (P-P)	Time Constant (τ)		% Error
			Exp. Calc.	Theo. Calc.	
1.	56.07	3.0	3.56×10^{-3}	5.772×10^{-3}	38%
2.	62.25	3.0	3.0×10^{-3}	5.772×10^{-3}	48%
3.	45.05	3.0	3.75×10^{-3}	5.772×10^{-3}	35%

Questions -

- 1) Calculate the time constant using eqn(1) and compare it to the measured values.

Ans: Time constant $\tau = RC = 1.48 \text{ k}\Omega \times 3.9 \mu\text{F}$
~~= $1.48 \times 10^3 \times 3.9 \times 10^{-6}$~~
 $= 5.772 \times 10^{-3} \text{ s.}$

Variation from Readings.

Frequency (Hz)	τ (Theoretical) (s)	τ (Experimental) (s)	% Error
56.07	5.772×10^{-3}	3.56×10^{-3}	38%
62.25	5.772×10^{-3}	3.0×10^{-3}	48%
45.05	5.772×10^{-3}	3.75×10^{-3}	35%


- 2) Discuss the Effect of changing component value.

Ans: We know $\tau = RC$. Thus changing R , or C is directly proportional to increasing the time constant. A higher value of R or C will give a higher time constant and vice versa.

Increasing R or C increases the time constant.

Charging:

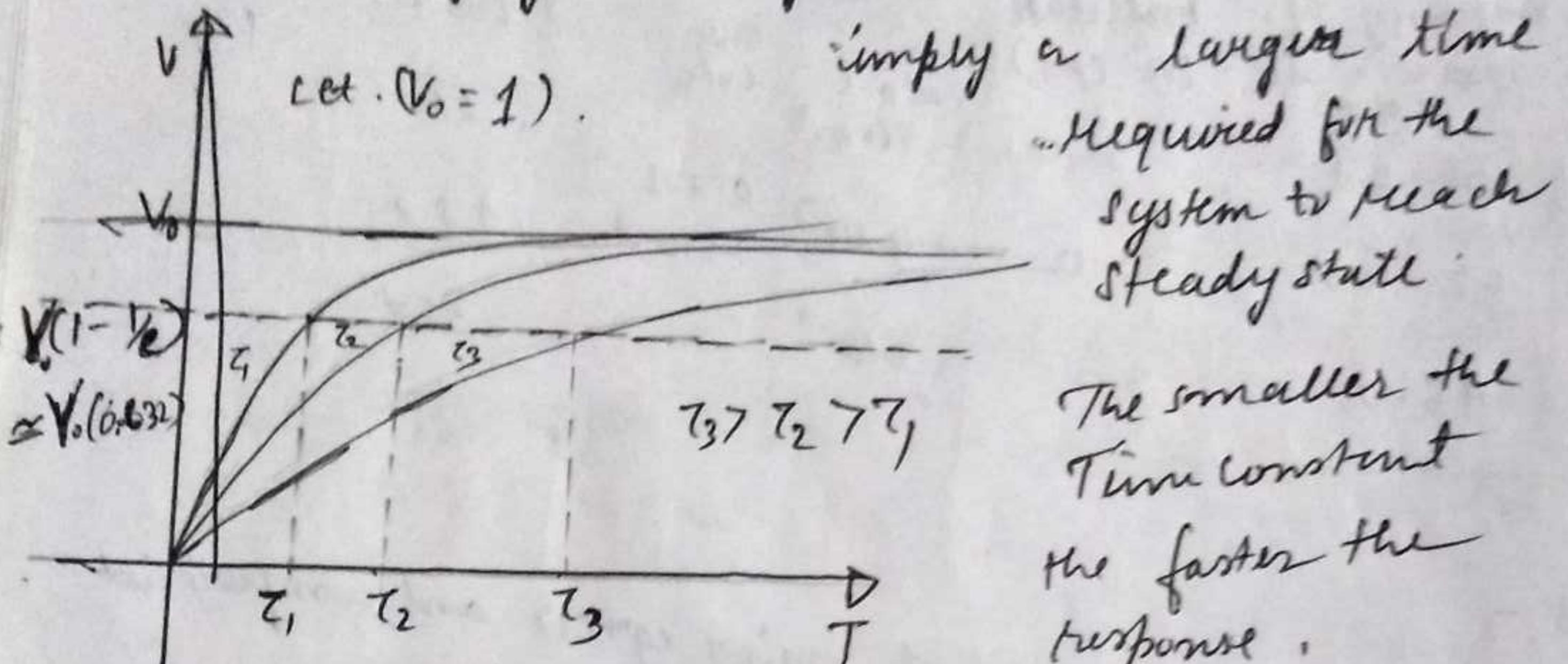while charging a larger time constant would




imply a larger time required for the system to reach steady state.

The smaller the Time constant the faster the response.

Fig - Plot of curves having different time constant for $V_0 = 1$.

Discharging:

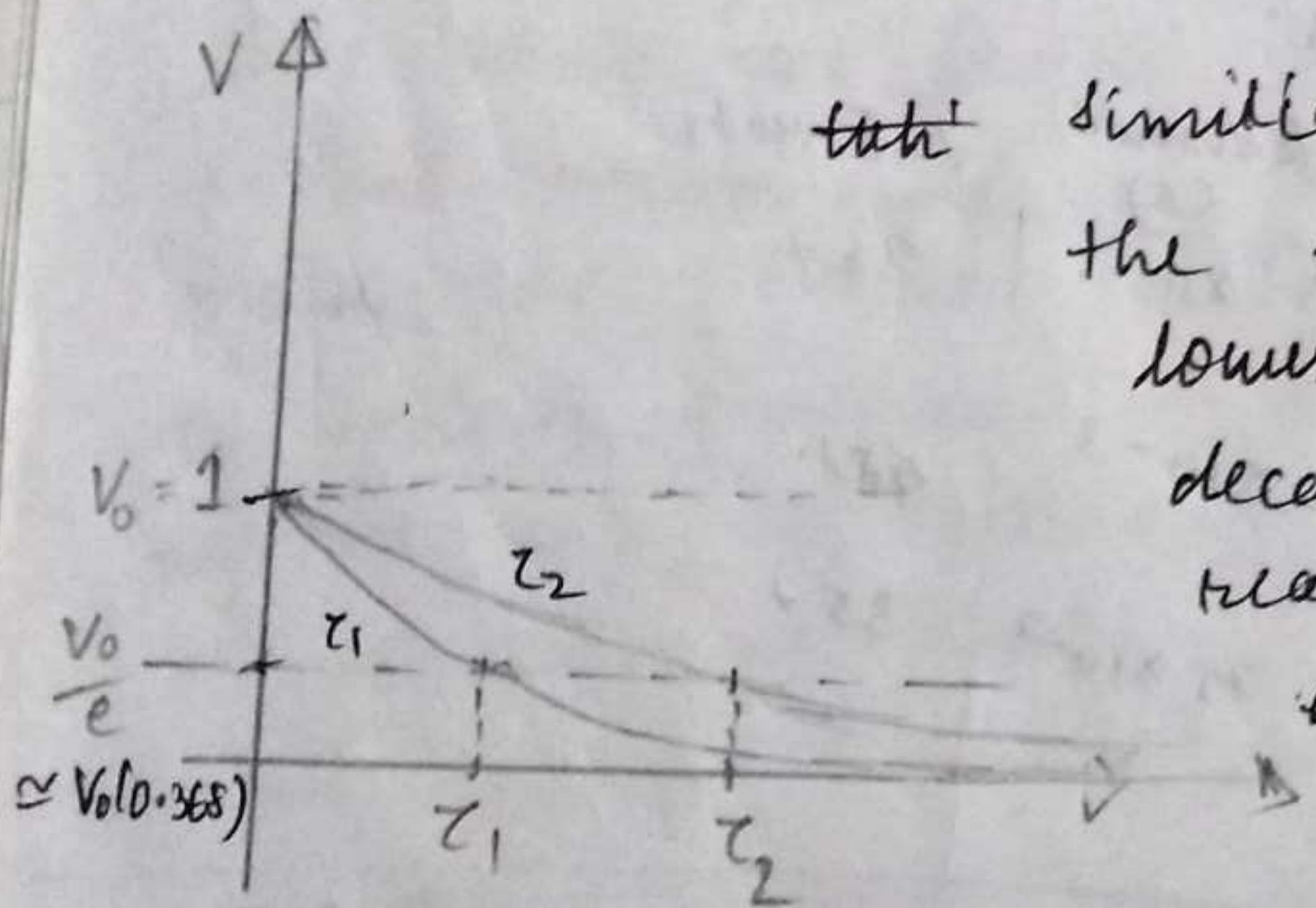

Similarly while discharging the system with lower time constant decays faster and hence reaches steady state faster and in fast thus smaller time constant implies faster response.

$$\tau_2 > \tau_1$$

Fig - Plot of Discharge for 2 different curves with different time constants

Sl. No.	Frequency of squarewave (Hz)	Amplitude v (p-p)	Time constant		% Error
			Exp calc.	Theo calc.	
1.	59.73	2.1	2.17×10^{-3}		31.5%
2.	65.85	2.1	1.97×10^{-3}	1.65×10^{-3}	19.3%
3.	50.10	2.1	2.79×10^{-3}		69%

Q) A capacitor stores charge. What do you think an inductor stores? Answer in brief.

Ans: It stores energy in the form of magnetic field which surrounds it.

Suppose an inductor of inductance L is connected to a variable DC supply. The supply is adjusted so as to increase the current i flowing through the inductor from zero to some final value I . As current through the inductor is ramped up an emf

$$dW = Pdt = -\epsilon_{idt} = iL \frac{di}{dt} dt = Lidi$$

Here $P = -\epsilon i$ as the instantaneous rate of work done by no tag.

$$\therefore W = \int_0^I Lidi = \frac{1}{2} LI^2$$


This energy is actually stored in the magnetic field generated by the current flowing through it. In a pure inductor the energy is stored without loss, and is returned to the rest of the circuit when the current through the inductor is ramped down, and its associated magnetic field collapses.

$$W = \frac{1}{2} LI^2 = \frac{\mu_0 N^2 A}{2\ell} \left(\frac{Bl}{\mu_0 N} \right)^2$$


$$= \frac{B^2}{2\mu_0}$$

Circuit Diagram

D) RC circuit

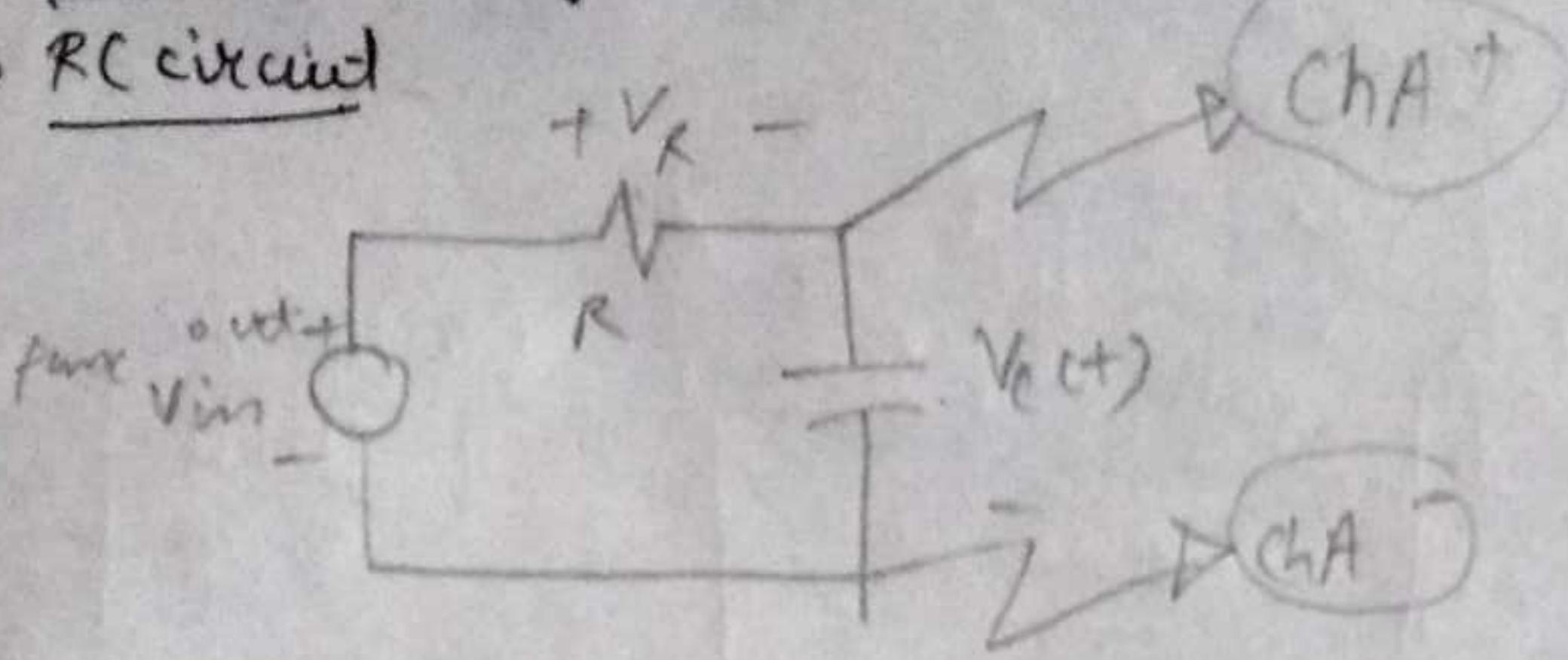


Experimental Ckt diagram

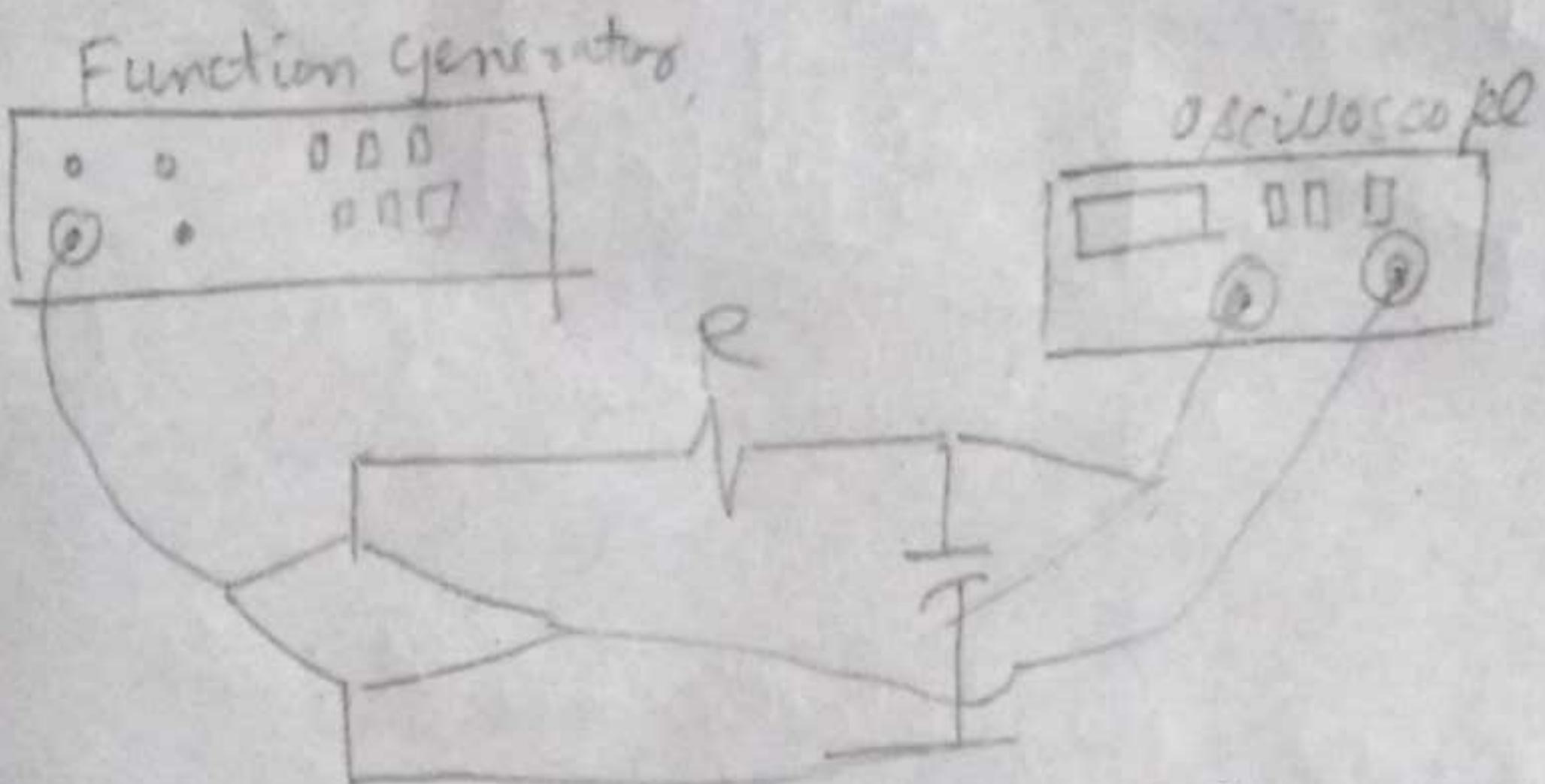


2) RL circuit

Experimental Setup

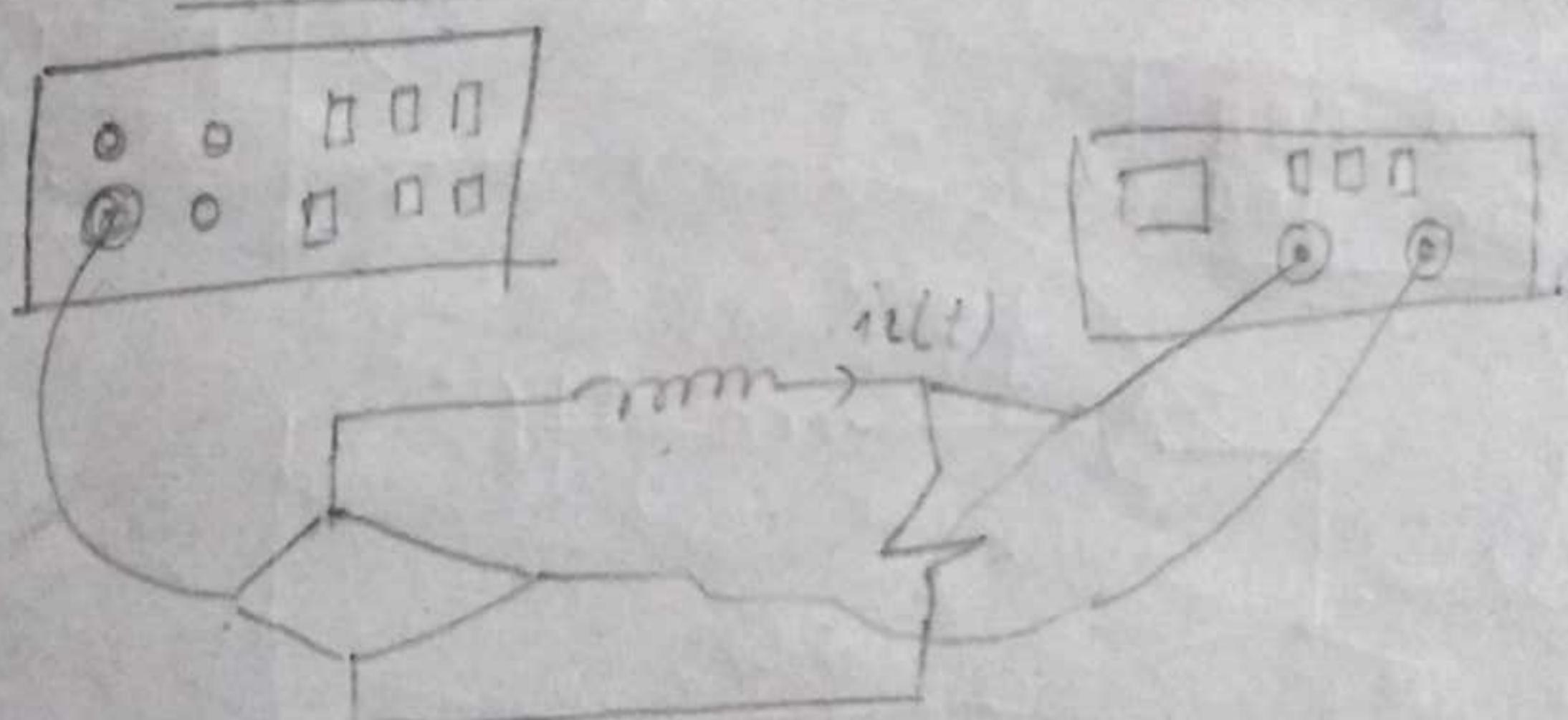

Circuit Diagram

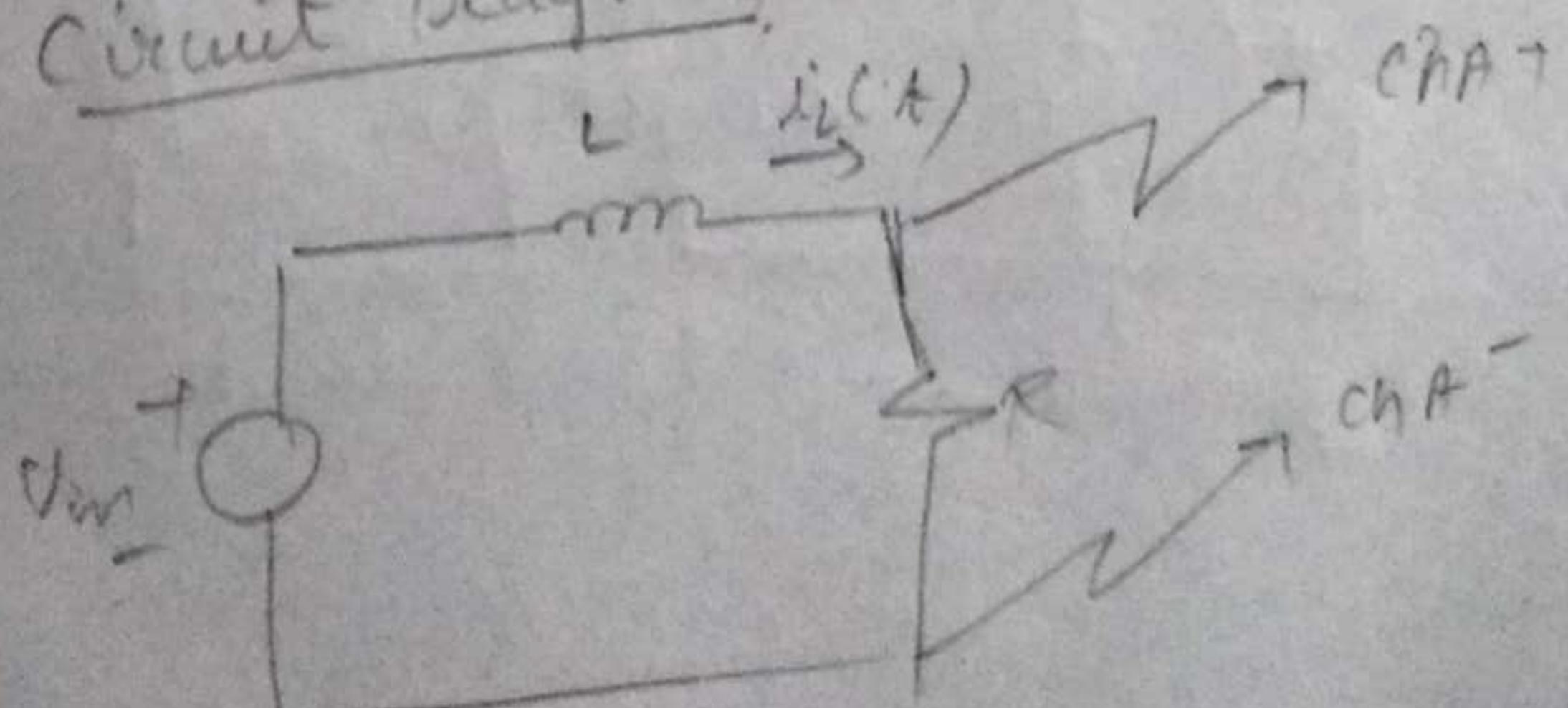

Experiment 1.

Given $R_f = 2\text{k}\Omega$, $C_1 = 1\text{MF}$, $V_p = 4V$ (peak to peak)

~~$R_2 = 10\text{k}\Omega$~~ , ~~$C_2 = 0.01\mu\text{F}$~~

Equation while charging -

$$V_C(t) = V_p(1 - e^{-t/\tau}) \quad \text{if } V_d = V_p e^{-t/C} \\ = 4(1 - e^{-500t}) \quad \text{if } V_d = 4 e^{-500t}$$


Values for the graph.

Time constant τ	Value	Voltage across capacitor (V)	Voltage constant value (discharging)	Time constant (while discharging)
0	0	0	3.990	0.012
τ	0.002	2.5284	1.4678	0.014
2τ	0.004	3.486	0.5399	0.016
3τ	0.006	3.8585	0.1986	0.018
4τ	0.008	3.9267	0.07308	0.02
5τ	0.01	3.9730	0.02688	0.022
6τ	0.012	3.9900	0.00900	0.024

$$v_c(t) = v_p(1 - e^{-\frac{t}{RC}})$$

$$-500t \quad \& \quad v_d = 4 e^{-500t}$$

Experiment - I (RC circuit)

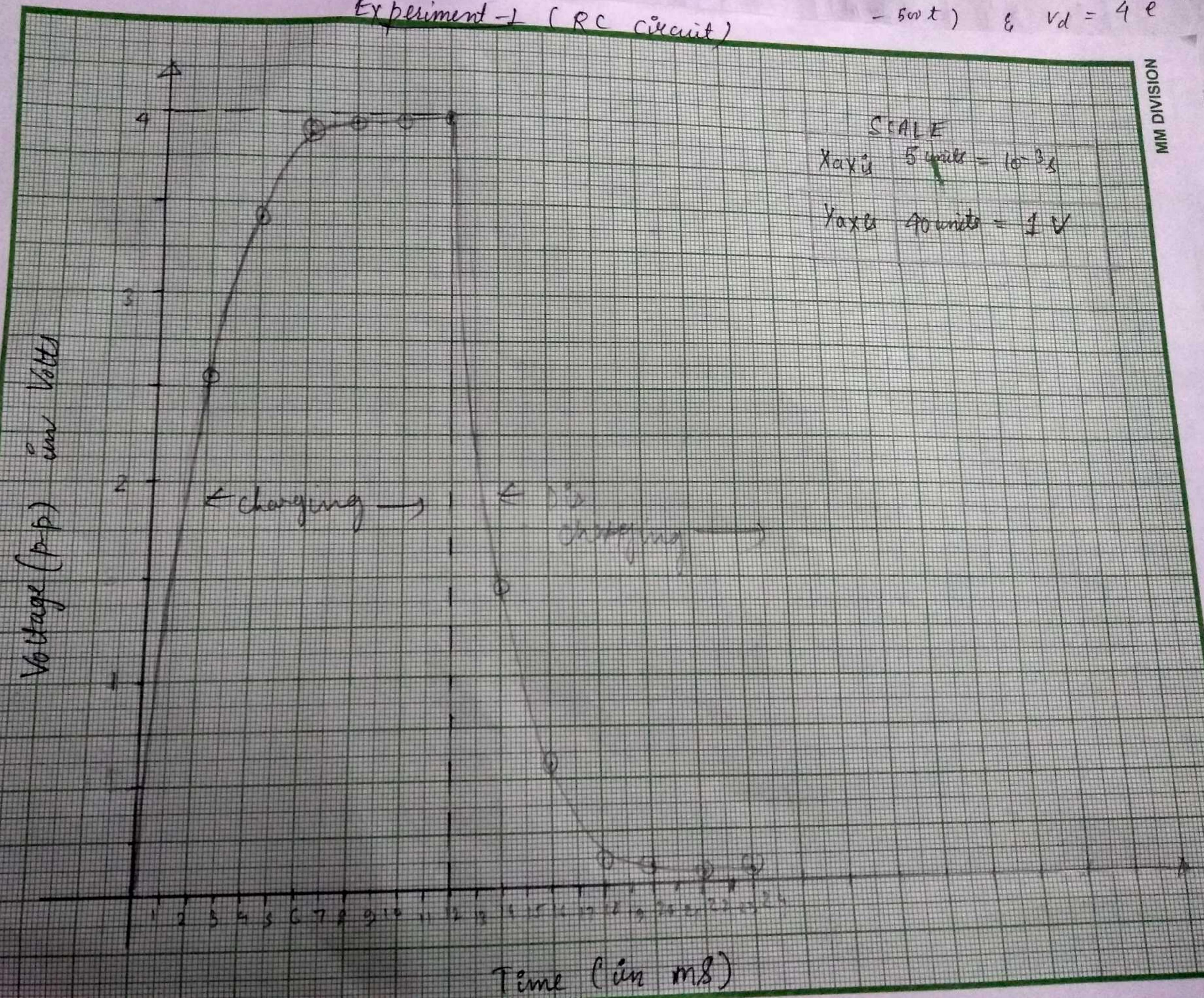

Experiment 1.

Part II : RL circuit

Expe

Obs

T

Time constant τ	Value (in s)	Current Voltage (charging) (in mA)	Value (charging) (in mA)	Value discharging (in s)	Current discharging (mA)	Supply Voltage (V)
0	0	0	0			
1	0.00015	0.00252	0.0009	0.00399		
2	0.0003	0.00345	0.00105	0.001467		
3	0.00095	0.00380	0.0012	0.005399		
4	0.0006	0.00392	0.0015	0.00019865		
5	0.00075	0.00397	0.00165	7.38 \times 10^{-5}		
6	0.0009	0.00399	0.0018	2.685 \times 10^{-5}		
				9.8904 \times 10^{-6}		

Calculation.

$$\rightarrow R = 103\Omega$$

$$\rightarrow L = 150 \text{ mH}$$

$$\rightarrow \tau_C = \frac{L}{R} = 1.5 \times 10^{-4}, V_p = 9 \text{ V} (P-P)$$

$$\therefore I_C = \frac{V_p}{R} (1 - e^{-t/\tau_C})$$

$$I_C = \frac{9}{10^3} (1 - e^{-\frac{t}{1.5 \times 10^{-4}}})$$

$$I_C = 0.004 (1 - e^{-\frac{t}{1.5 \times 10^{-4}}})$$


$$E_d = 0.004 (e^{-0.004 \cdot 10^{-4} t})$$

Windi
sid

P Min

deon

Outline Map & Graph

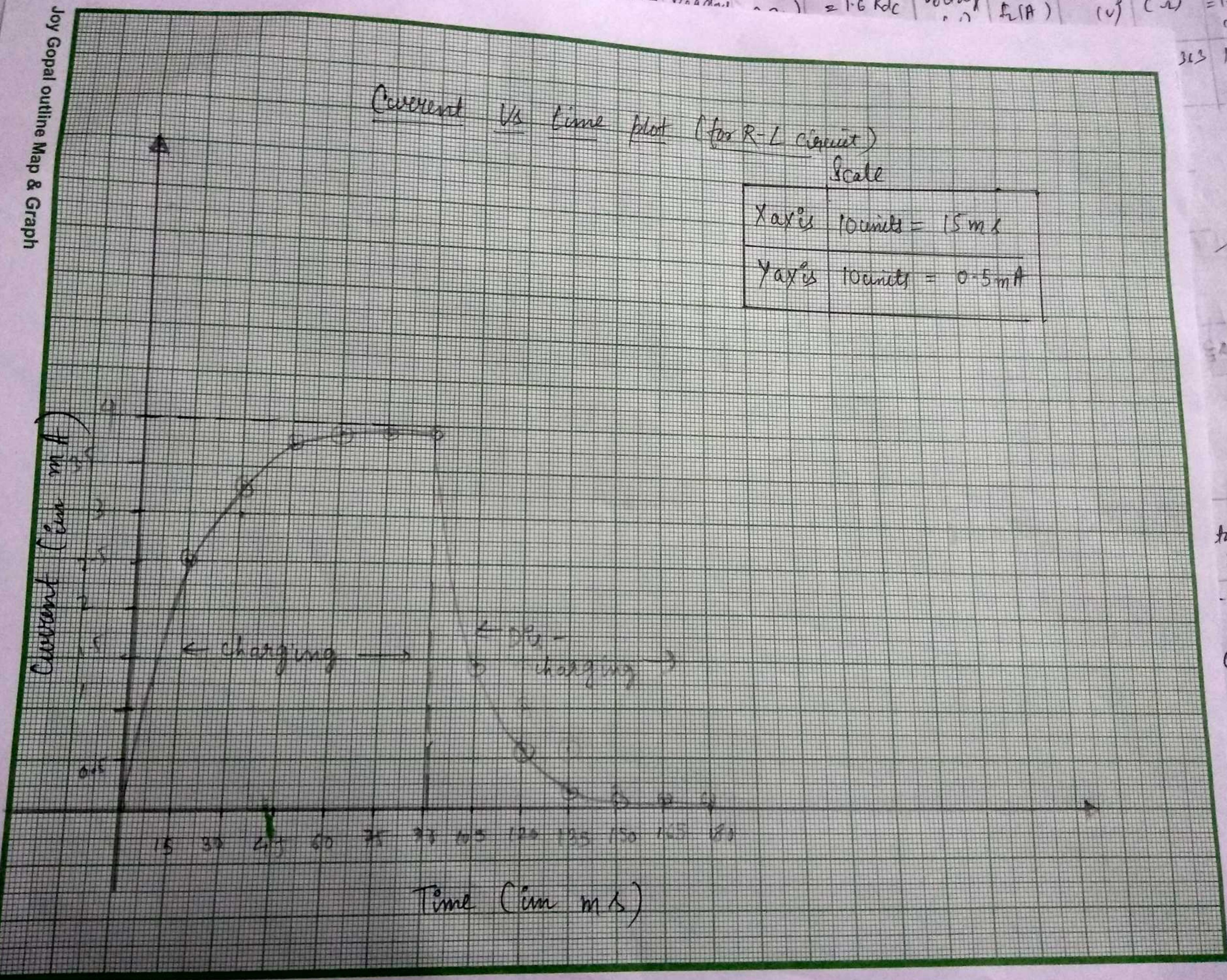

wt - 6

on Tab 4

: Determin

w

inary Wma

Votmeter Rdc

Readay (v)

C2

?

1.7

Experiment - 2

Transient Response of RLC series circuit

one
with

→ Experiment No.: EES /95)/02

→ Title: Transient Response of RLC series circuit

→ objective. To design an over-damped, under-damped and critically damped series R-L-C circuit and observe their transient response.

→ Theory.


A series RLC ckt can be modelled as a 2nd order differential equation, having solution under three condition of roots.

1) Critically damped → Roots are real & equal

2) Over damped → Roots are unequal

3) Under damped → Roots are complex conjugate pairs.

Analysis.

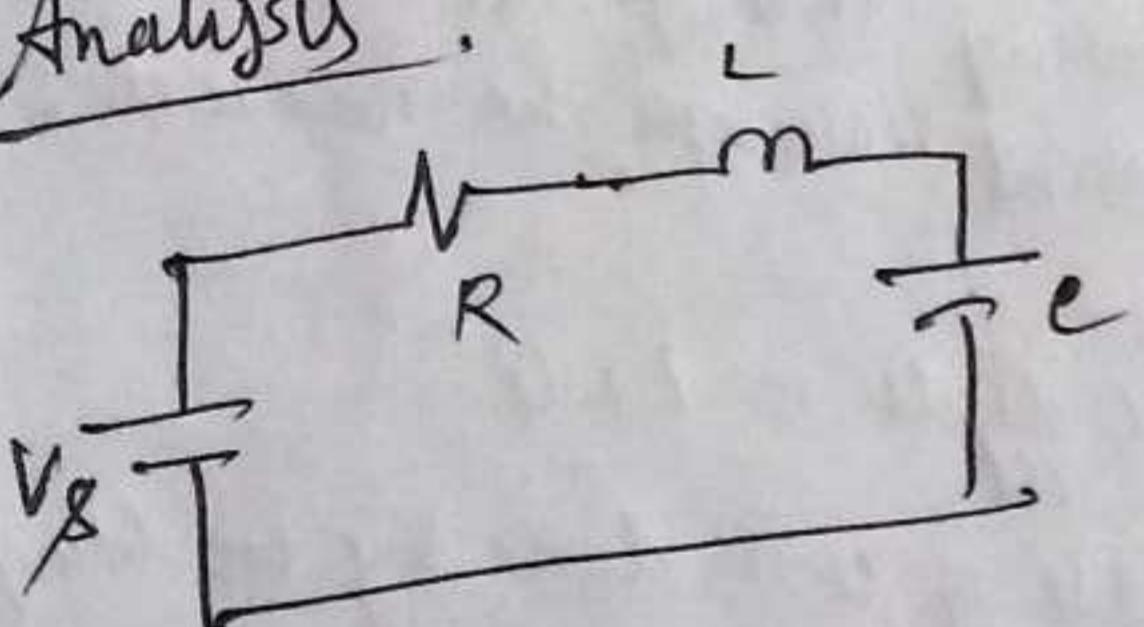

Using KVL,

$$\Rightarrow V_R + V_L + V_C = V_s \quad \dots (1)$$

The current flowing in the ckt.

$$I = C \frac{dV}{dt} \quad \dots (2)$$

$$\therefore V_R = IR = R C \frac{dV}{dt} \quad \dots (3)$$

Substituting all values in eq(1)

$$\frac{d^2V}{dt^2} + \frac{R}{L} \frac{dV}{dt} + \frac{1}{LC} V = \frac{1}{L} (V) \quad \dots (4)$$

The solⁿ is a linear combination of homogeneous & particular solution

The particular solⁿ is $V_{CP} = V_s \quad \dots (5)$

and the homogeneous eqn satisfies

$$\frac{d^2V}{dt^2} + \frac{R}{L} \frac{dV}{dt} + \frac{1}{LC} V = 0$$

Assuming the ~~solution~~^{solution is} of form $A \cdot e^{st}$ and substituting
 $\alpha = \frac{R}{2L} = \text{Damping ratio}$ -- (9) and

$$\omega_0 = \frac{1}{\sqrt{LC}} \quad \dots \text{natural frequency} \quad \text{-- (10)}$$

The characteristics eqⁿ

$$\Rightarrow s^2 + 2\alpha s + \omega_0^2 = 0$$

Its roots are

$$s_1 = -\alpha + \sqrt{\alpha^2 - \omega_0^2} \quad \text{-- (11)} \quad \text{and} \quad s_2 = -\alpha - \sqrt{\alpha^2 - \omega_0^2}$$

And the homogenous solution becomes

$$V_{ch} = A_1 e^{s_1 t} + A_2 e^{s_2 t} \quad \dots \quad \text{-- (14)}$$

The total solution now becomes

$$V_C = V_s + A_1 e^{s_1 t} + A_2 e^{s_2 t} \quad \dots \quad \text{-- (15)}$$

The parameters A_1 and A_2 are constants and can be determined by the application of initial conditions of the system.

The value of the term $\sqrt{\alpha^2 - \omega_0^2}$ determines the behaviour of the response.

1) If $\alpha = \omega_0$, then $s_1 = s_2$ and $s_1, s_2 \in \mathbb{R}$
Response is critically damped.

2) If $\alpha > \omega_0$, then $s_1, s_2 \in \mathbb{R}$,
and no oscillatory behaviour, the ct is over damped.

3) If $\alpha < \omega_0$, i.e. $\sqrt{\alpha^2 - \omega_0^2} = j\sqrt{\omega_0^2 - \alpha^2}$. In this case s_1 and s_2 are complex numbers, system exhibits complex oscillatory behaviour i.e. underdamped.

LC
pound m1

18

Experiments

Transient

Over Damped

Condition ($\alpha > \omega_0$), ~~case~~

$$V_C(t) = V_C(\infty) + A_1 e^{s_1 t} + A_2 e^{s_2 t}$$

Equating at time $t=0$, we get

$$V_C(0) = V_C(\infty) + A_1 + A_2$$

$$\text{and also, } \frac{dV_C}{dt}(0) = \frac{dL}{C} (0^+) = s_1 A_1 + s_2 A_2$$

Once s_1, s_2 are known from,

$$s_1 = -\alpha + \sqrt{\alpha^2 - \omega_0^2} \quad \& \quad s_2 = -\alpha - \sqrt{\alpha^2 - \omega_0^2}$$

A_1, A_2 can be easily found out

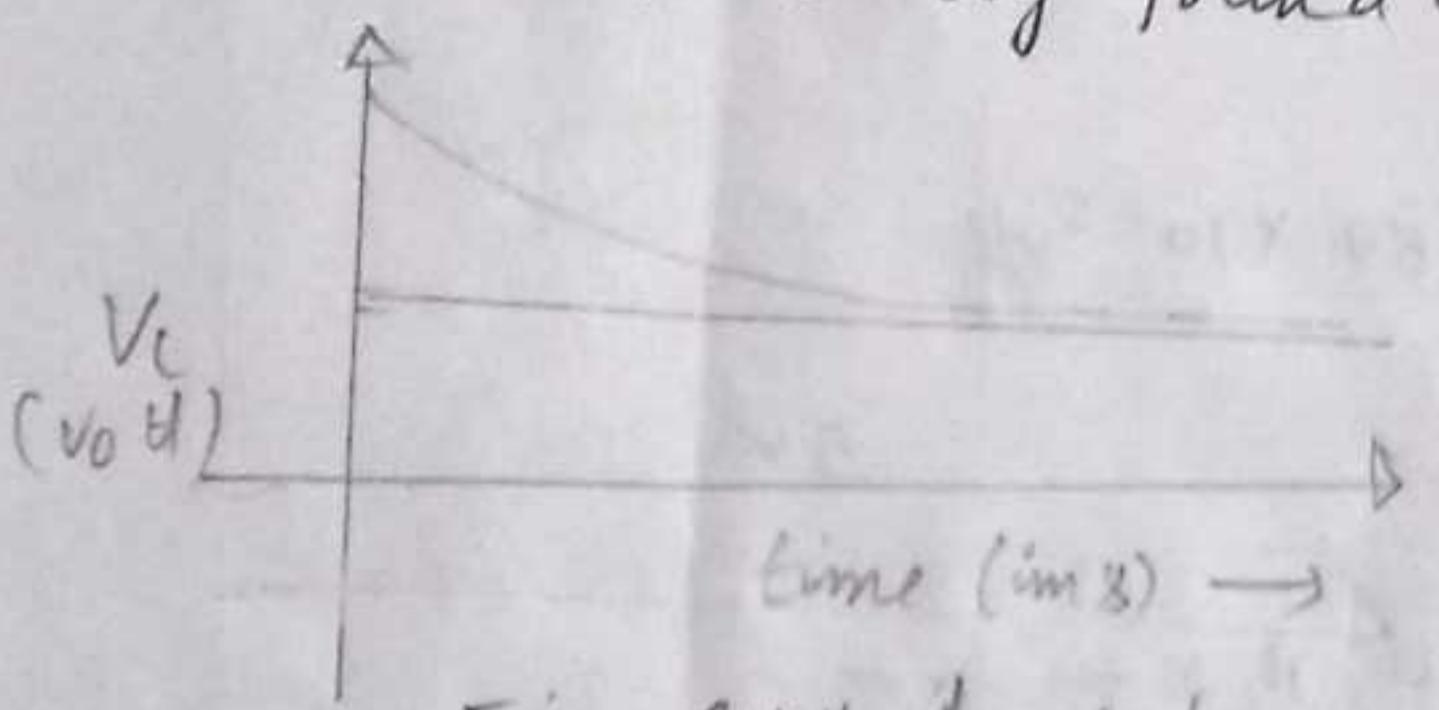


Fig - over damped

Under Damped

Condition ($\alpha < \omega_0$)

$$\text{As in Eq 7} \rightarrow V_C(t) = V_C(\infty) + (B_1 \cos \omega_d t + B_2 \sin \omega_d t) e^{-\alpha t}$$

to get B_1, B_2 we equate find the voltage at $t=0$

$$V_C(0) = V_C(\infty) + (B_1 \cos(0) + B_2 \sin(0)) e^{-\alpha(0)}$$

$$V_C(0) = V_C(\infty) + B_1 \quad \dots \quad (1)$$

from here we get B_1 now to calculate B_2 we differentiate $V_C(t)$ w.r.t time

$$\begin{aligned} \frac{dV_C}{dt}(t) &= (B_1 \cos \omega_d t + B_2 \sin \omega_d t)(-\alpha e^{-\alpha t}) \\ &\quad + (-\omega_d B_1 \sin \omega_d t + \omega_d B_2 \cos \omega_d t) e^{-\alpha t} \end{aligned}$$

Again equating at $t=0$ we get

$$\begin{aligned} \frac{dV_C}{dt}(0^+) &= \frac{dL}{C}(0^+) = (\cancel{B_1 \cos \omega_d t} + \cancel{B_2 \sin \omega_d t})(-\alpha) \\ &= R_C(B_1)(-\alpha) + \omega_d(B_2) \end{aligned}$$

Thus we calculate the values of B_1 & B_2

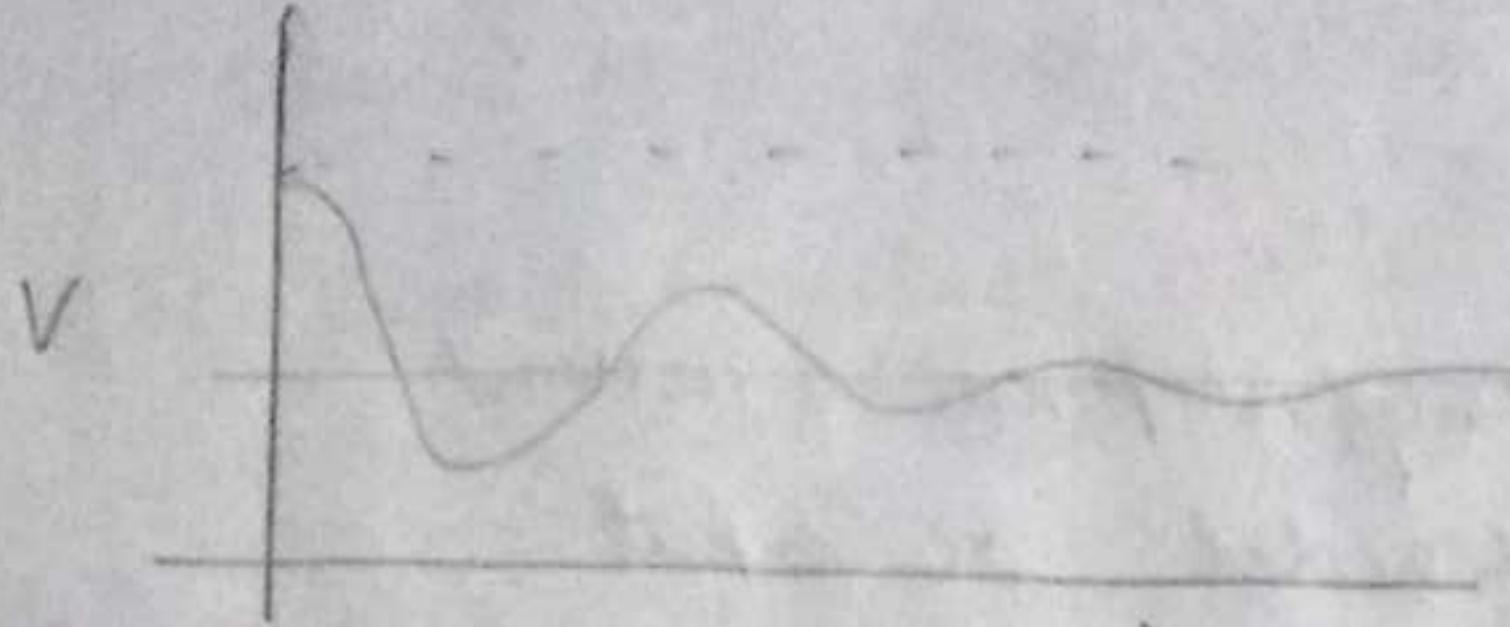


Fig - Response for Under damped ct

critically
~~over damped~~

$$V_C(t) = V_C(\infty) + (C_1 + C_2 t) e^{-\alpha t}$$

at time $t = 0$

$$V_C(0) = V_C(\infty) + [C_1 + C_2(0)] e^0$$

$$V_C(0) = V_C(\infty) + C_1$$

from here we get C_1 , and we calculate C_2 by differentiating.

$$\frac{dV_C(t)}{dt} = [C_1 + C_2(0)] (-\alpha e^0) + C_2 e^0$$

$$\frac{dV_C(0)}{dt} = C_1(-\alpha) + C_2$$

from this we get C_1, C_2

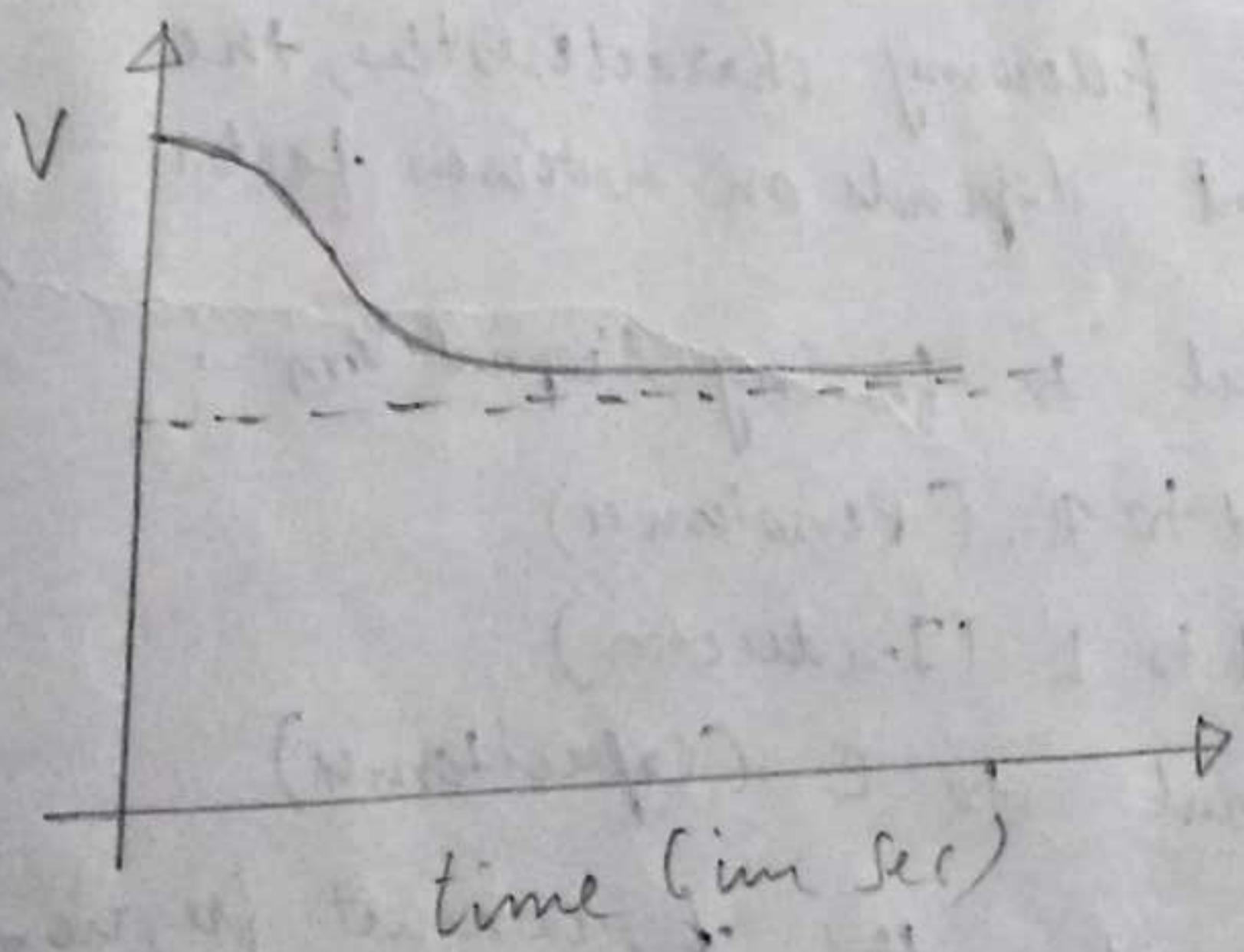


Fig: Critically Damped.

Observation Table - I

Table for reading data for overdamped RLC circuit

SL. No	quantity	Calculated Values	Measured values
1.	R	-	3180 Ω
2.	α	$\frac{3180}{2} \times 44 \times 10^{-3} = 0.036$	-
3.	ω_0	48.309×10^3	-
4.	s_1, s_2	$s_1 = 0.032$ $s_2 = -72272.68$	-
5.	$V_C(0)$	-	0V
6.	$\frac{d}{dt}[V(0)]$	$1.57 \times 10^{-5} \text{ V/s}$	-
7.	$V_C(\infty)$	-	5V
8.	A_1 and A_2	$A_1 \approx 0, A_2 \approx -5$	-
9.	Equation for $V_C(t)$		
10.	$V_C(0.03\text{ms})$	4.2V	4.4V
11.	$V_C(0.04\text{ms})$	4.8V	4.7V
12.	$V_C(0.5\text{ms})$	5V	5V

Calculations

over damped

$$\rightarrow \text{The damping factor } \alpha = \frac{R}{Lc} = \frac{3180}{2} \times 44 \times 10^{-3} = 0.036$$

$$\rightarrow \text{The undamped natural frequency } (\omega_0) = \frac{1}{\sqrt{Lc}} = 48.369 \times 10^3$$

Experiments

Transient

Analysis & Result.

1) Over Damped.

Condition ? α (damping factor) $> \omega_0$ (undamped frequency)

The voltage across capacitor in this case

$$\rightarrow V_C(t) = V_C(0) + A_1 e^{st} + A_2 e^{s_2 t}$$

We calculate A_1, A_2 , by putting $t=0$,

we get the following equation - (from the observation fig 1)

$$\Rightarrow V_C(t) = 5 + 0(e^{0.032t}) + (-5)e^{-72272.68t}$$

$$\Rightarrow V_C(t) = 5 - 5e^{-72272.68t}$$

$$\Rightarrow V_C(t) = 5(1 - e^{-72272.68t})$$

Ob-

11


10

11

12

2) Experiment - 2.

Circuit Diagram

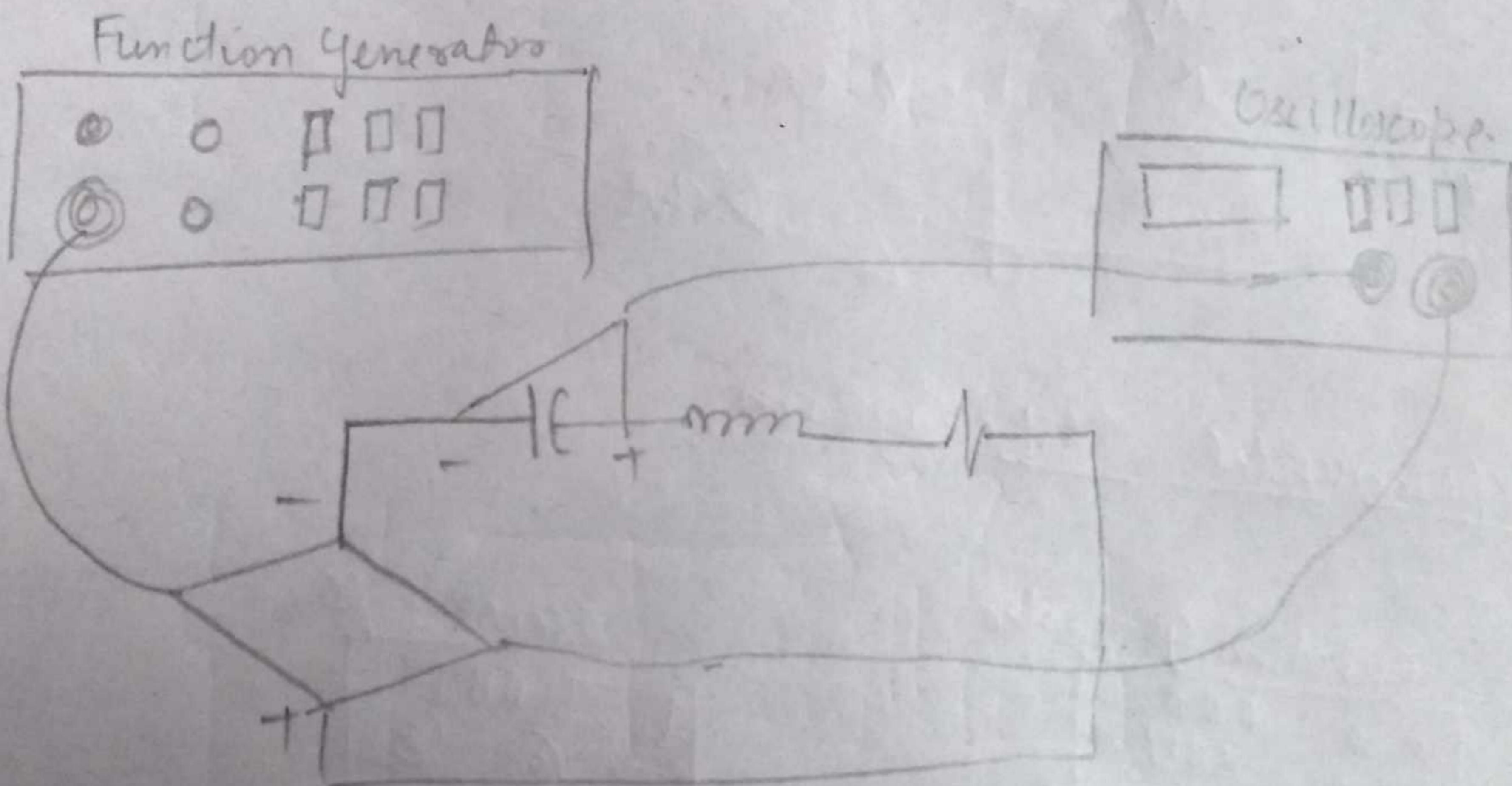

Experiment - 3

Determination of frequency response
of current in RLC circuit with
sinusoidal ac input

$$\text{one of } \frac{V_m}{R}$$

Title: Determination of frequency response of current in RLC circuit with sinusoidal ac input

Objective: To observe amplitude and phase change in an RLC circuit w.r.t. under sinusoidal forcing function

Theory: A network is in resonance when the voltage and current at the network input terminals are in phase and the input impedance of the network is purely resistive.

1) Series Resonant RLC circuit - The frequency at which where $X_L = X_C$, is called Resonant frequency (f_R)

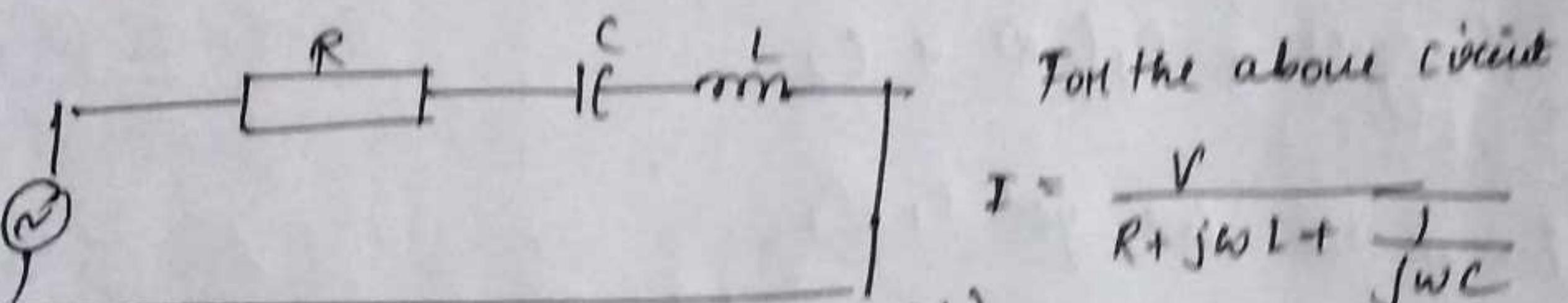


Fig-1 (series RLC circuit). 8

If $V = V_m \angle 0^\circ$, we get the following characteristics, the amplitude of current depends on various factors-

- 1) Directly proportional to forcing signal V_m ,
- 2) Inversely related to R . (Resistance)
- 3) Inversely related to L (Inductor)
- 4) Directly proportional to C (Capacitance)


In series resonant circuit, the of resonant frequency $f_R = \frac{1}{2\pi\sqrt{LC}}$, when $\omega = \frac{1}{\sqrt{LC}}$, the current will have a maximum value of $\frac{V_m}{R}$.

The phase angle of the current -

- 1) The source voltage will be leading by 90° at a frequency very close to zero. As the frequency is increased, this leading angle will start to decrease up to the point $\omega = \frac{1}{\sqrt{LC}}$ at which there will be no phase shift. As frequency is further increased, the current starts to lag and when $\omega \rightarrow \infty$, the phase angle will tend to approach 90° lagging.
- 2) A decrease in the value of R serves to increase the sharpness of the curve and compress it at the point of immersion.
- 3) A change in the value of L or C will move the point of immersion along the frequency axis.

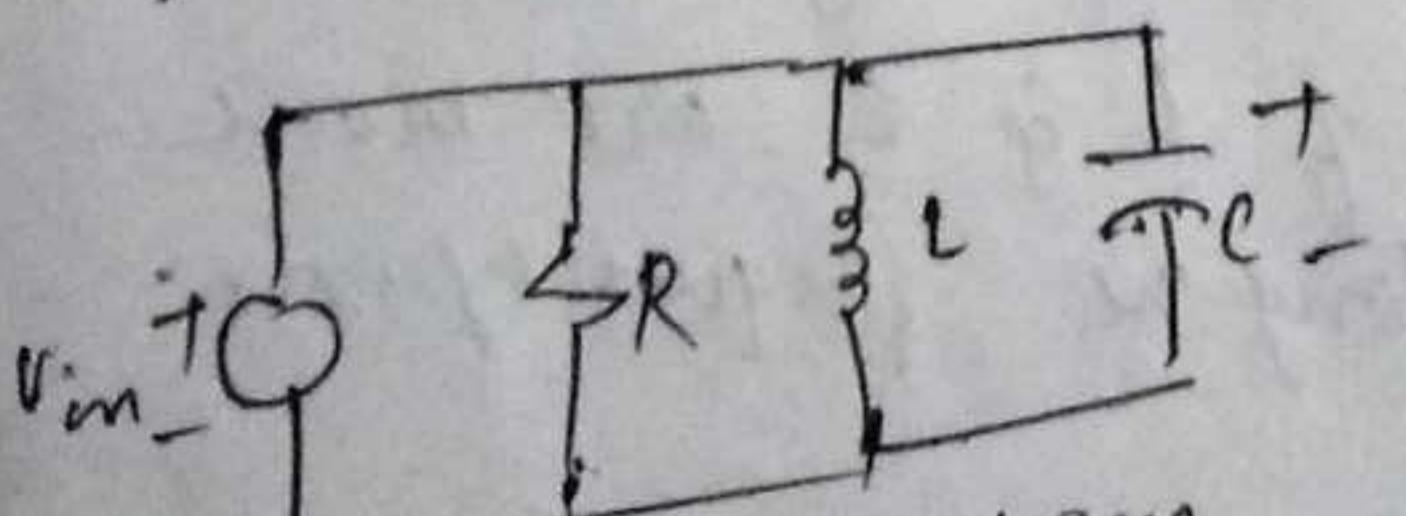2) Parallel Circuit Resonance -

- When resultant current through the parallel combination is in phase with supply voltage the circuit is said to achieve parallel resonance or anti-resonance.
- At resonance there will be a large circulating current between the inductor and capacitor due to the energy of oscillations.
- At resonance the inductor and capacitor draw zero current from the supply, as $I_C = I_L$, hence they their vector addition cancels each other. Only current flows through the resistor.



Fig' Ckt diagram

At steady state admittance,

$$Y = \frac{1}{R} + j(\omega C - \frac{1}{\omega L})$$

Resonance occurs when current and voltage are in phase, this corresponds to purely real admittance, so necessary condition $\Rightarrow \omega C = \frac{1}{\omega L} = 0 \Rightarrow \omega = \frac{1}{\sqrt{LC}}$

The forced response is in the form

$$I = \frac{1}{R} + j(\omega C + \frac{1}{j\omega L})V$$

If we let $V = V_m \angle 0^\circ$, the amplitude of current depends

- Directly proportional to amplitude of forcing signal V_m and value of capacitor.
- Inversely proportional to R and L .


For current I ,

With increase in frequency, the current starts off from a value of ~~zero~~ close to infinity upto a point where $\omega = \frac{1}{\sqrt{LC}}$ where the current will have a minimum value / amplitude of V_m , as ω is increased further the current will increase back to infinity as $\omega \rightarrow \infty$. to decrease

The phase angle of current -

At $\omega = 0$, the ~~source no~~ ^{current} will be lagging by 90° ; with increase the lagging angle will start to decrease upto a point where $\omega = \frac{1}{\sqrt{LC}}$ at which there will be no phase shift. As ω is increased further current will lead starting by 90° to lead ultimately when $\omega \rightarrow \infty$, $\phi \rightarrow 90^\circ$ leading

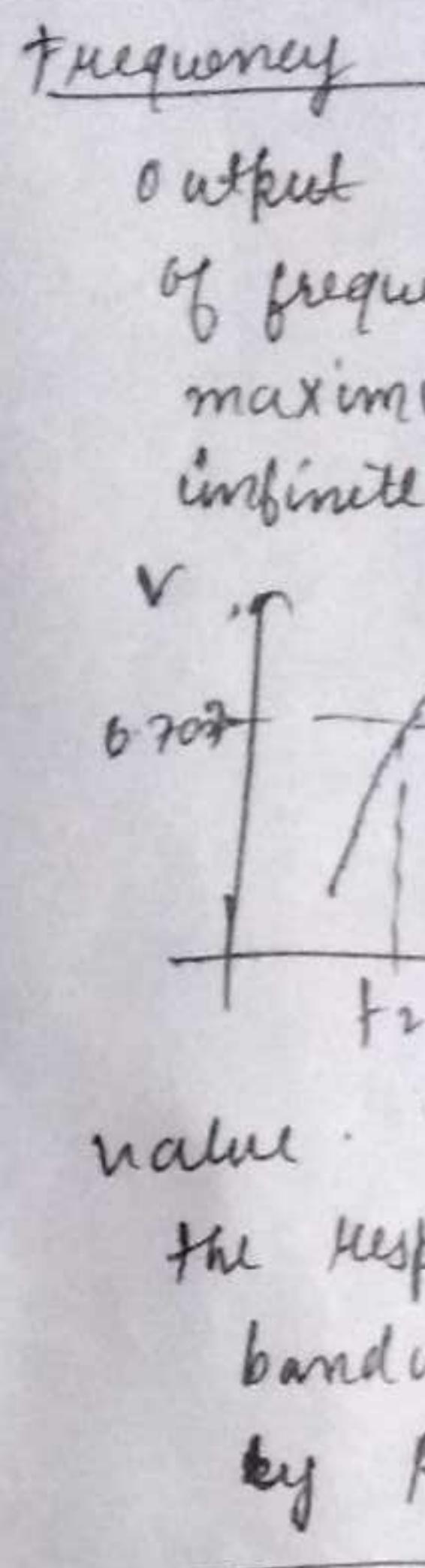
- A decrease in R , serves to decrease the sharpness of curve and expands the pt. of inversion.
- A change in the value of L & C will move the pt. of inversion along the frequency axis.



Sl. No.
1.
2.
3.
4.
5.
6.
7.
8.
9.
10.
11.

Experiment - 3

Circuit Diagram

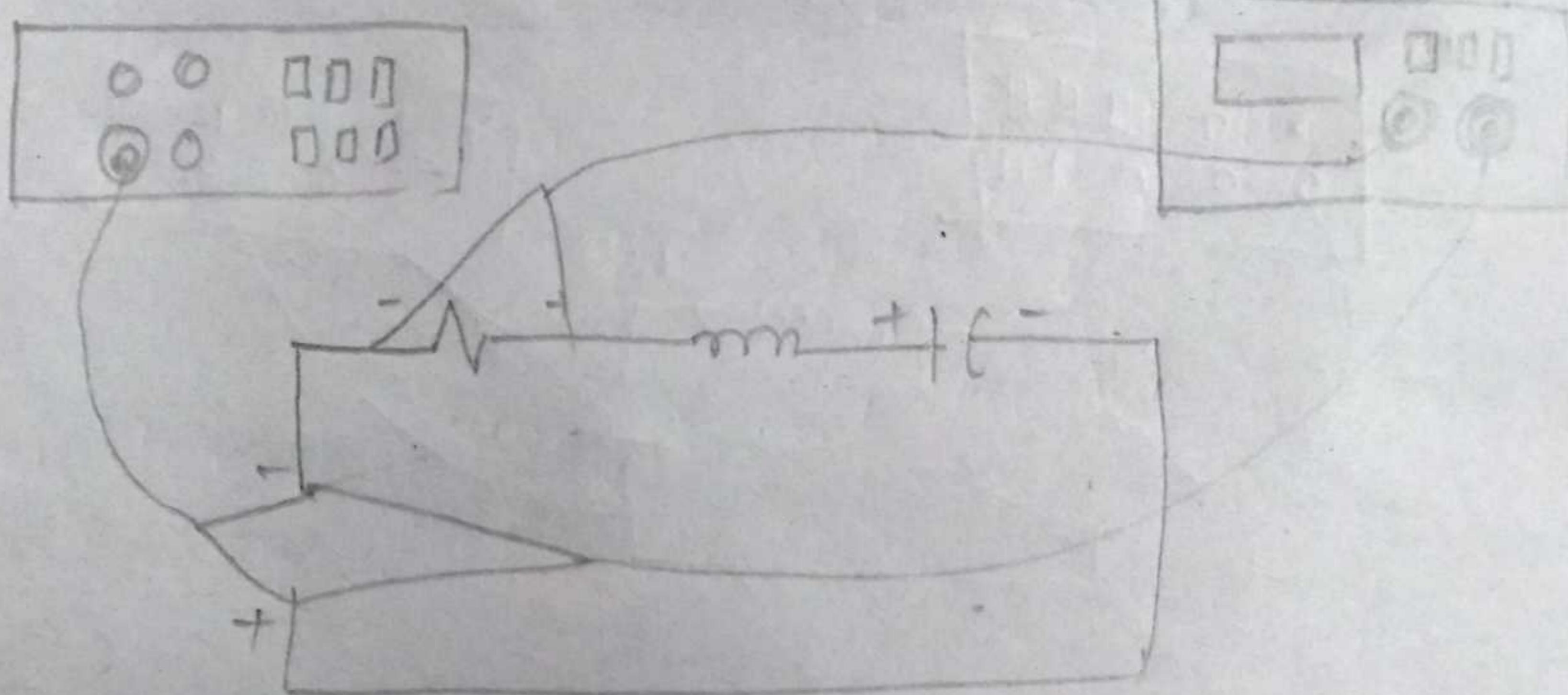


Exp

Circu

D Pe



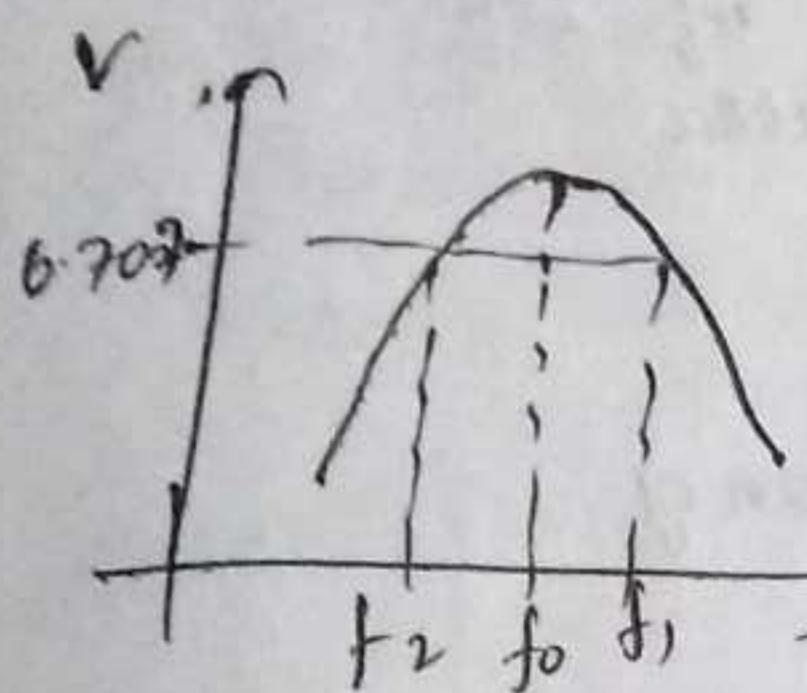Frequency Response - Plot of magnitude of the output voltage of a resonant circuit as a function of frequency. The curve starts at zero reaches a maximum and again drops to zero as ω becomes infinite.



The frequencies f_1 and f_2 are called half power frequencies. They locate at those points on the curve at which voltage response is $\frac{1}{\sqrt{2}}$ or 0.707 times the maximum value. They are used to measure the band width of the response curve. They are called half power frequency band width of the resonant curve and is denoted by $B = f_2 - f_1$.

lock
made in 1

Observations table (Series Resonance)

Sl. No.	Frequency (Hz)	Voltage drop across R (VR) (V)	Current (A)
1.	5	1.12	9.86×10^{-4}
2.	10	1.23	1.683×10^{-3}
3.	15.4	1.37	1.207×10^{-3}
4.	22	1.51	1.321×10^{-3}
5.	31.47	1.53	1.348×10^{-3}
6.	45	1.25	1.101×10^{-3}
7.	57.8	1.04	9.162×10^{-4}
8.	61.4	0.88	7.753×10^{-4}
9.	69.08	0.80	7.048×10^{-4}
10.	80.05	0.65	5.726×10^{-4}
11.	89.07	0.58	5.11×10^{-4}

w) 8
eaf ↵

" 1. Function of ...
and nature of capacitor
infinite sum again drop to zero

Time

is finite

at those

which

0.707 t


we the be

used half


use and

The

Current (in 10^4 A)

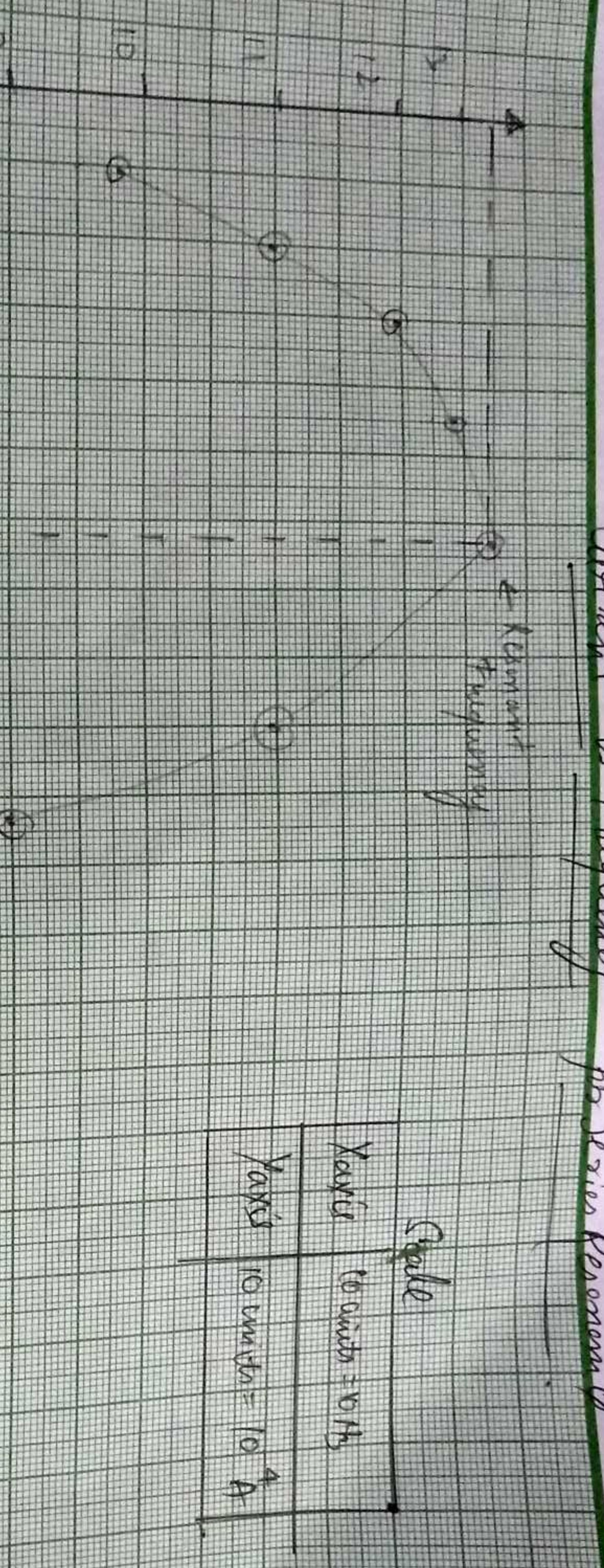

frequency (in Hz)

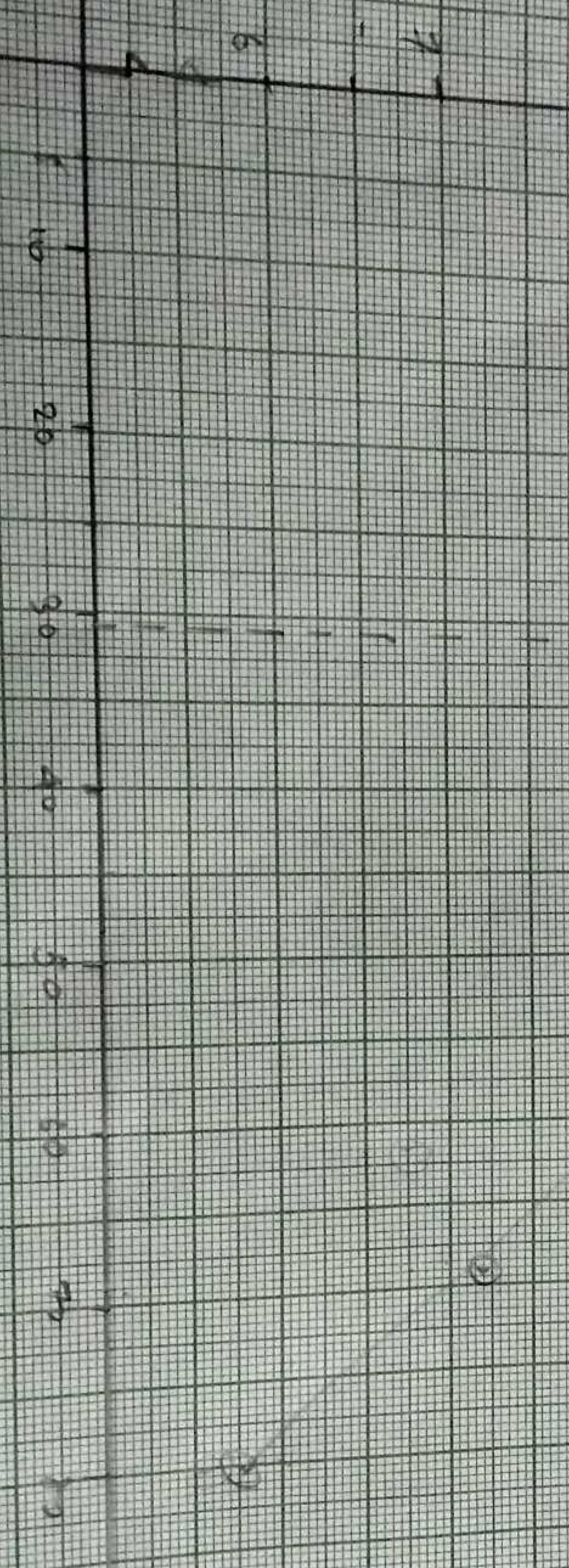

Joy Gopal outline Map & Graph

a)
across
(V)

EXP 3

Table - II :


For parallel circuit -

Sl. No.	Frequency (Hz)	Voltage drop across R (V_R) (V)	Current (mA)
1.	0.605	0.3	0.264×10^{-3}
2.	0.86	0.4	0.352×10^{-3}
3.	5.49	1.0	0.88×10^{-3}
4.	15	1.5	1.32×10^{-3}
5.	25	1.7	1.49×10^{-3}
6.	33.177	1.9	1.67×10^{-3}
7.	40	1.5	1.32×10^{-3}
8.	62.316	1.4	1.23×10^{-3}
9.	80.083	1.2	1.057×10^{-3}
10.	100.43	1.0	0.88×10^{-3}
11.	126.90	0.8	0.748×10^{-3}

Table - III

Summary of the experiment performed.

Sl. No.	Parameters	Series Resonance		Parallel Resonance	
		Theoretical	Practical	Theoretical	Practical
1.	Resonant frequency	50.34 Hz	31.97 Hz	50.32 kHz	33.14 kHz
2.	Bandwidth	181.607 kHz	45.6 kHz	14.02 kHz	54.4 kHz
3.	Q-factor	0.278 kHz	0.176 kHz	3.589 kHz	5.44 kHz

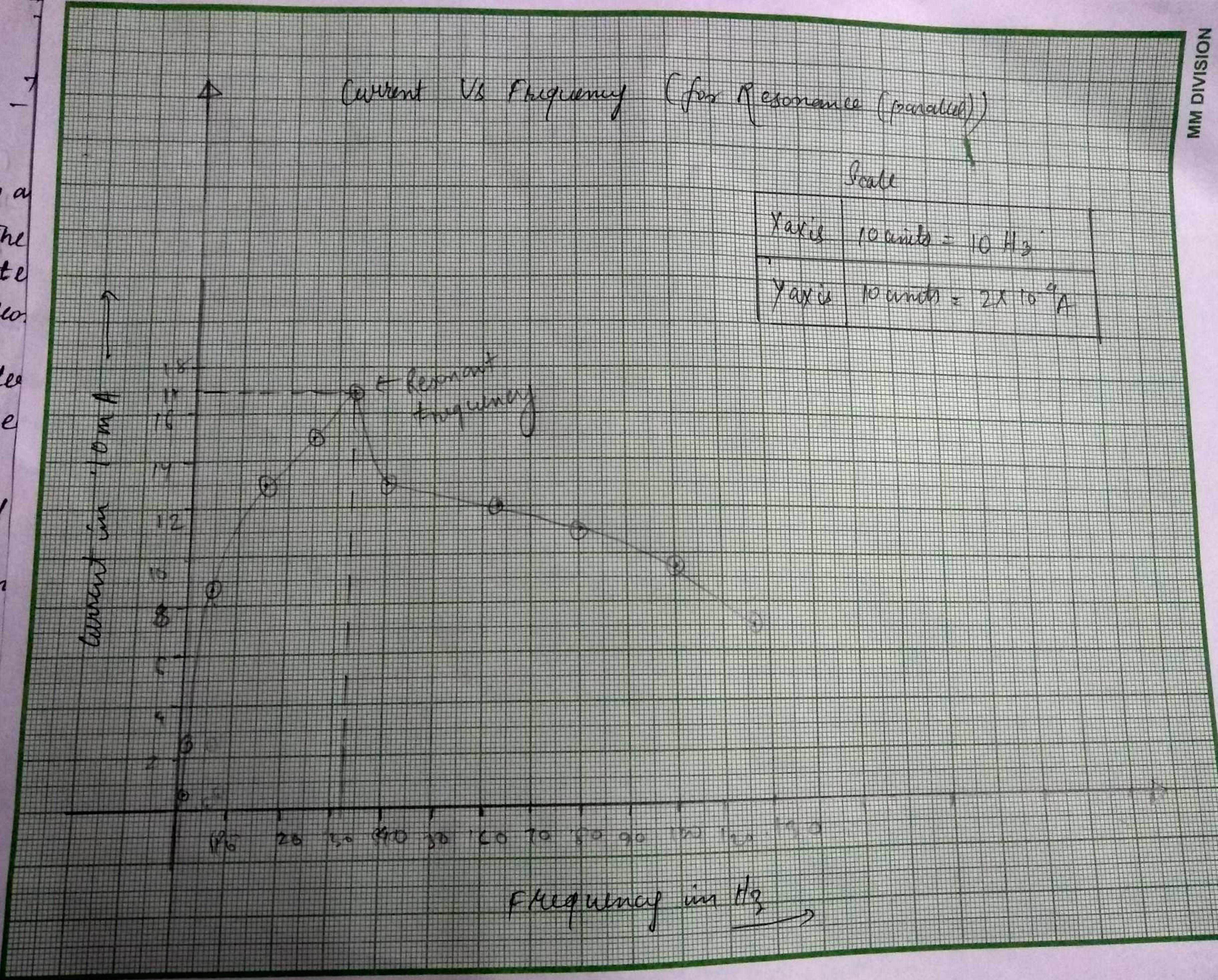

Experiment - 4

Determination of Frequency Response of
low pass and High pass passive filters

Experiment - 5

Title: Determination of frequency response of a low pass and high pass passive filters.

Objectives - Study the characteristics of passive filters by obtaining the frequency response of low pass RC filter and High pass RL filter.

Theory:

- The impedance of the inductor \propto frequency
- the impedance of capacitor \propto frequency.
- These characteristics can be used to select and reject a particular frequency. The selection and rejection of frequency is called filtering the corresponding LC in the filter circuit.
- High pass - passes high frequency and rejects low frequency.
- Low pass - passes low frequency and rejects high frequency.
- A frequency is considered passed if magnitude within $f_0 \pm (\text{or } \frac{1}{f_2})$ of maximum ~~frequency~~ amplitude or rejected otherwise.
- The $f_0 \pm$ frequency is called corner frequency, roll off frequency or half power frequency.

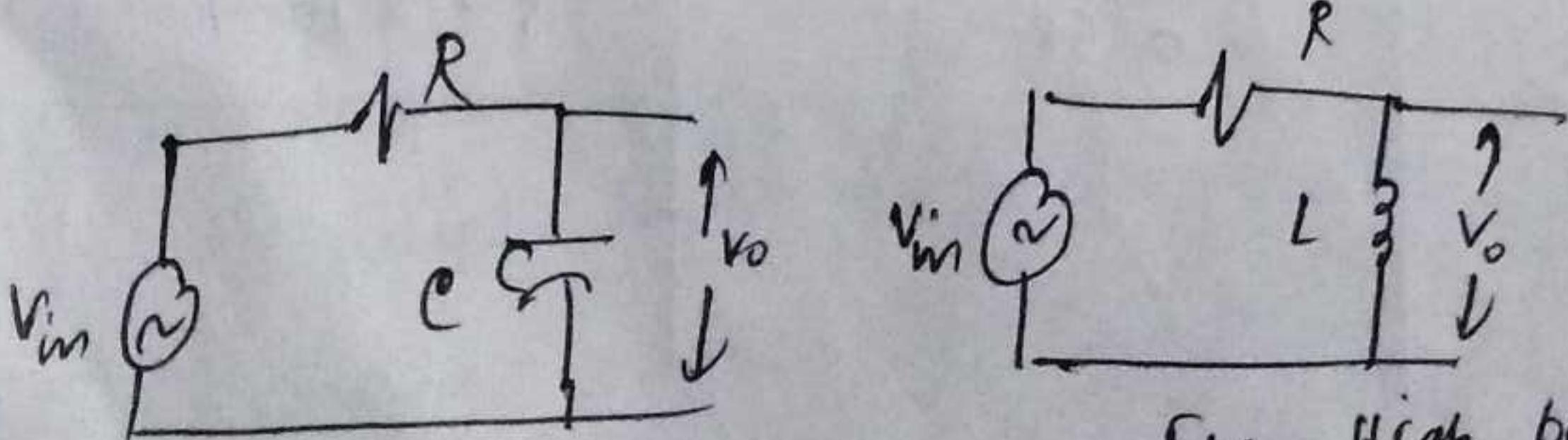


Fig - Low pass RLC filter.

Fig - High pass RL filter

Frequency
of the
It is g
frequen
operati
magnitude


V_o

Observation
Frequenc

For RC filter,

$$f_c = \frac{1}{2\pi R C} \quad \text{and for RL filter } f_c = \frac{R}{2\pi L}$$

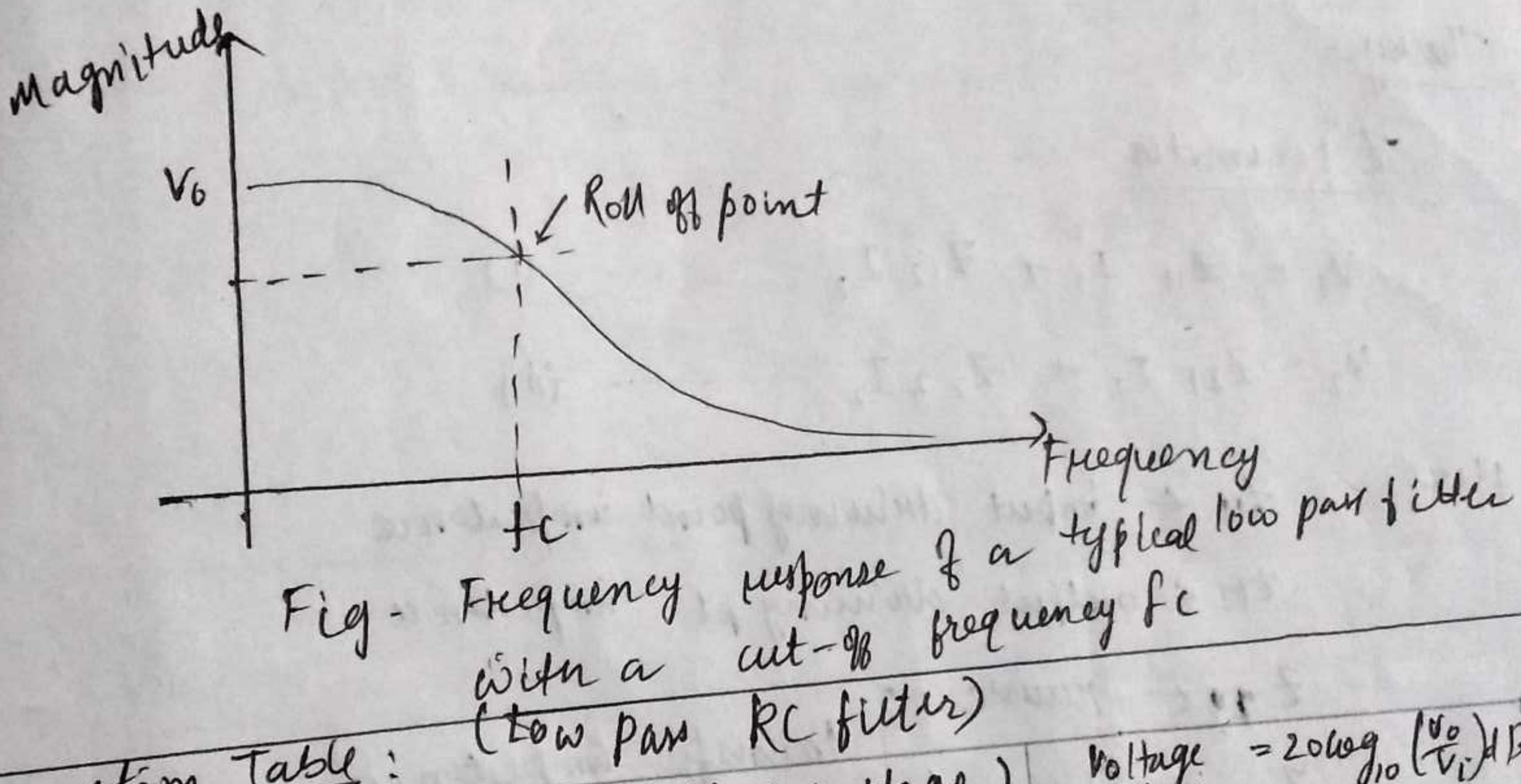Frequency Response - It is the graph of magnitude of the output voltage as a function of the frequency. It is generally used to characterize the range of frequencies in which the filter is designed to operate within.



Observation Table :

Frequency (Hz)	V_o (Output Voltage)	Voltage gain = $20 \log_{10} \left(\frac{V_o}{V_i} \right) \text{dB}$
28.1	4.32	-1.1
34.3	4.29	-1.31
40.1	4.08	-1.61
49.8	3.92	-1.93
57.2	3.84	-2.12
54.4	3.76	-2.38
56.6	3.68	-2.48
63.3	3.60	-2.68
65.0	3.44	-3.09
72.1	3.2	-3.79
79.6	3.2	-3.72
80.0	3.12	-3.93
	3.12	-3.93
	3.12	-4.03
	3.12	-4.15

Exp- 9.

Table 1 for Closé pair R.C filter.)

Sl. No.	Frequency (Hz)	No (output voltage)	Voltage gain $= 20 \log_{10} \left(\frac{V_o}{V_i} \right) (\text{dB})$
1.	28.1	9.32	-1.1
2.	34.3	9.29	-1.31
3.	40.1	9.08	-1.61
4.	46.8	3.92	-1.93
5.	51.2	3.84	-2.12
6.	54.4	3.76	-2.38
7.	56.6	3.68	-2.48
8.	63.3	3.60	-2.68
9.	65.0	3.52	-2.8
10.	72.1	3.44	-3.07
11.	79.6	3.2	-3.74
12.	80.0	3.12	-3.93
13.	81.1	3.12	-3.93
14.	82.0	3.12	-3.93
15.	84.9	3.04	-4.152
16.	89.0	2.96	-4.43
17.	90.6	2.87	-4.62
18.	95.5	2.64	-4.88
19.	98.3	2.56	-5.51
20.	110.6	2.48	-5.6


Table 2:

For High pass RL filter -


Frequency (Hz)	V_o (Output Voltage)	$\text{Voltage Gain} = 20 \log\left(\frac{V_o}{V_{in}}\right)$
47.9	2.40	-6.37
50.2	2.44	-6.79
52.8	2.56	-5.67
55.3	2.64	-5.38
57.0	2.68	-5.35
58.08	2.72	-5.19
61.90	2.88	-4.73
68.0	2.96	-4.37
70.2	3.00	-4.25
72.5	3.08	-4.01
75.6	3.12	-3.74
79.6	3.20	-3.4
81.7	3.28	-3.22
90.1	3.90	-3.09
91.1	3.44	-2.97
97.6	3.52	-2.85
100.9	3.56	-2.68
104.2	3.60	-2.59
107.6	3.64	-2.48
109.8	3.68	-2.3
116	3.76	-2.27
122	3.80	

Experiment - 9

1) Circuit pass filter (RC)

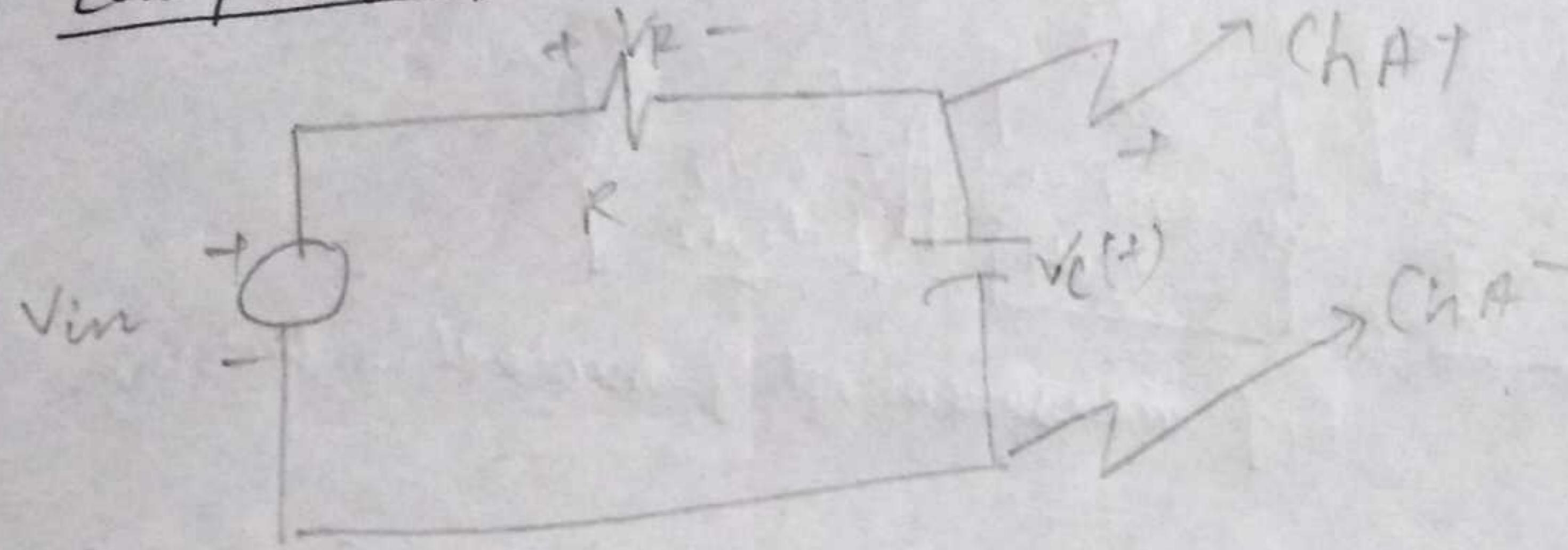

2) High pass Filter (RL)

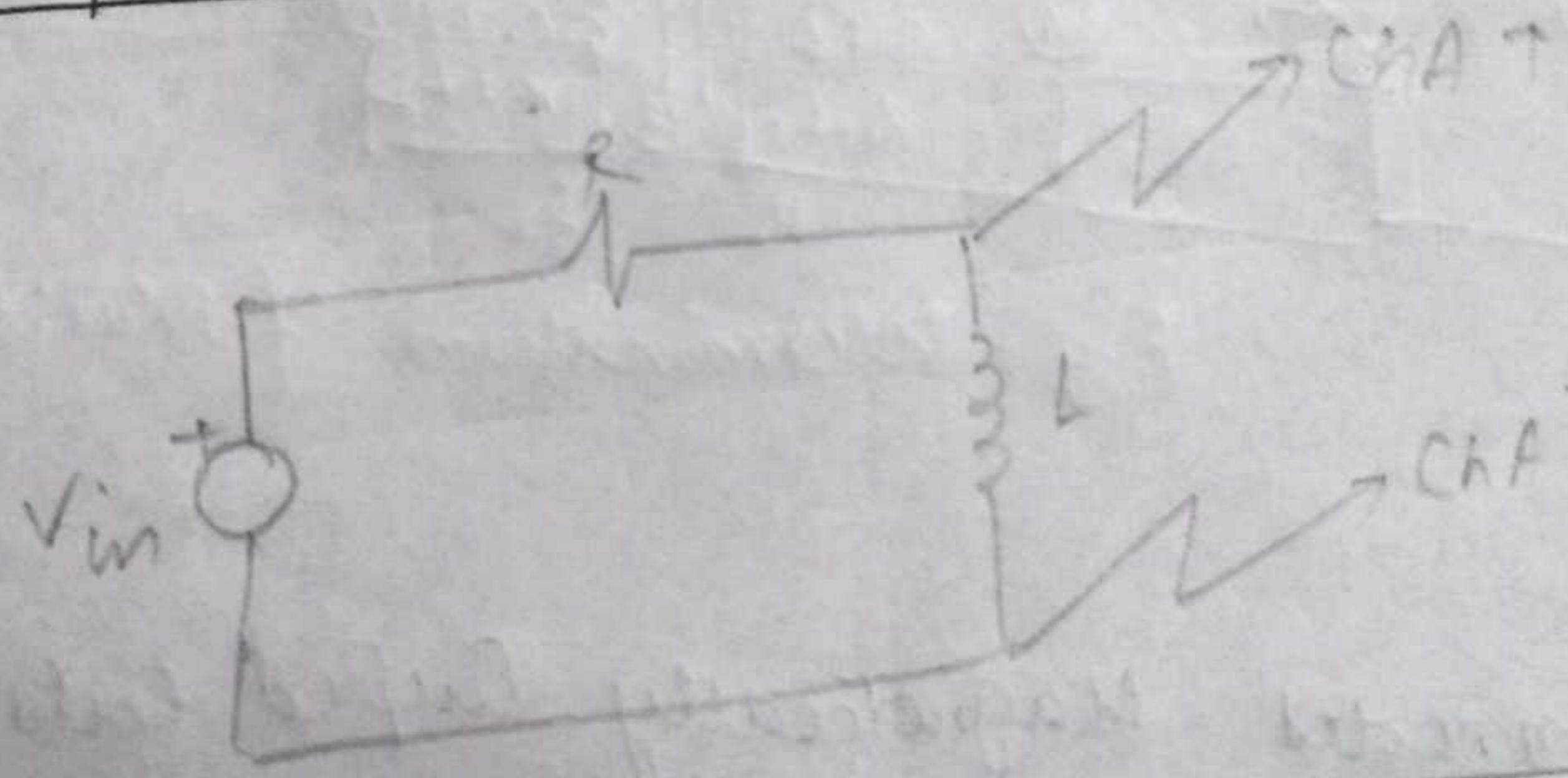


Experiment - 5

~~Ques = RE 909.09 (from 9)~~

Bode plot Calculation

1) RC circuit

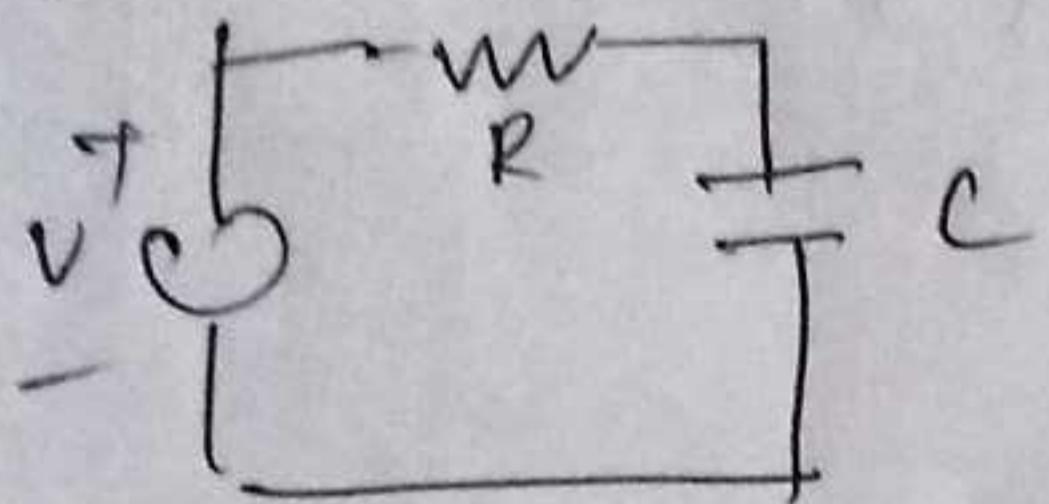

Transfer Function:


$$= \frac{V_C}{V_C + V_R} = \left(\frac{X_C}{X_C + R} \right) V$$

~~$= \frac{K(s) \left(\frac{1}{Cs} \right)}{\left(\frac{1}{Cs} + K \right)}$~~

$$= \frac{1}{1 + RCs}$$

$$= \frac{1}{1 + 0.0011s} \approx \frac{1}{1 + \frac{s}{909.09}}$$

2) RL circuit

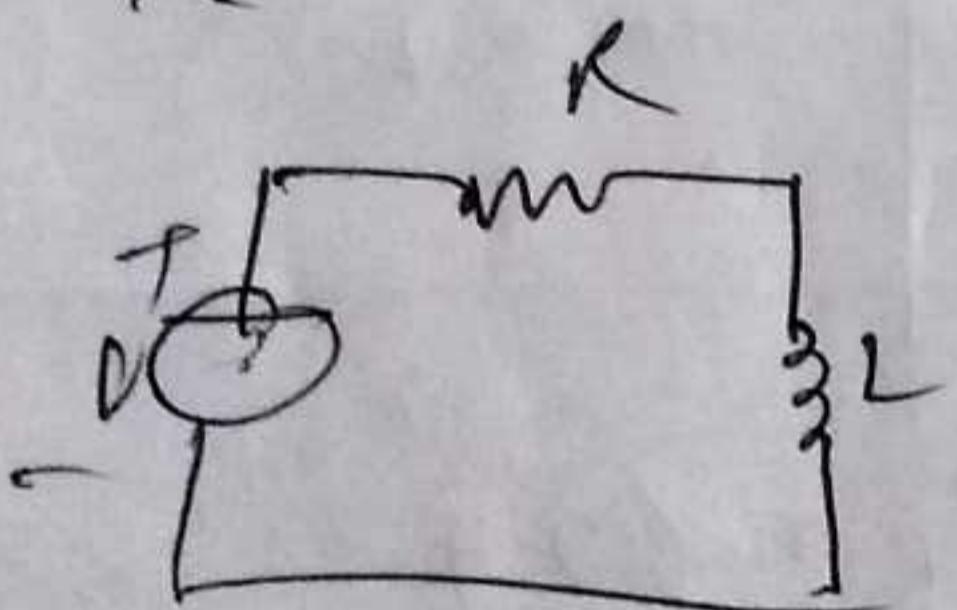

Transfer Function $= \frac{V_L}{V_L + R} = \left(\frac{X_L}{X_L + R} \right) V$

$$= \frac{Es}{Ls + R} = \frac{s}{s + (R/L)}$$

~~$= \frac{(s) \times 3 \times 10^5}{\left(1 + \frac{s}{3 \cdot 3 \times 10^4} \right)}$~~

Cut off frequency

at 0dB frequency

$$\omega = \frac{1}{RC} = \frac{1}{909.09}$$

(from)

$$\omega = \frac{1}{RC}$$

EEWeb

TITLE	Bode plot of RC circuit
NAME	Sayan Mondal
DATE	5/07/21

Bode


circuit

5

L C

m

2

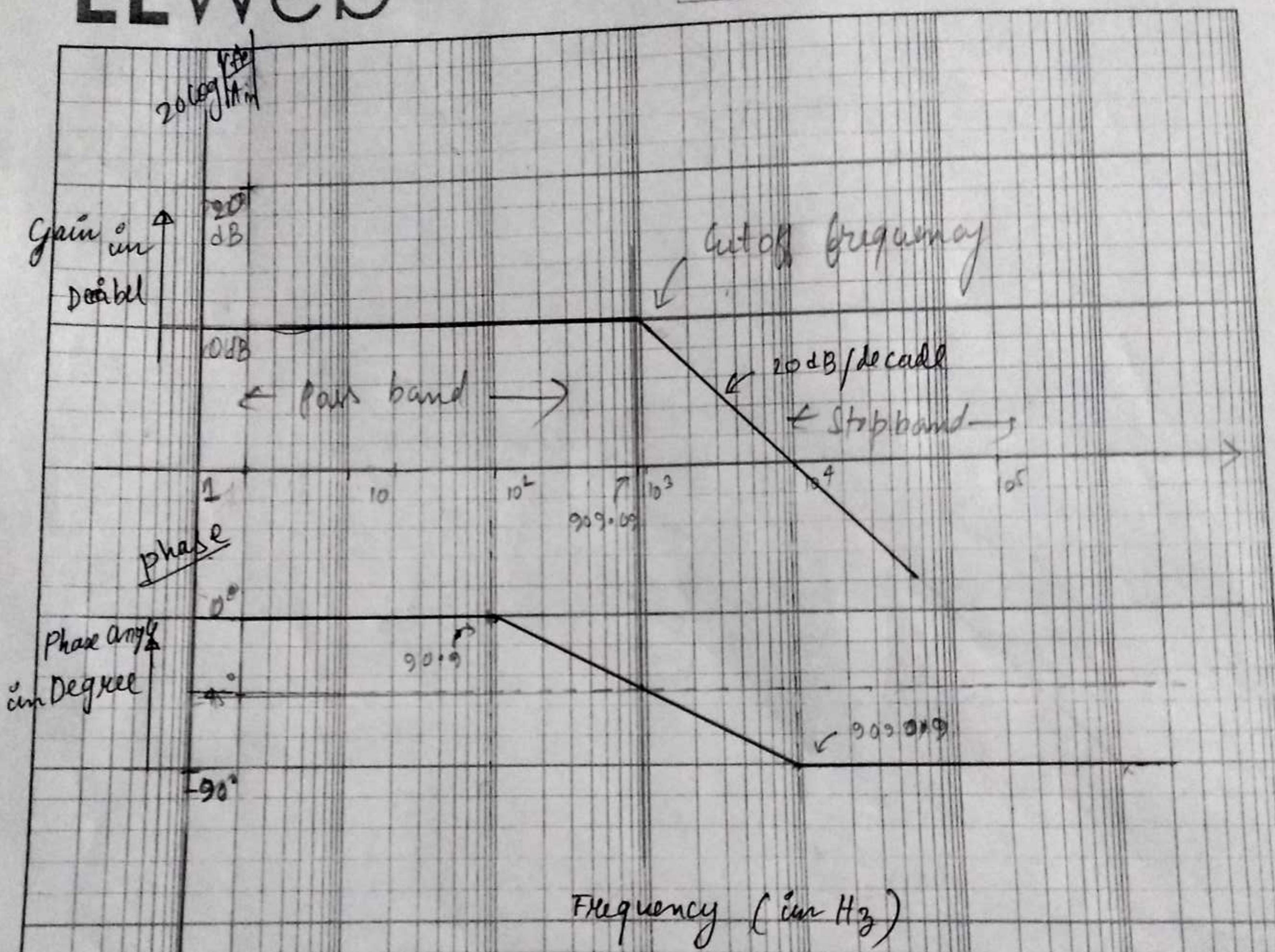


Transfer Function = $\left(\frac{1}{1 + \frac{s}{909.09}} \right)$

at 86 frequency

EEWeb

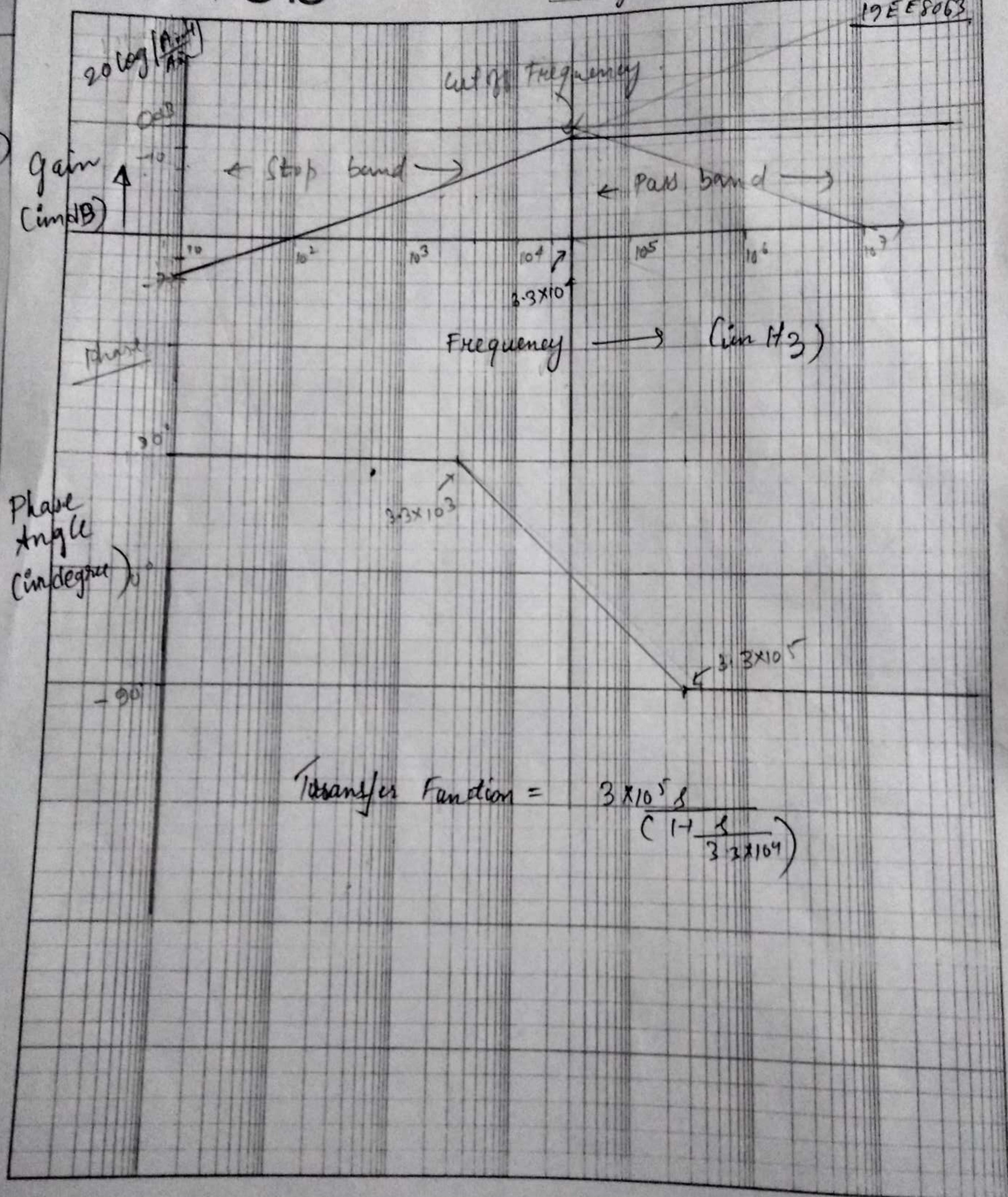TITLE Frequency Response of High pass RLCKT
NAME Sayan Mondal DATE 5/02/11
19EE8063



at N frequency

$$\Rightarrow Tf \omega = \frac{1}{1+RC} \quad (\text{Transfer function})$$

$$\therefore \text{cut off frequency} \Rightarrow \omega = \frac{1}{RC}$$

$$\therefore \omega = 0.909 \cdot \frac{1}{1.14162 \times 10^{-6}} \\ = 909.09$$

$$\therefore \text{and } f = \frac{1}{2\pi RC}$$

$$\approx 289.0519 \text{ Hz}$$

2) For RL circuit

$$Tf = \frac{L}{(R + \frac{L}{f})}$$

$$\therefore \text{cut off frequency} \Rightarrow f = \frac{1}{2\pi RL} \frac{R}{2\pi L}$$

$$= \frac{100}{2 \times 3.14 \times 33 \times 10^{-3}}$$

$$= 5.307 \times 10^3 \text{ Hz}$$

Experiment - 5.

Determination of z and y parameters (dc
only) for two port network

Experiment No. EE 1451 / 05

Title - Determination of Z and Y parameters (dc only) for two port network.

Objectives -

1. To calculate and verify Z parameters of two port network
2. To calculate and verify Y parameters of two port network.

Theory

Z parameter.

$$V_1 = Z_{11} I_1 + Z_{12} I_2 \quad \dots \quad (i)$$

$$V_2 = Z_{21} I_1 + Z_{22} I_2 \quad \dots \quad (ii)$$

Here, Z_{11} \leftarrow input driving point impedance
 Z_{12} \leftarrow output driving pt. impedance

$Z_{21} \leftarrow$ reverse } transfer impedance.
 $Z_{22} \leftarrow$ forward }


Now, $Z_{11} = \frac{V_1}{I_1}$ at $I_2 = 0$;

$$Z_{21} = \frac{V_2}{I_1} \text{ at } I_2 = 0 ;$$

$$Z_{12} = \frac{V_1}{I_2} \text{ at } I_1 = 0 ;$$

$$Z_{22} = \frac{V_2}{I_2} \text{ at } I_1 = 0 ;$$

Circuit Diagram

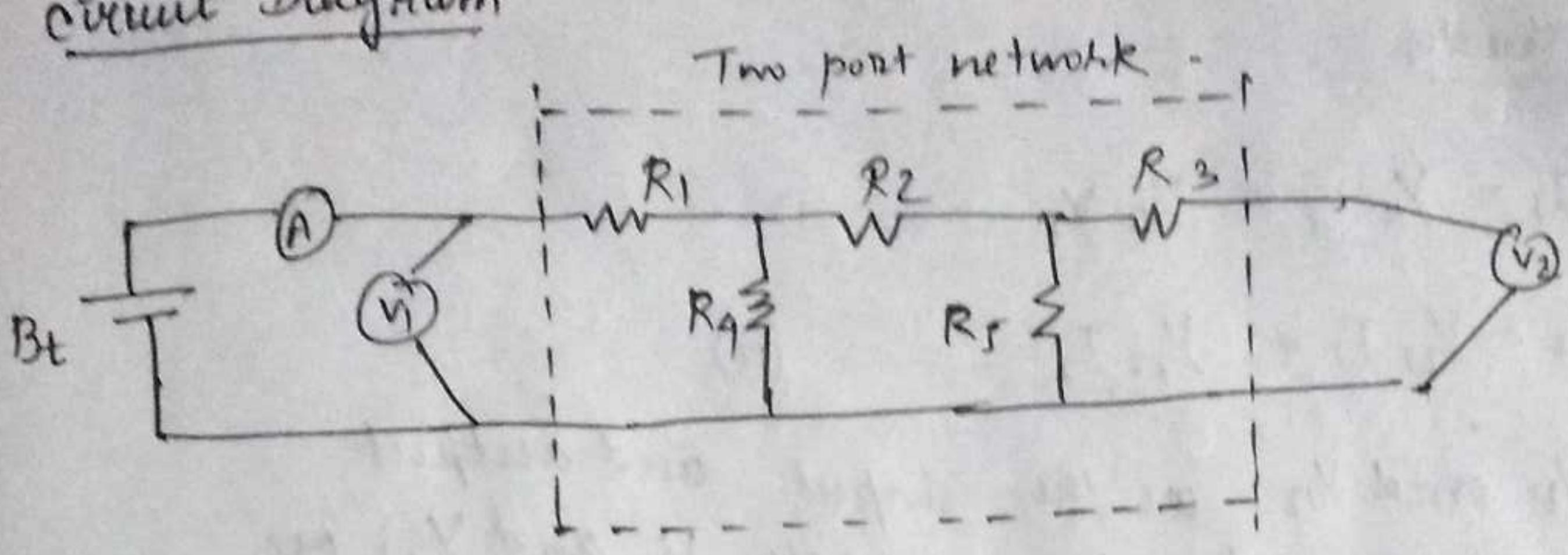

10
8
9
~~10~~
X
E T

Observation Table

For Z parameters

	When input port is open circuited			When output port is open circuited		
	V ₁ (V)	V ₂ (V)	I ₂ (A)	V ₁ (V)	V ₂ (V)	I ₁ (A)
1)	2.2	9.0	0.2	10.8	2.25	0.2
2)	4.45	19.8	0.4	19.8	4.35	0.4
3)	4.9	21.6	0.42	25.2	4.75	0.41

Verification table

Parameters	Practical Values (Ω)
Z ₁₁	-59
Z ₁₂	11
Z ₂₁	11.25
Z ₂₂	48

Result

	Parameter (Practical)	Parameter (Theoretical)	% error = Practical - Theory / Theory
Z ₁₁	54 Ω	44.57 Ω	21.1%
Z ₁₂	11 Ω	11.11 Ω	0.9%
Z ₂₁	11.25 Ω	11.11 Ω	1.26%
Z ₂₂	48 Ω	43.65 Ω	10.1%

Y parameter

$$I_1 = Y_{11} V_1 + Y_{12} V_2 \quad \text{--- (i)}$$

$$I_2 = Y_{21} I_1 + Y_{22} I_2 \quad \text{--- (ii)}$$

Here Y_{11} and Y_{12} are the input and output driving pt. admittances while Y_{21} and Y_{22} are the reverse and forward transfer admittances


$$\text{Now, } Y_{11} = \frac{I_1}{V_1} \text{ at } V_2 = 0$$

$$Y_{21} = \frac{I_2}{V_1} \text{ at } V_2 = 0$$

$$Y_{12} = \frac{I_1}{V_2} \text{ at } V_1 = 0$$

$$Y_{22} = \frac{I_2}{V_2} \text{ at } V_1 = 0$$

Circuit Diagram.

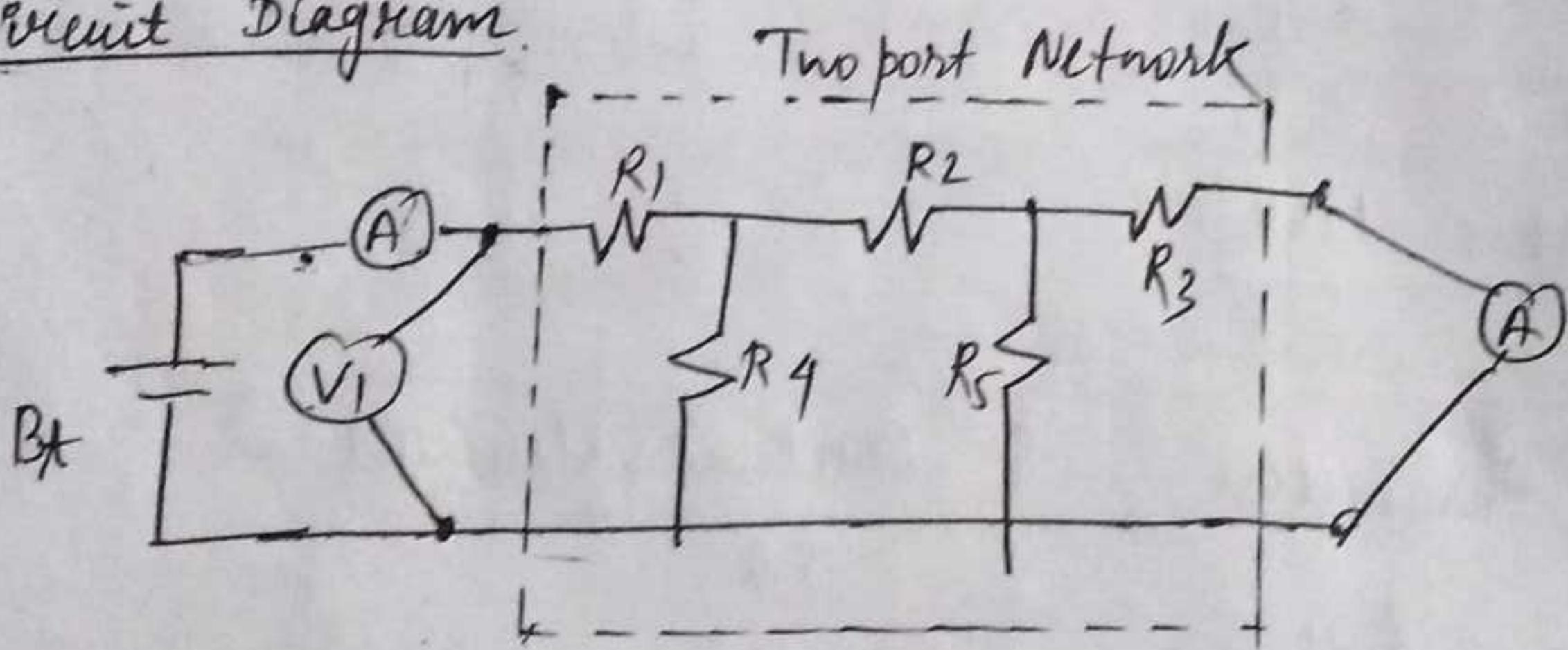

Observation Table.

Y parameter.

	When input is short circuited			When output is short circuited		
	$V_2(V)$	$I_1(A)$	$I_2(A)$	$V_1(V)$	$I_1(A)$	$I_2(A)$
1.	9.6	0.06	0.2	10.8	0.2	0.04
2.	18.0	0.1	0.4	19.6	0.4	0.1
3.	27.6	0.12	0.6	27.6	0.6	0.12

Verification Tab4

<u>Parameters</u>	<u>Practical Values</u>
y_{11}	0.018
y_{12}	6.25×10^{-3}
y_{21}	3.7×10^{-3}
y_{22}	0.02

Results

γ parameters

γ -parameter (practical)	γ -parameter (theoretical)	% error
$0.018 \Omega^{-1}$	$0.02 \Omega^{-1}$	101.
$-6.25 \times 10^{-3} \Omega^{-1}$	$-0.01 \Omega^{-1}$	57.51.
$-3.7 \times 10^{-3} \Omega^{-1}$	$-0.01 \Omega^{-1}$	63.1.
$0.02 \Omega^{-1}$	$0.02 \Omega^{-1}$	0%

Experiment - 6

Magnetically Coupled circuit

cal Values

10⁻³

=

2

wf

Title: Magnetically coupled Circuit

Objective -

1. Determination of self inductance, mutual inductance and coefficient of coupling for a magnetic coupled circuit.
2. Determination of driving point and transfer impedance of a coupled circuit.

Mutual Inductance
the m
turns co
by the
induct
as
link
this

Theory:

- Consider a single coil wound around a magnetic core as shown in fig. below.

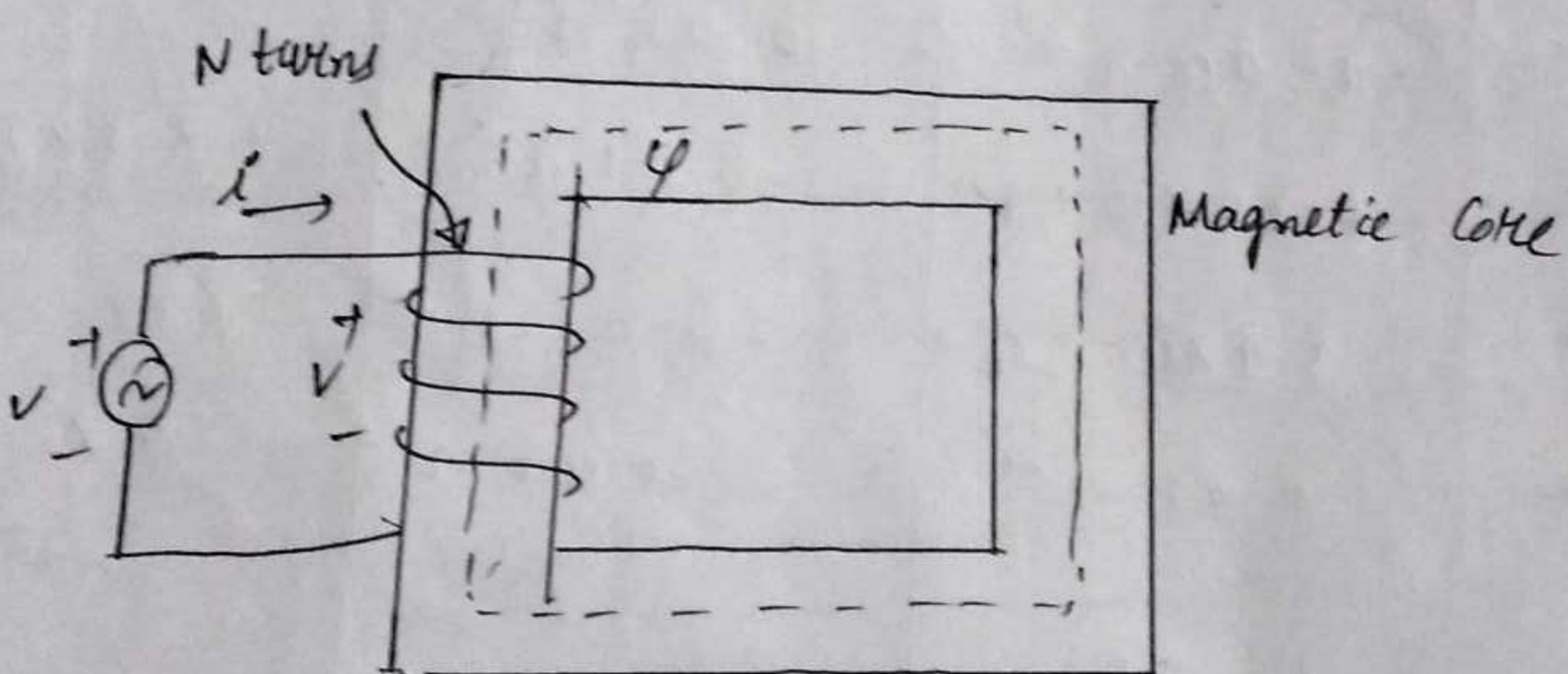


Fig. Single coil wound around a magnetic core.

A time varying current produces an induced voltage v across the coil terminals

$$\Rightarrow v = N \frac{d\phi}{dt} \quad \text{--- (i)}$$

→ The self inductance of the coil is defined as the ratio between the flux linkage, N , ϕ linking the coil and the current I , producing the flux

$$\text{So, } L = N \frac{d\phi}{dI} \quad \text{--- (ii)}$$

$V_1 =$

V_2

Whl

→ Substituting from equation (2) into (1) gives

$$V = L \frac{di}{dt} \quad \dots \dots (3)$$

Mutual Inductance: If a second coil is wound around the magnetic core of fig-1 as shown in fig 2 the two coils are magnetically coupled. The flux produced by the first links the second. The mutual inductance M_{12} , between coils 1 & 2 is defined as the ratio between the flux linkage, $N_2 \phi$ linking the coil 2, and the current i_1 producing this flux.

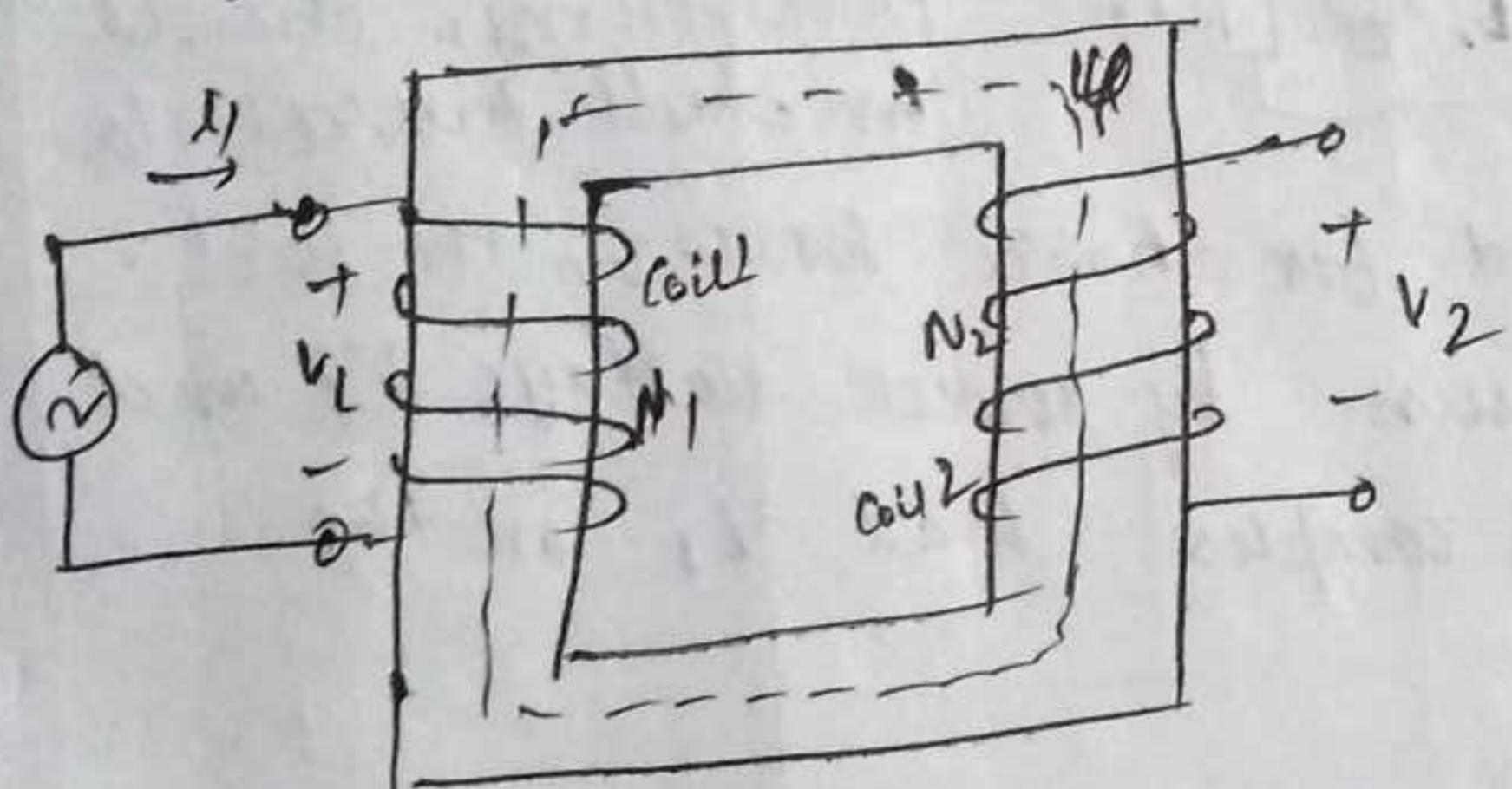


Fig-2: Two magnetically coupled coils

Therefore,

$$M_{12} = \frac{N_2 \frac{\Phi}{t}}{i_1} \quad \dots \dots (4)$$

when the terminals of coil 2 are open circuited, ie. no current flowing in the coil 2, then the following equations can be written-


$$V_1 = \frac{d}{dt} (N_1 \Phi) = L_1 \frac{di_1}{dt} \quad \dots \dots (6)$$

$$V_2 = \frac{d}{dt} (N_2 \Phi) = \pm M_{12} \frac{di_1}{dt} \quad \dots \dots (5)$$

Where V_2 is the induced voltage in coil 2 due to current i_1 in coil 1.

Coefficient of coupling - A small amount of flux produced by the core leaks away from the core. This is known as leakage flux. The measurement of leakage flux is the coefficient of coupling k and can be expressed as $k = \frac{M}{\sqrt{L_1 L_2}} \dots (i)$

Input Impedance -

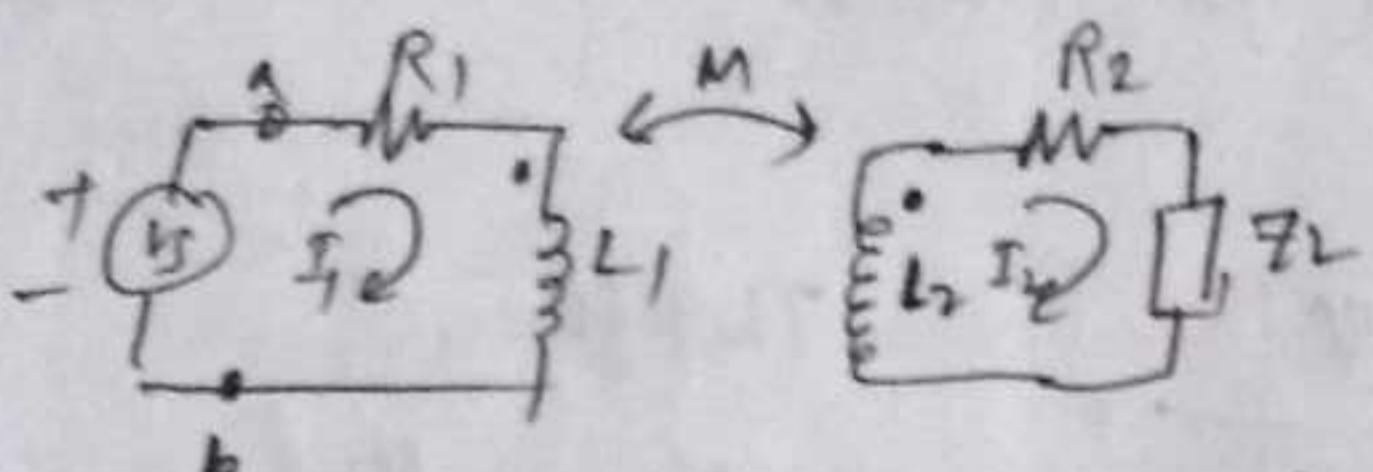

In addition to the coupled coils a realistic transformer should include two resistors

R_1 and R_2 to account for ohmic losses in the coil. The circuit is driven by source voltage V_s and terminated on the complex load Z_L on the secondary side.

In terms of designated mesh currents I_1 and I_2 the KVL equations are -

$$V_s = I_1 R_1 + j\omega L_1 I_1 - j\omega M I_2 \dots (i)$$

$$\text{and } 0 = I_2 R_2 + j\omega L_2 I_2 - j\omega M I_1 + E_2 Z_L \dots (ii)$$

The input driving point is given by

$$Z_D = \frac{V_s}{I_1} = R_1 + j\omega L_1 + \frac{j\omega^2 M^2}{R_2 + j\omega L_2 + Z_L}$$

$$= R_1 + j\omega L_1 + Z_R \dots \text{(iii) answer}$$

Z_R is defined as reflected impedance and given by


$$Z_R = \frac{j\omega^2 M^2}{R_2 + j\omega L_2 + Z_L}$$

In a similar manner we can derive the expression for transfer impedance -

$$Z = \frac{V_2}{I_2} = j$$

Sl. No.	Fun
1.	
2.	
3.	
4.	
5.	
6.	
7.	
8.	
9.	
10.	
11.	

llo scope

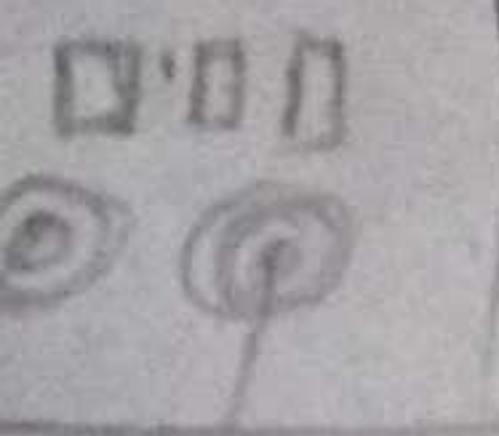

Experiment - 5

Circuit Diagram

D Determination of self Inductance L_1 & L_2

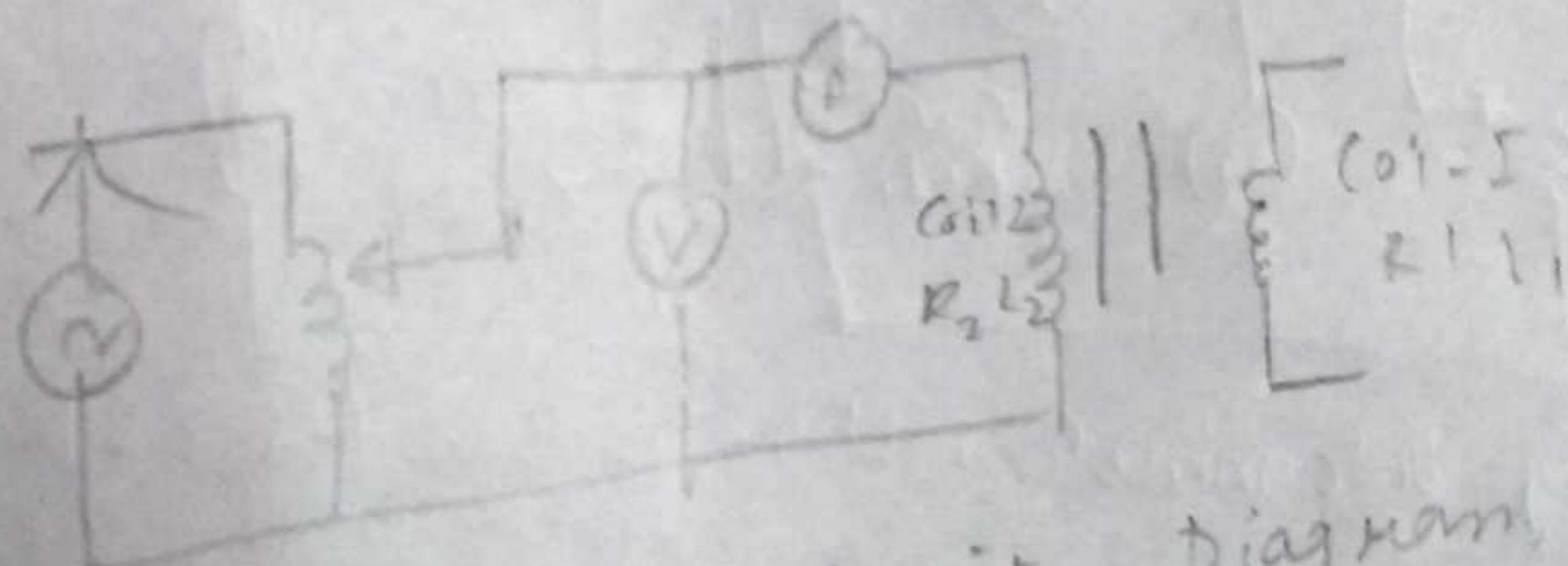
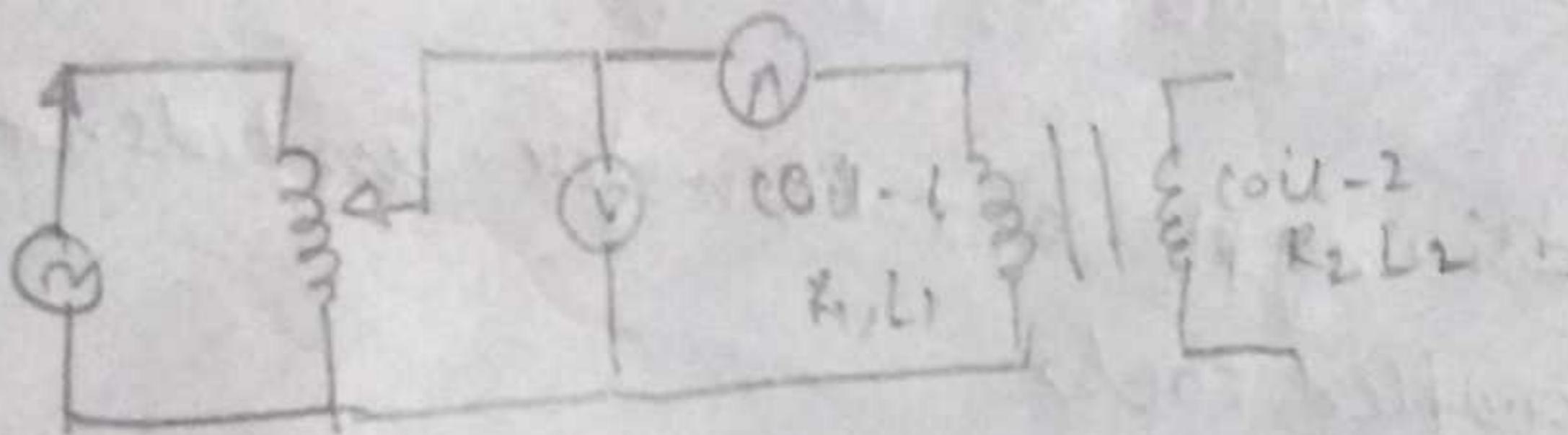


Fig. Circuit Diagram for L_1 , L_2

II) Determination of mutual Inductance.

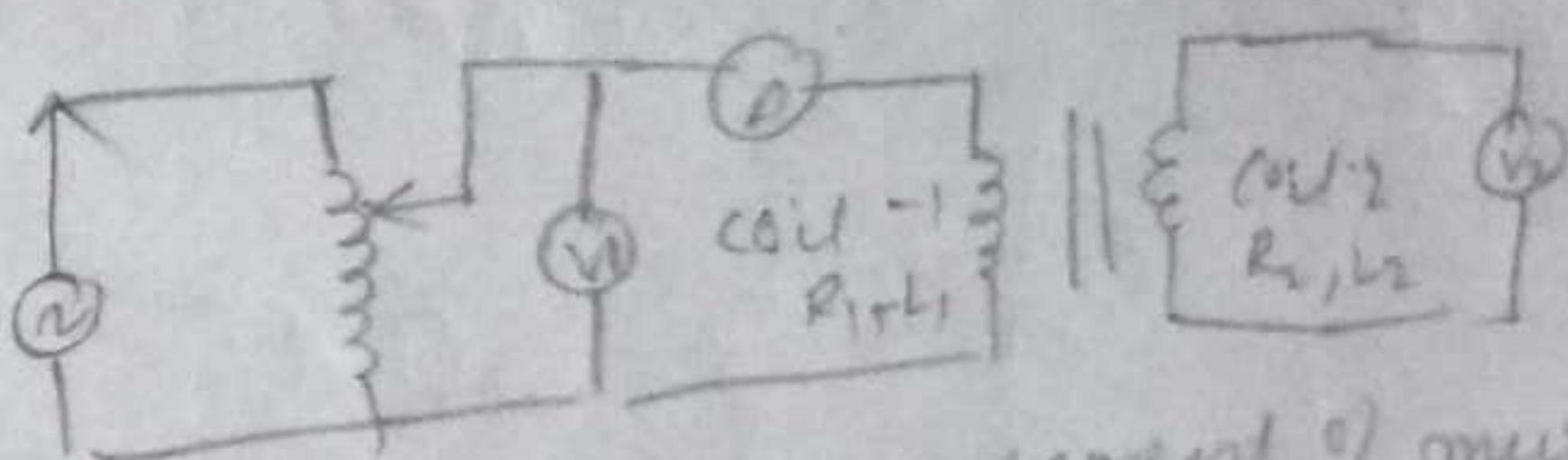


Fig - measurement of mutual inductance

III) Determination of Polarity of Magnetically Coupled Coils

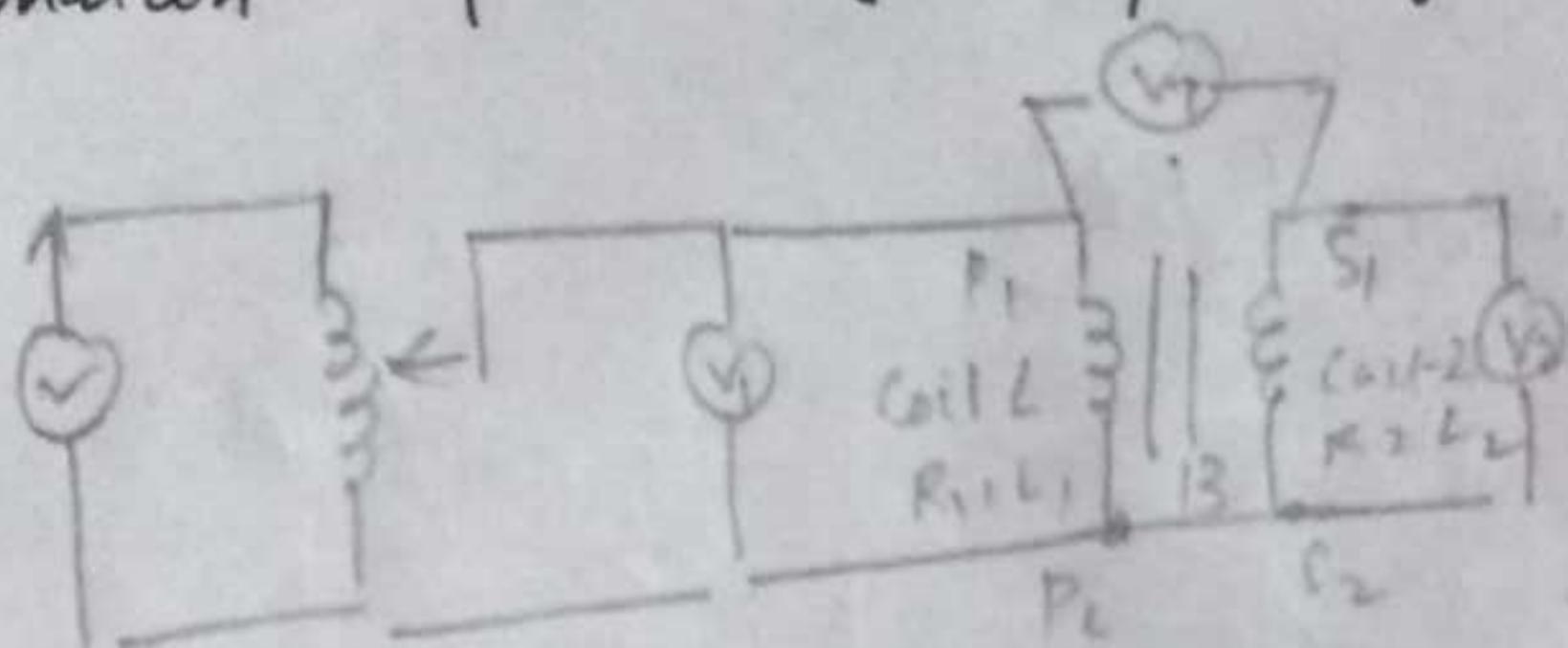


Fig - Determination of polarity

IV) Series-Connected Magnetically Coupled Coils

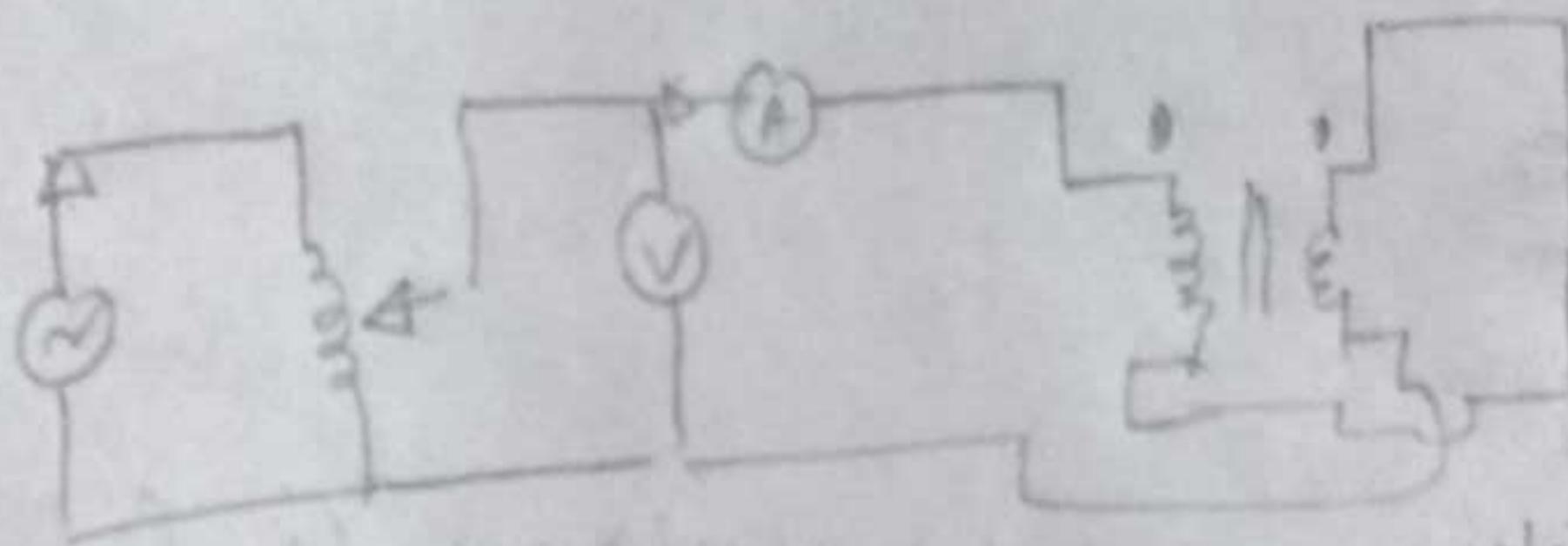


Fig - Series Connected magnetically coupled coils (adding)

V) Determination of driving pt. and transfer impedance of magnetically coupled coils.

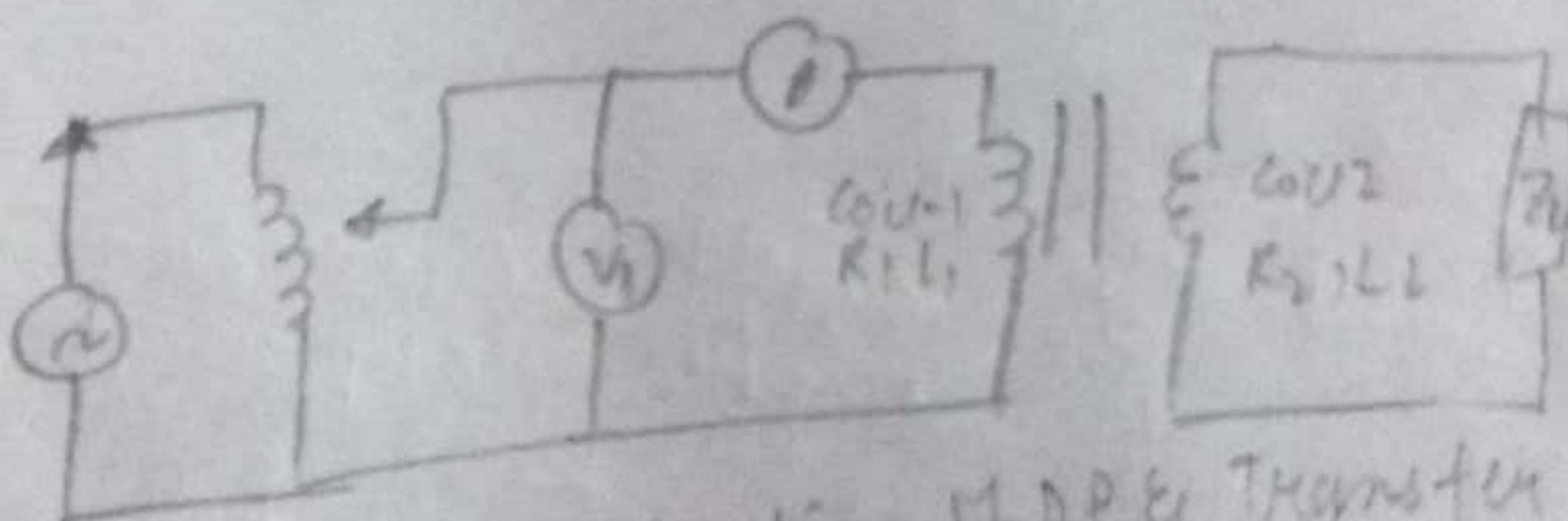


Fig - Determination of DP & Transfer Impedance

Experiment - 6

Observation Tab^{le}

Table 1: Determination of Resistance.

Current Exchanging (Am A)	Primary Winding					Secondary Windings					$R_{dc} = R_s$ $E = I$
	Supply Voltage (v)	Ammeter Reading I_1 (A)	Voltmeter Reading (v)	R_{dc} (Ω)	$R_{dc} = R_s$ $= 1.6 R_{dc}$ $E = I$	Supply Voltage (v)	Ammeter Reading I_2 (A)	Voltmeter Reading (v)	R_{dc} (Ω)	$R_{dc} = 1.15 R_{dc}$ (Ω)	
0.399											
0.1467	3.44	1	1.7	1.7	1.45	3.44	11	1.8	1.6363	1.58	
0.5399											
0.19865											
8.81×10^{-5}											
8.5×10^{-5}											
9.64×10^{-6}											

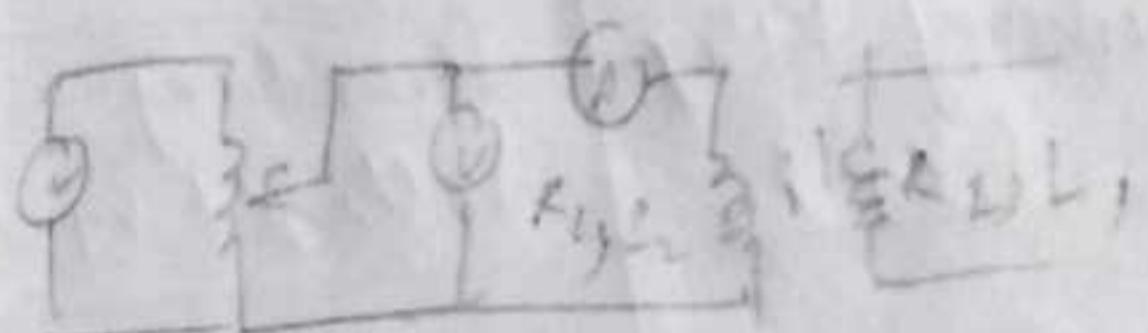
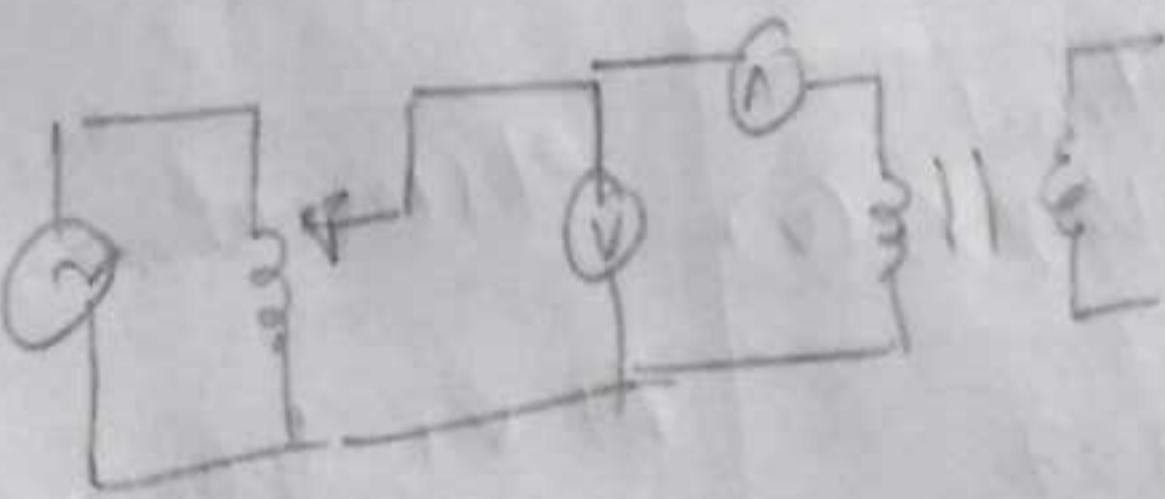
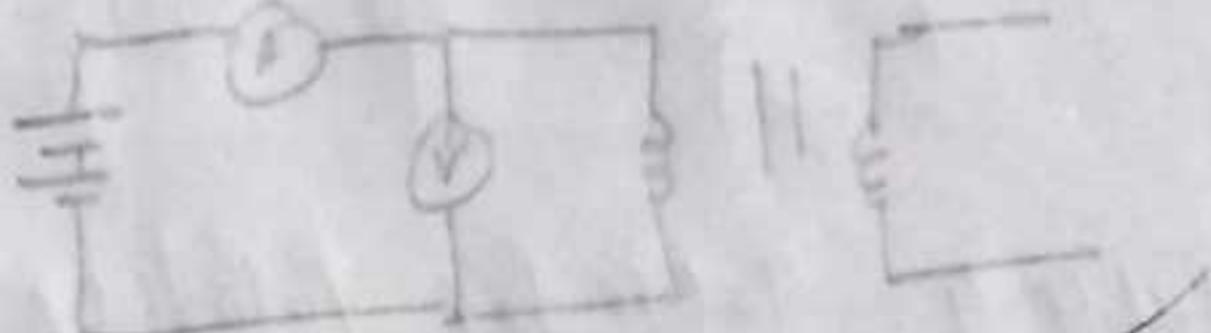
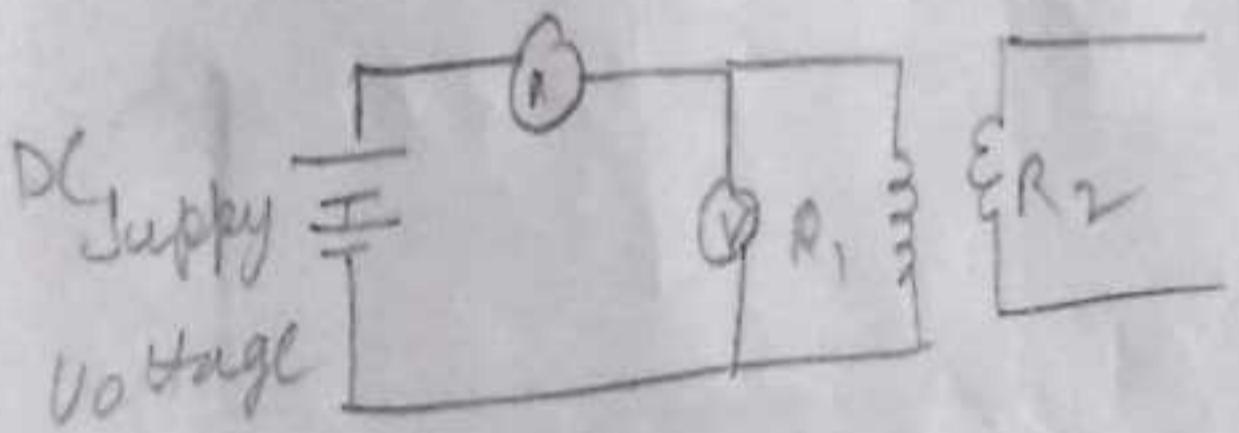


Table 2: Determination of Self Inductance.

Winding Side	Voltage Applied V_1 (v)	Current flow I_1 (A)	Net Impedance Z_1 (Ω)	Net reactance X_1 (Ω)	Self Inductance $L = X_1/I_1$ (H)
P Primary	210	0.3	700	699.99	2.22
Secondary	110	0.5	220	219.9	0.7

Table 3: Determination of mutual inductance

Sl. No.	Secondary Voltage V_2 (v)	Primary Voltage and Current	$\gamma_m = \frac{V_2}{I_1}$ (n)	Mutual Inductance $M = \gamma_m / \pi l_{yy}$	Voltage (PP)
1.	96V	V_1 I_1 200V 0.2A	480nH	652	180
2.	102V	210V 0.3A	340nH	108	110

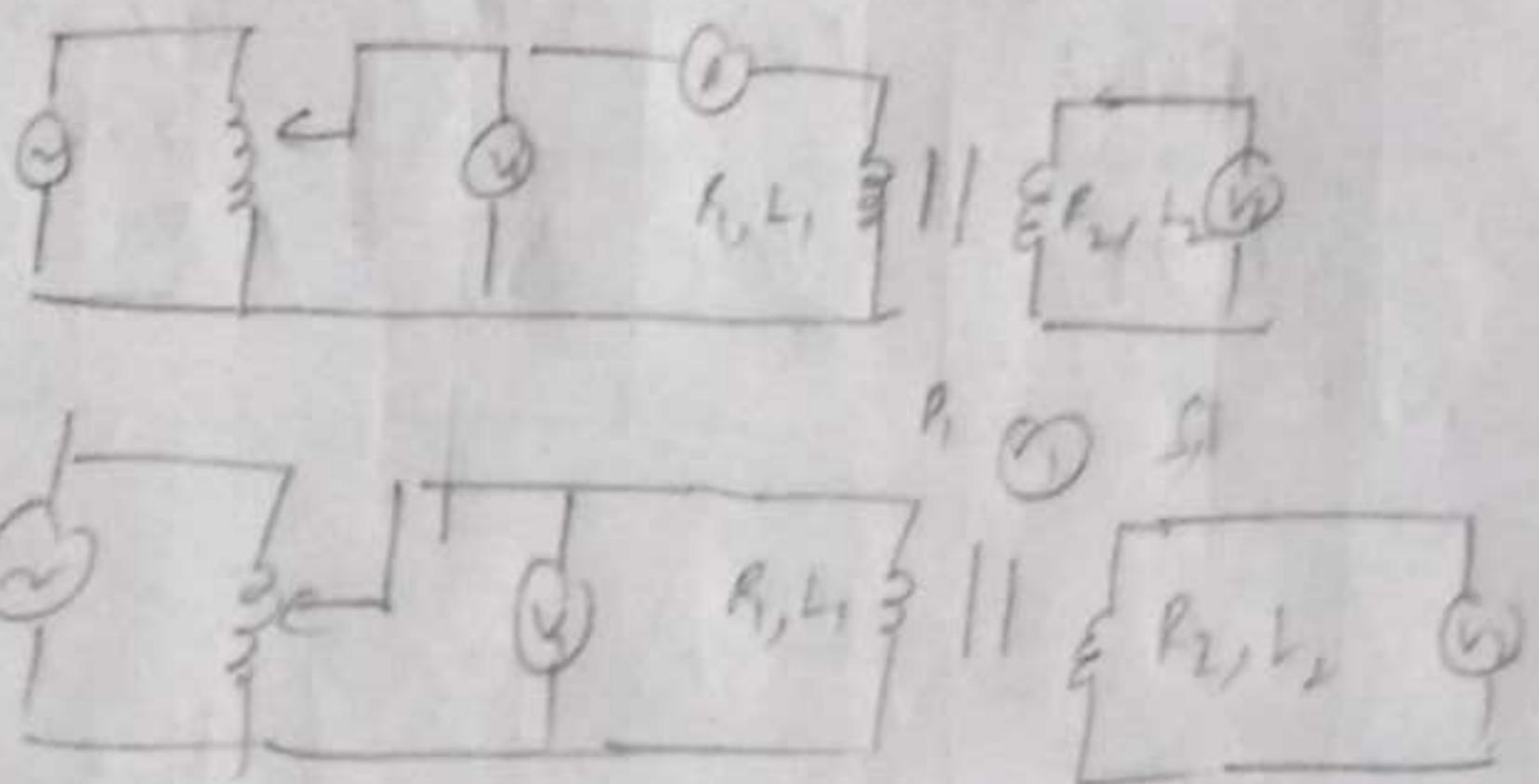


Table 4: Table for Polarity Test

Primary Voltage (V_1)	Secondary Voltage (V_2)	Resultant Voltage V_T (v)	Observation
200	103	297	At V_T found from experiment is the addition of the 2 induced voltages i.e., V_1 & V_2
210	109	311	is its opposite polarity dots are on opposite side

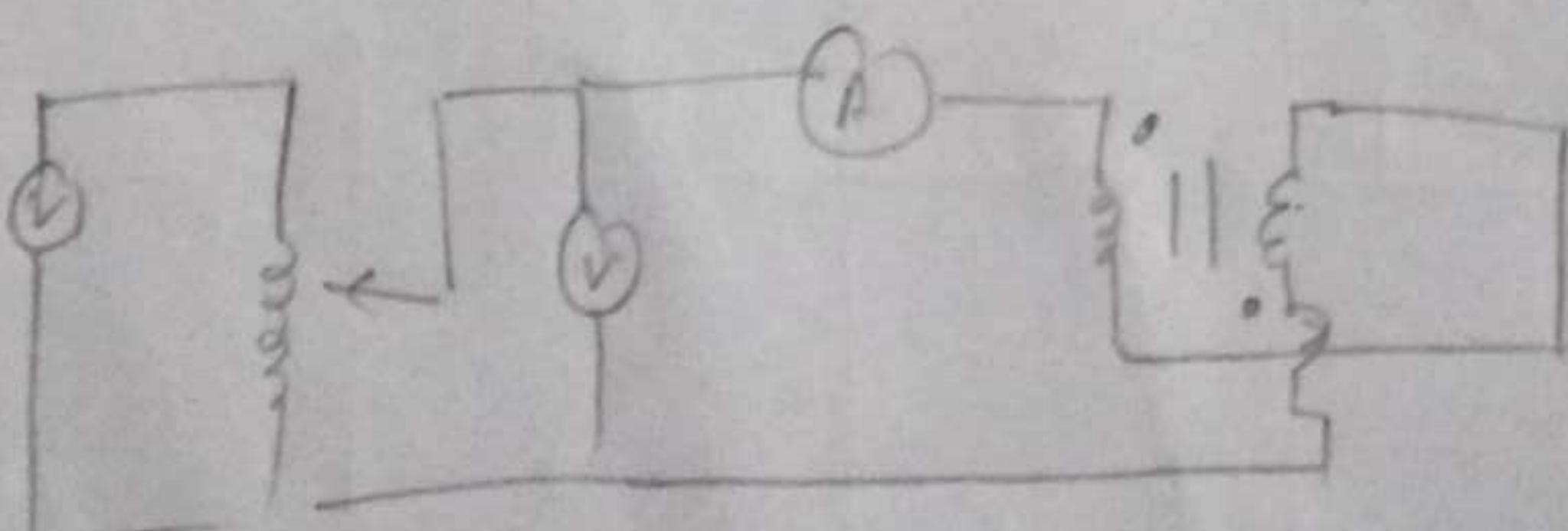


Table 5: Determination of magnetic reactance for series connected coupled coils.

Voltage Applied (V_1)	Current I_1 (A)	Net impedance $Z_1 = V_1/I_1$ (Ω)	$X_{eq} = \sqrt{Z_1^2 - (R_1 + R_2)^2}$ (Ω)
100	0.25	400	$400 - 9 = X_{eq}$ (connected as per polarity)
110	0.44	250	299.97
100	0.51	190	$191.9 = X_{eq}$ (connected in opp.)
110	0.77	142.85	145.0

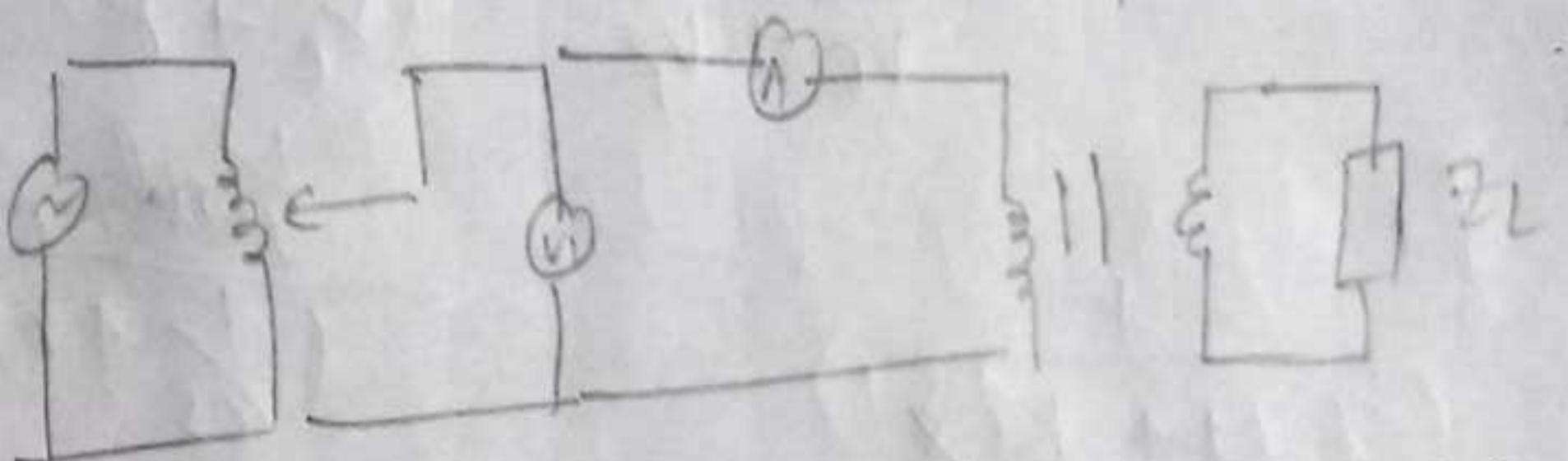


Table 6: Determination of driving pt. & transfer impedance

Primary Voltage (V_1)	Primary current (A)	Secondary current (I_2) (A)	Driving pt. impedance $Z_0 = V_1/I_1$ (Ω)	Transfer Impedance $Z_T = \frac{V_1}{I_1}$ (Ω)
200	0.36	6.59	555.55	370.32
210	0.42	5.5	500.00	420.2

Table 7: Comparison b/w measured values of Z_0 and Z_T

	Measured	Calculated
Driving pt. Impedance Z_0 (Ω)	555.5	335.59
Transfer Impedance Z_T (Ω)	370.3	477.88